




Convertidores con aislamiento

Objetivos


- ⚡ Aislamiento entre entrada y salida por requisitos de seguridad**
- ⚡ Reducción eliminación del transformador de línea por uno de alta frecuencia**
- ⚡ Minimizar los estreses de corriente y tensión cuando se precisan grandes relaciones de conversión (n)**
- ⚡ Obtener varias tensiones de salida**

Modelo simple de transformador

Multiple winding transformer

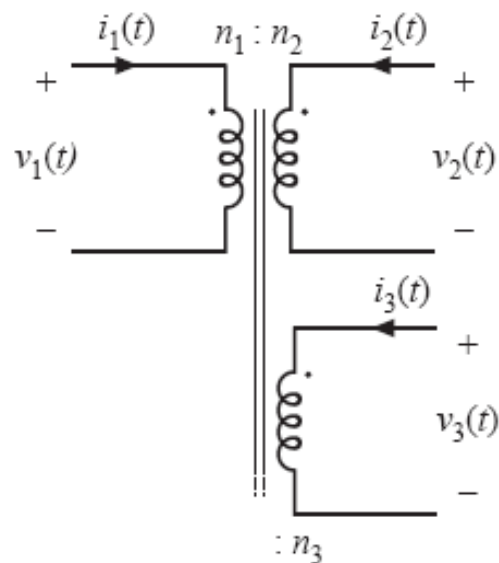

Equivalent circuit model

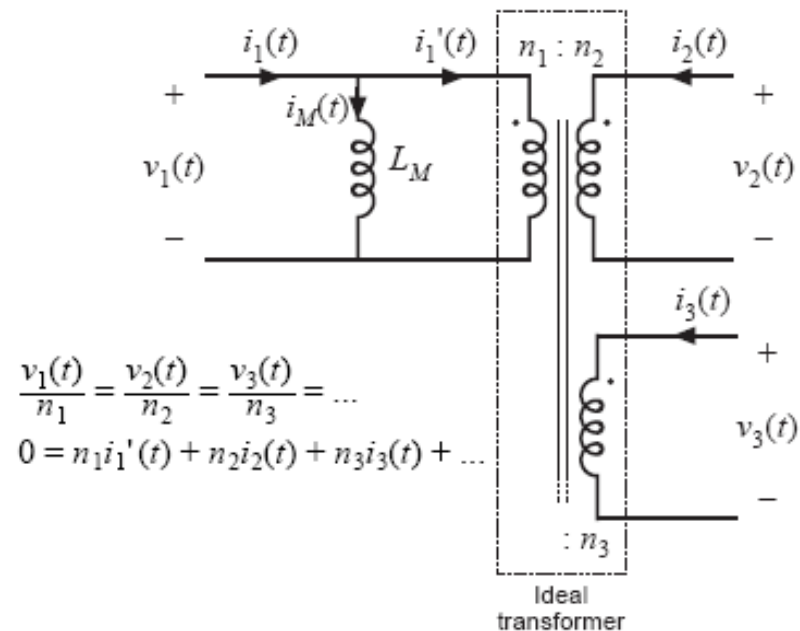

Balance de voltios-segundo

The magnetizing inductance is a real inductor, obeying


$$v_1(t) = L_M \frac{di_M(t)}{dt}$$

integrate:

$$i_M(t) - i_M(0) = \frac{1}{L_M} \int_0^t v_1(\tau) d\tau$$

Magnetizing current is determined by integral of the applied winding voltage. The magnetizing current and the winding currents are independent quantities. Volt-second balance applies: in steady-state, $i_M(T_s) = i_M(0)$, and hence
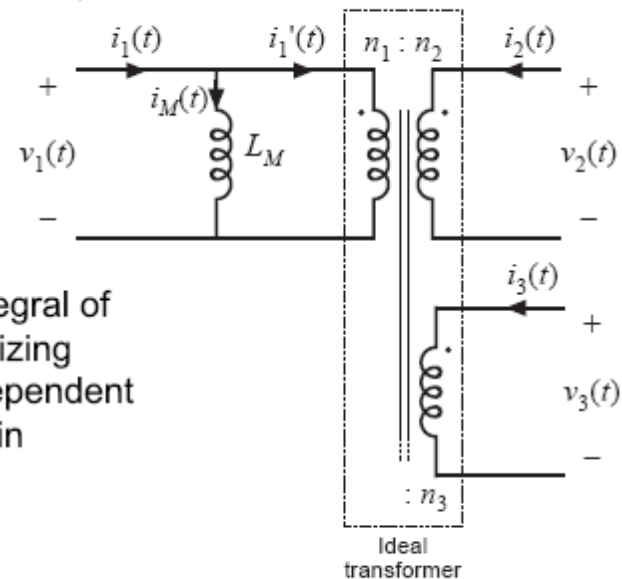
$$0 = \frac{1}{T_s} \int_0^{T_s} v_1(t) dt$$




Reset del transformador

Mecanismo para obtener
Balance voltios-segundo de la inductancia magnetizante




Puente completo

Full-bridge isolated buck converter

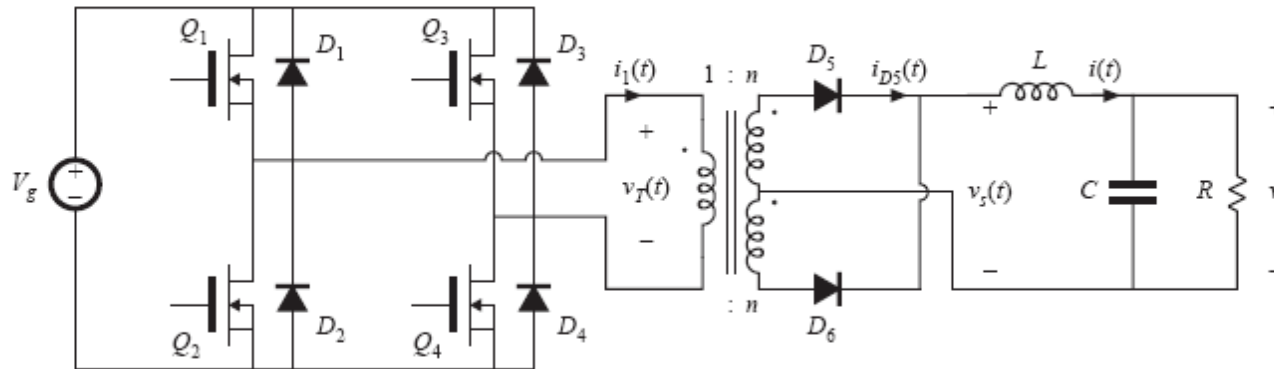


Circuito equivalente del transformador

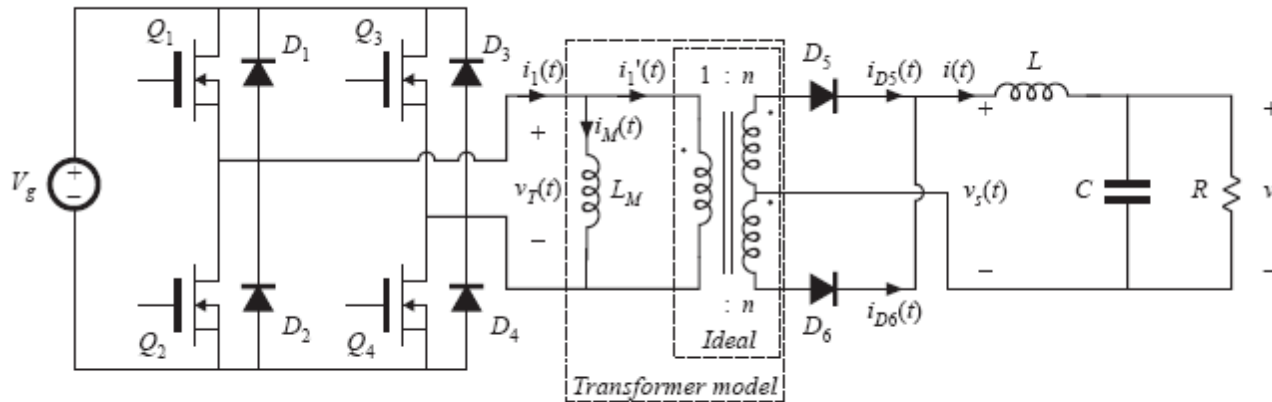

Puente completo

Formas de onda

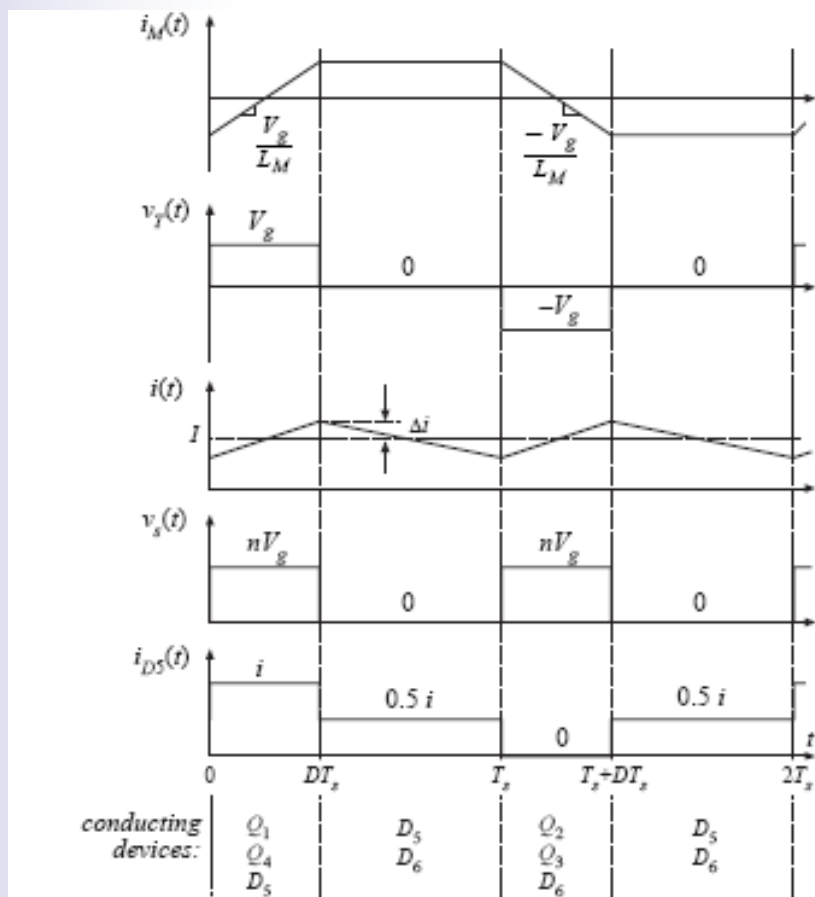

- During first switching period: transistors Q_1 and Q_4 conduct for time DT_s , applying volt-seconds $V_g DT_s$ to primary winding
- During next switching period: transistors Q_2 and Q_3 conduct for time DT_s , applying volt-seconds $-V_g DT_s$ to primary winding
- Transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities?

Efecto de no idealidades

Volt-seconds applied to primary winding during first switching period:

$$(V_g - (Q_1 \text{ and } Q_4 \text{ forward voltage drops}))(Q_1 \text{ and } Q_4 \text{ conduction time})$$

Volt-seconds applied to primary winding during next switching period:

$$-(V_g - (Q_2 \text{ and } Q_3 \text{ forward voltage drops}))(Q_2 \text{ and } Q_3 \text{ conduction time})$$

These volt-seconds never add to *exactly* zero.

Net volt-seconds are applied to primary winding


Magnetizing current slowly increases in magnitude

Saturation can be prevented by placing a capacitor in series with primary, or by use of current programmed mode (Chapter 12)




Puente completo

Operación de los diodos de secundario

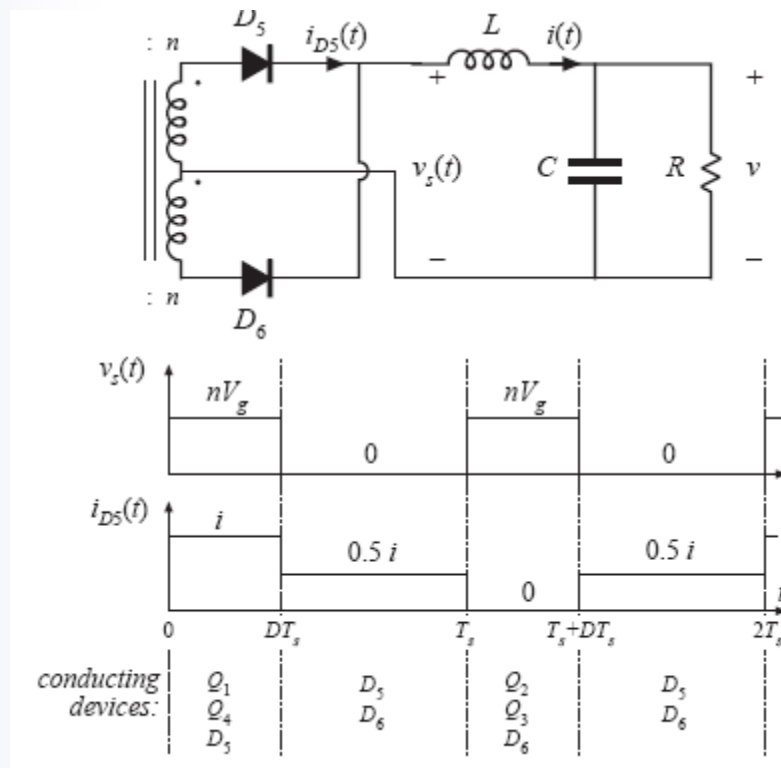

Puente completo


Balance voltios-segundo L secundario

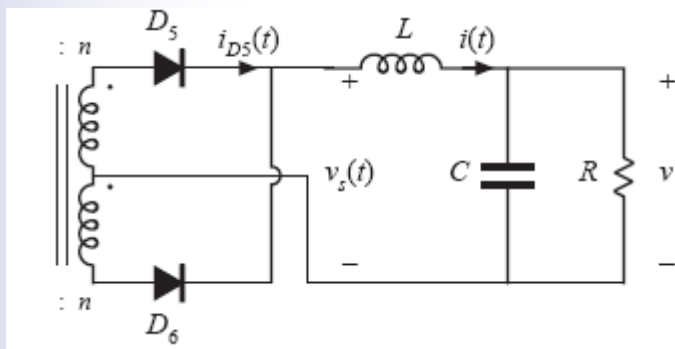

$$V = \langle v_s \rangle$$


$$V = nDV_g$$

$$M(D) = nD$$

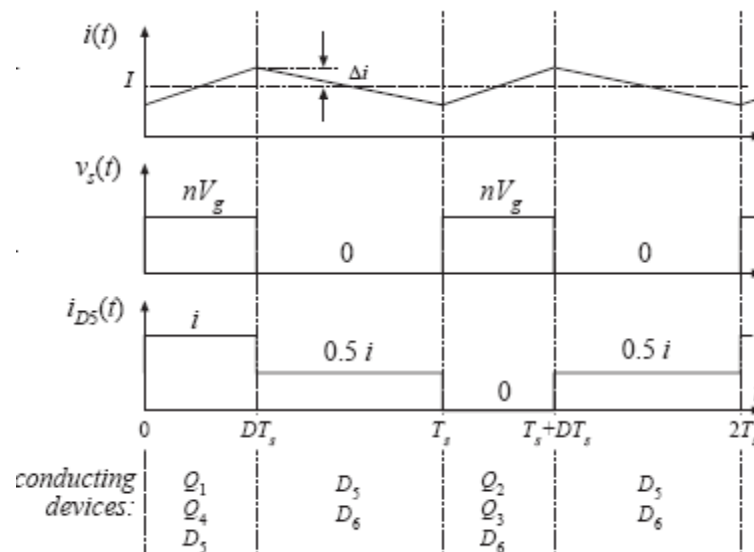


Convertidor reductor con relación de vueltas

Medio puente con aislamiento

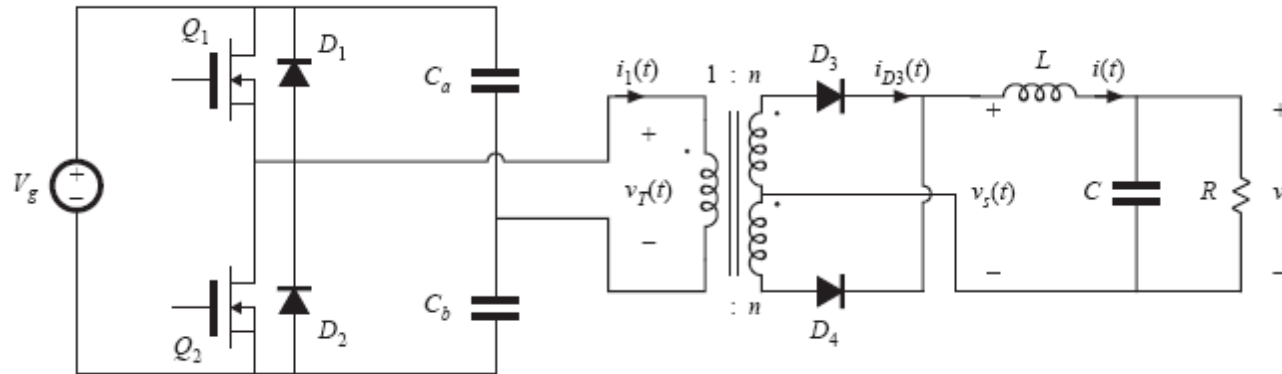


- Replace transistors Q_3 and Q_4 with large capacitors
- Voltage at capacitor centerpoint is $0.5V_g$
- $v_s(t)$ is reduced by a factor of two
- $M = 0.5 nD$

Convertidor directo (forward)

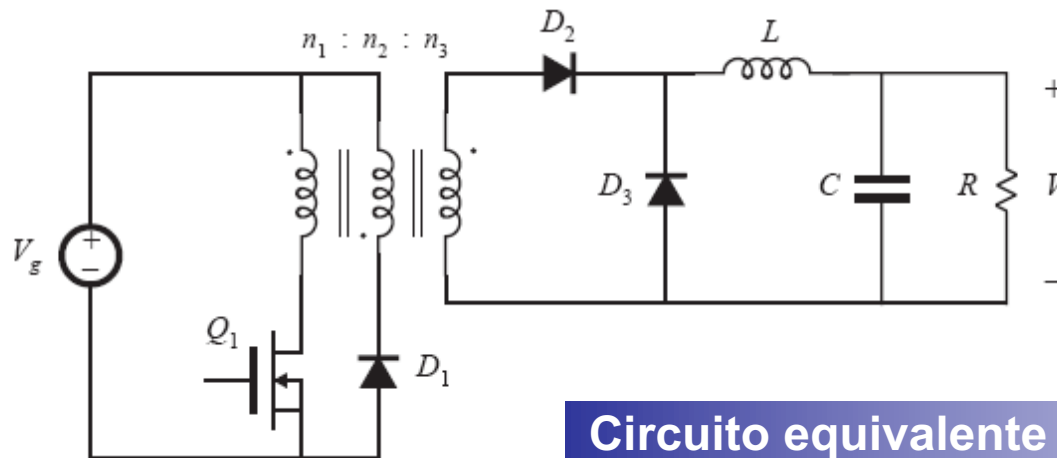

- + • Buck-derived transformer-isolated converter
- Single-transistor and two-transistor versions
- Maximum duty cycle is limited
- • Transformer is reset while transistor is off



Circuito equivalente

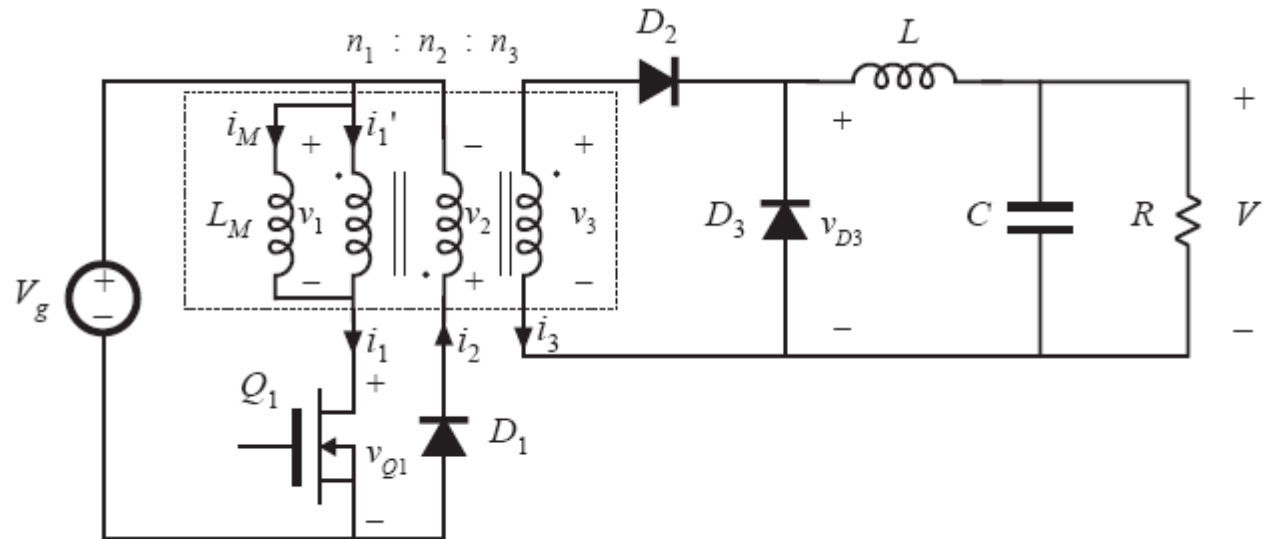



Convertidor directo (forward)



Formas de onda I

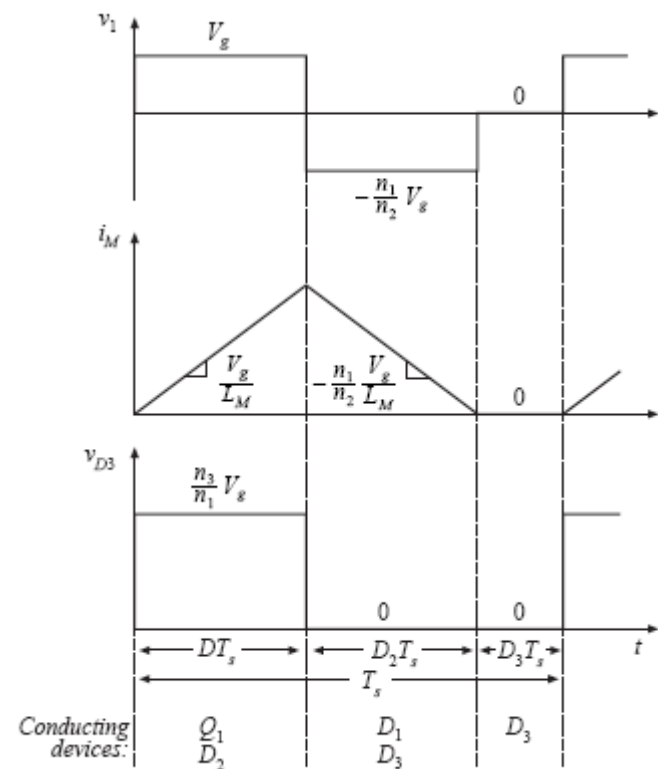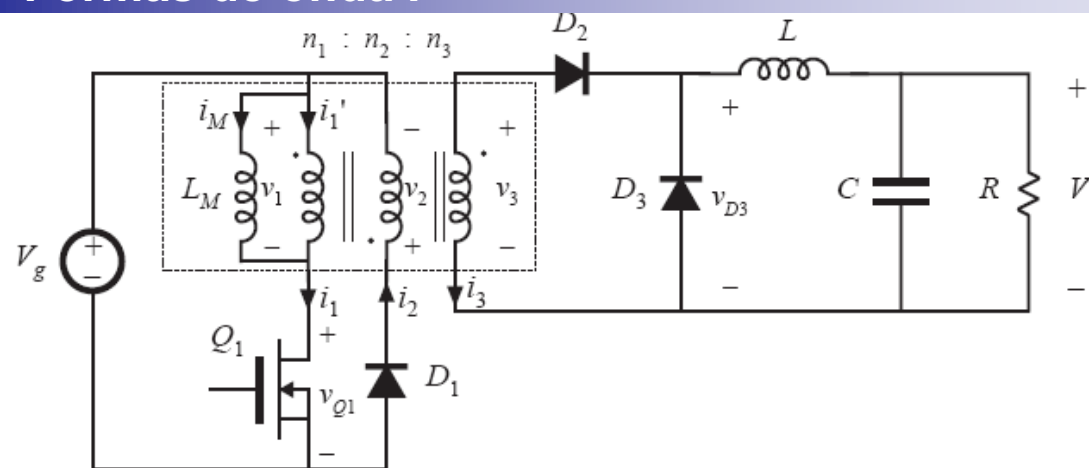





Convertidor directo (forward)

Formas de onda II

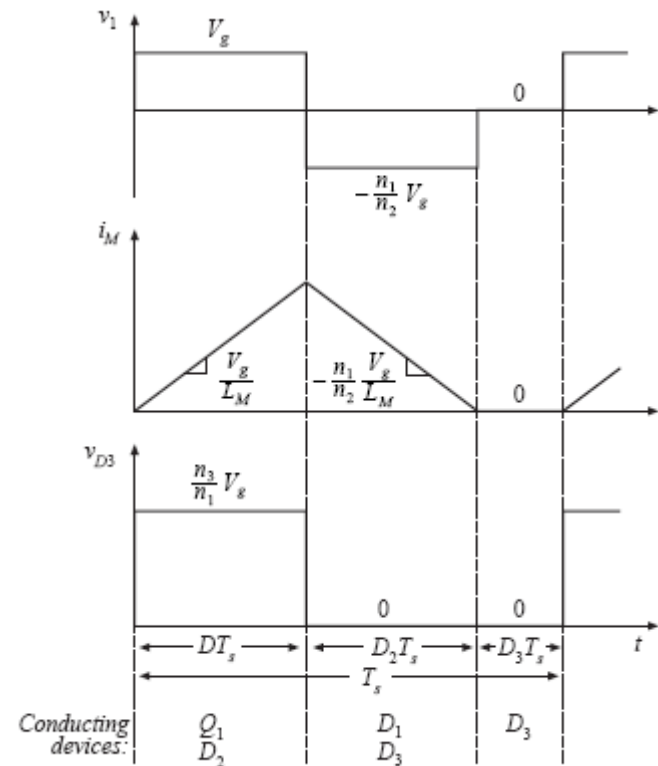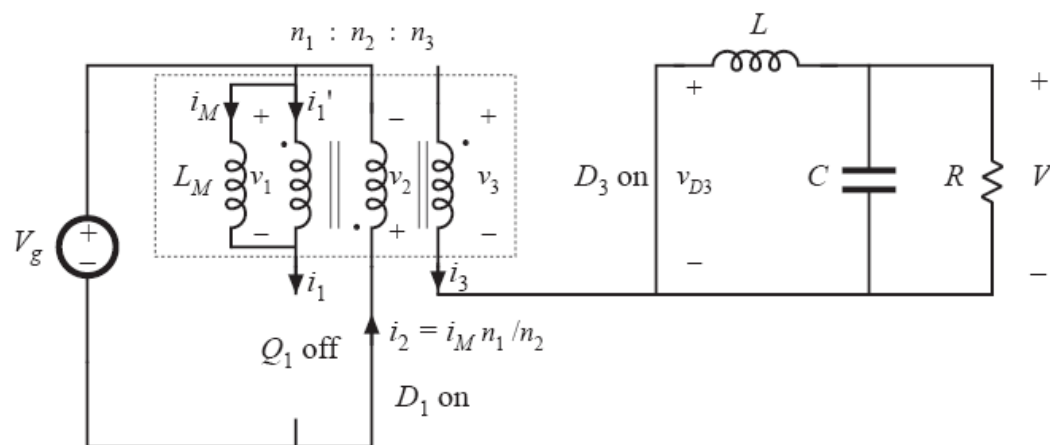

Convertidor directo (forward)



Formas de onda III

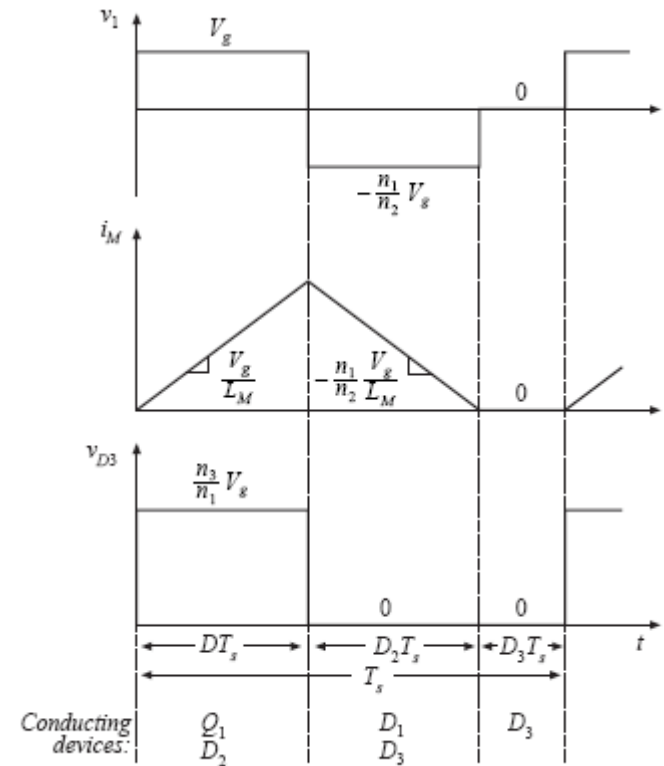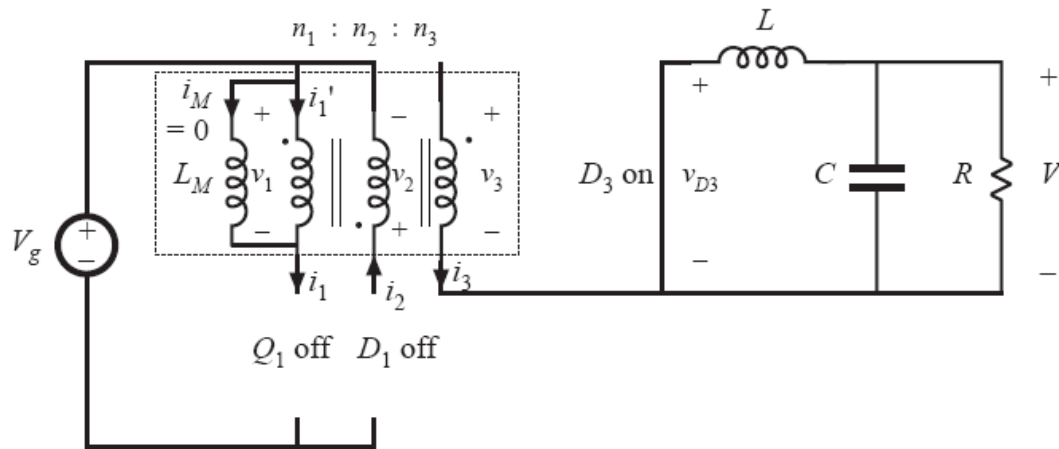




Convertidor directo (forward)

Balance v-s en magnetizante

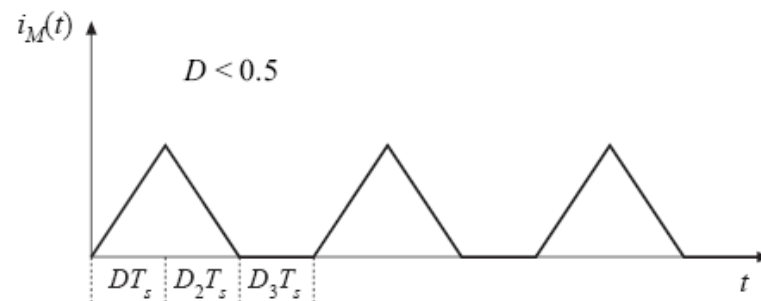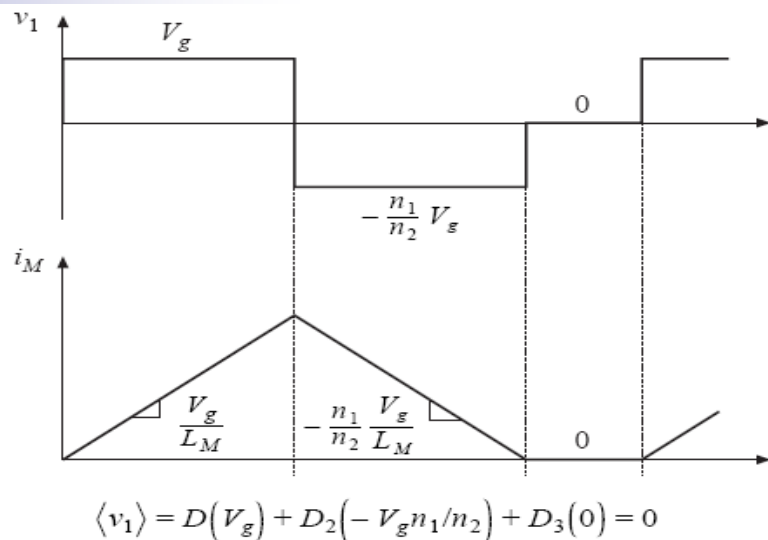


$D > 0.5$

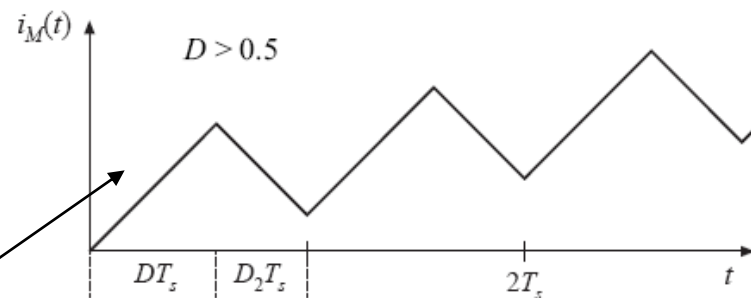



Convertidor directo (forward)

Relación de conversión

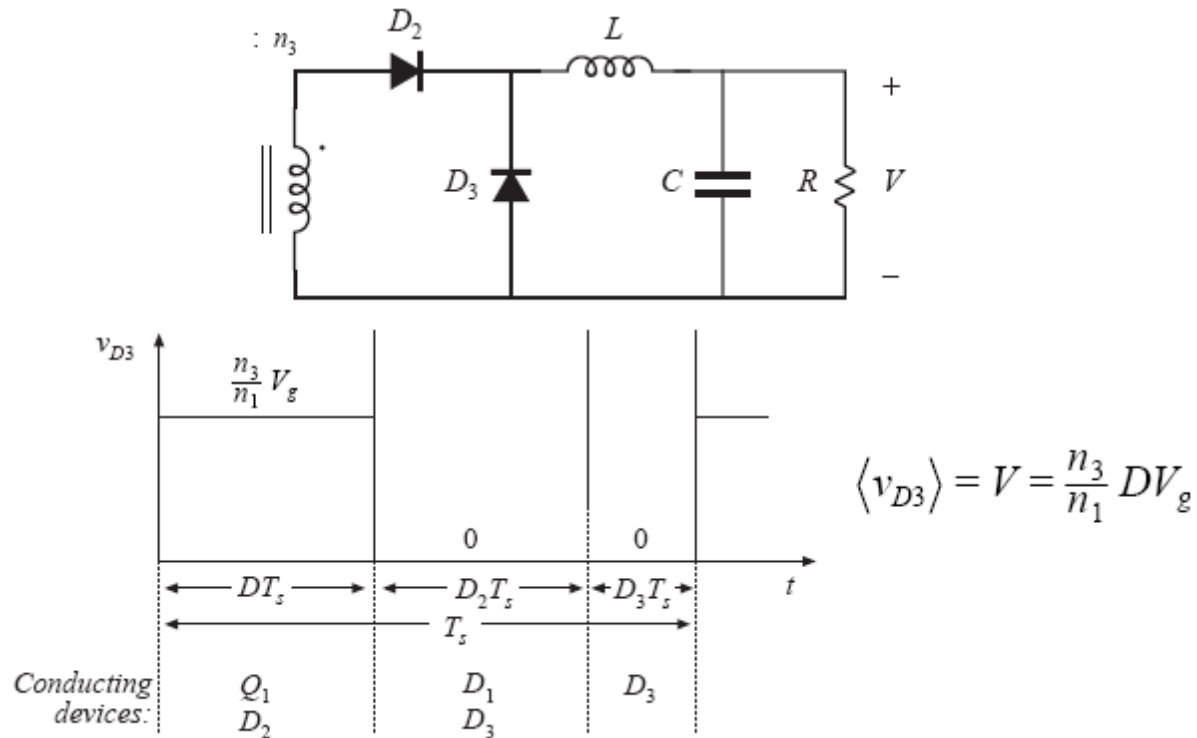



Convertidor directo (forward)

Relación entre máximo ciclo de trabajo y estrés en transistor

Maximum duty cycle limited to

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$

which can be increased by increasing the turns ratio n_2 / n_1 . But this increases the peak transistor voltage:

$$\max(v_{Q1}) = V_g \left(1 + \frac{n_1}{n_2} \right)$$


For $n_1 = n_2$

$$D \leq \frac{1}{2} \quad \text{and} \quad \max(v_{Q1}) = 2V_g$$




Convertidor directo de dos transistores

Relación de conversión

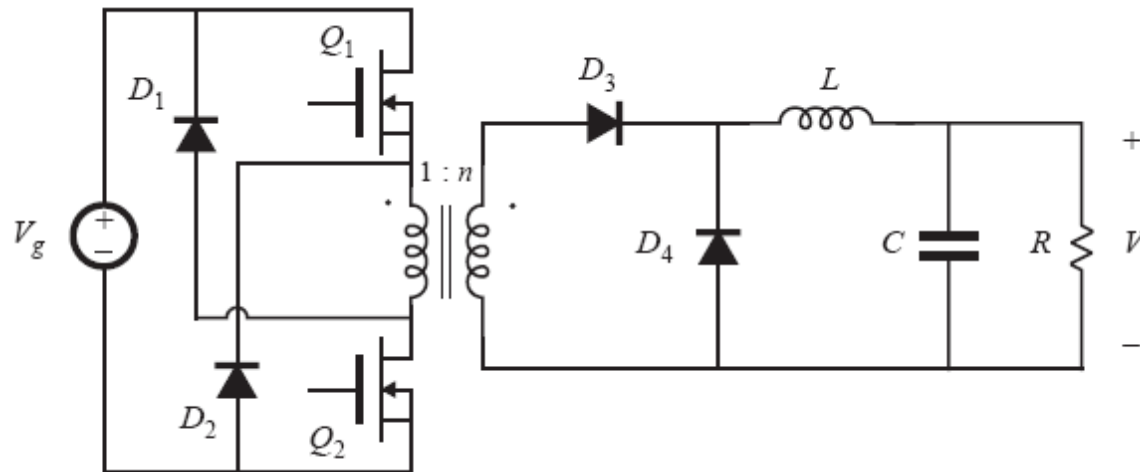


Convertidor Push-pull

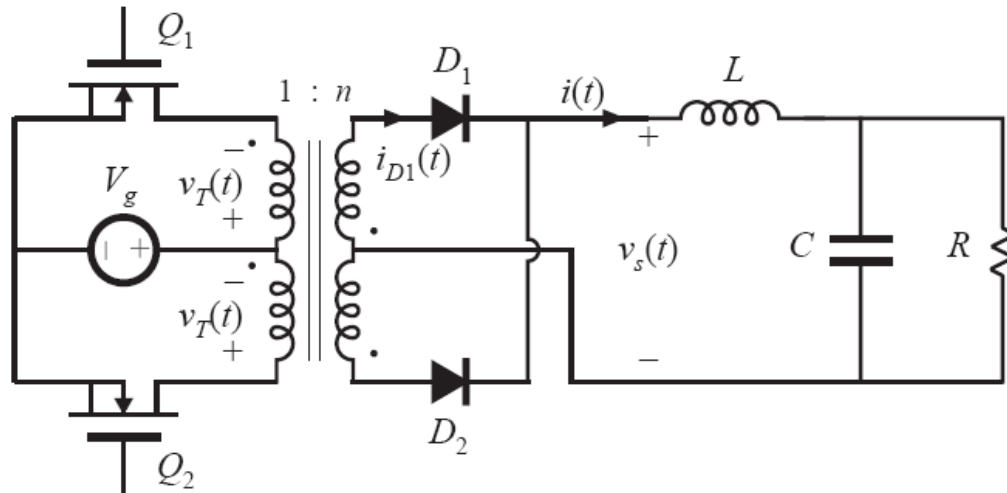

$$V = nDV_g$$


$$0 \leq D \leq 1$$

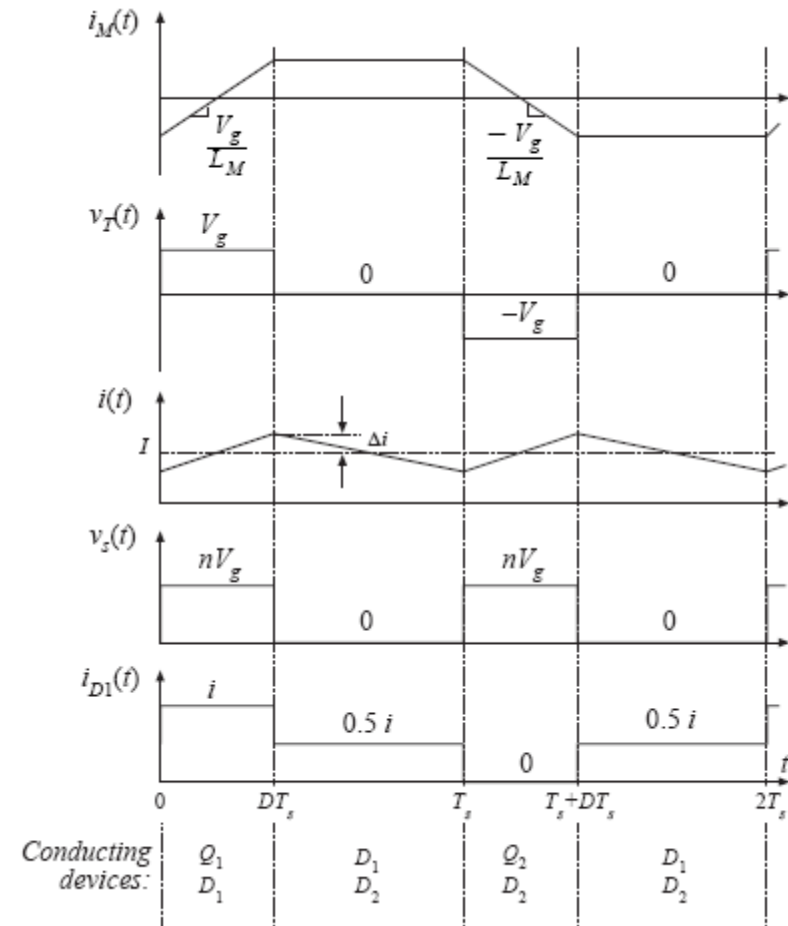



Convertidor Push-pull



Formas de onda

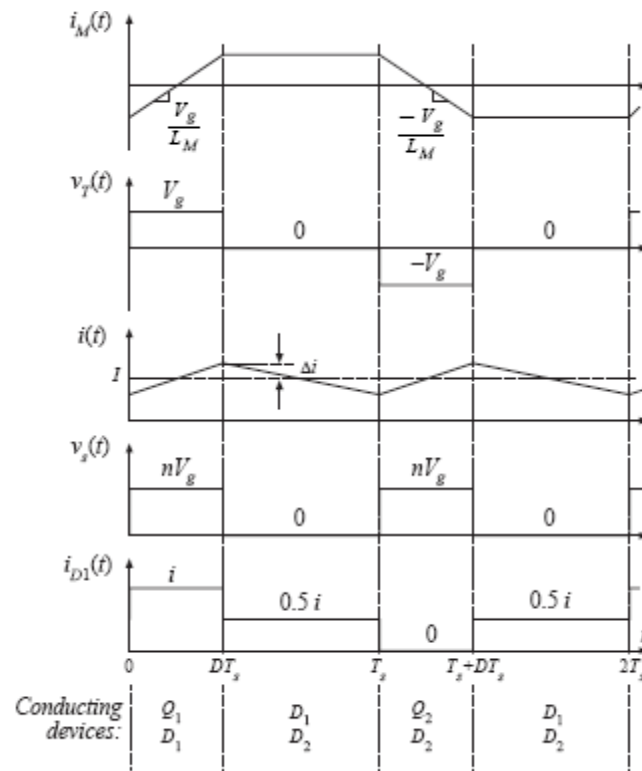



Convertidor Flyback



Derivación del flyback

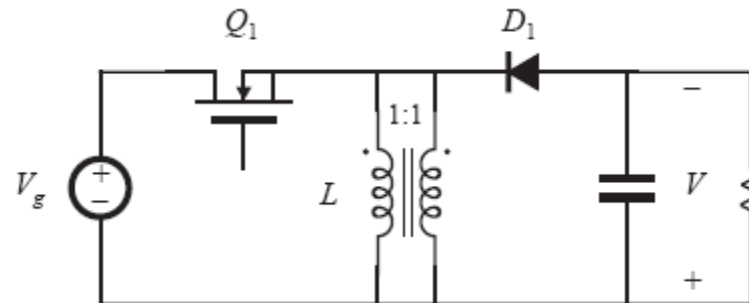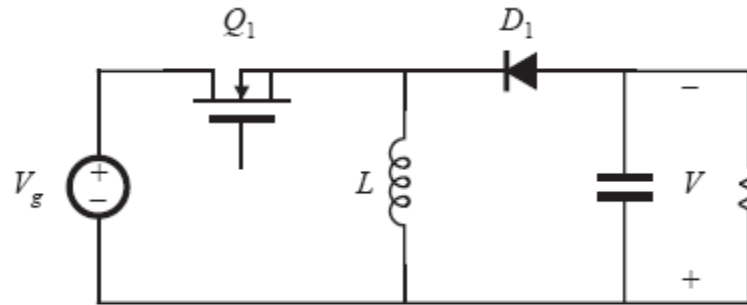




Convertidor Flyback

Derivación del flyback

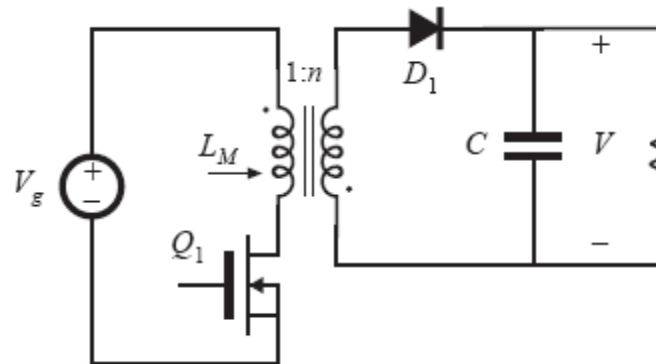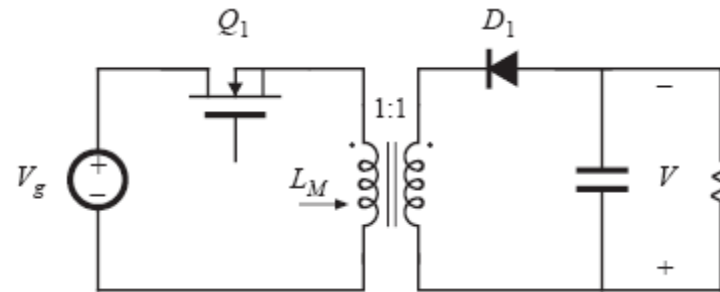

Convertidor Flyback

Transformador del flyback

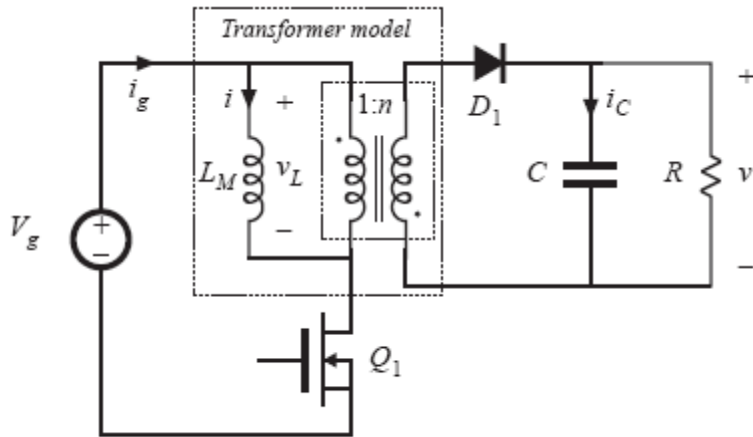



- A two-winding inductor
- Symbol is same as transformer, but function differs significantly from ideal transformer
- Energy is stored in magnetizing inductance
- Magnetizing inductance is relatively small

- Current does not simultaneously flow in primary and secondary windings
- Instantaneous winding voltages follow turns ratio
- Instantaneous (and rms) winding currents do not follow turns ratio
- Model as (small) magnetizing inductance in parallel with ideal transformer



Convertidor Flyback



Transformador del flyback

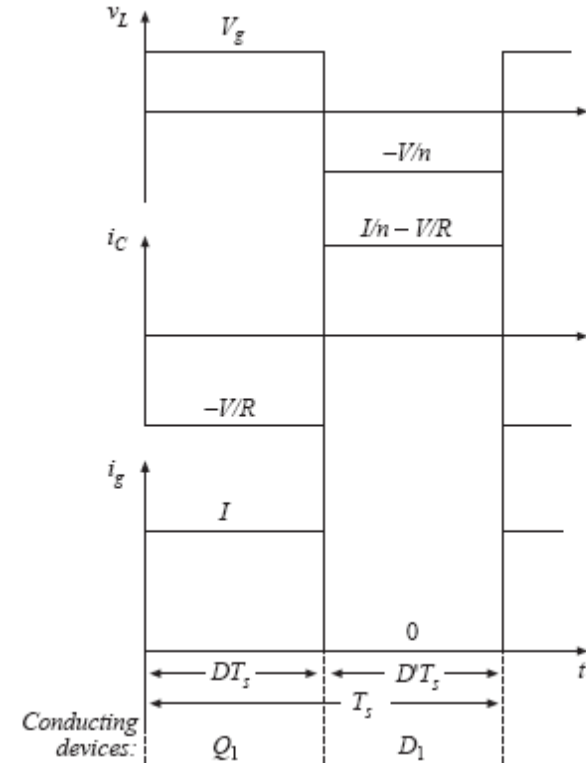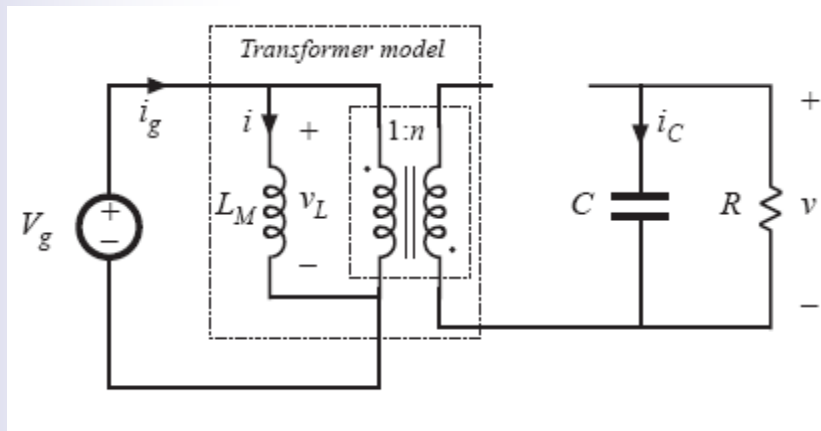



Convertidor Flyback

Transformador del flyback

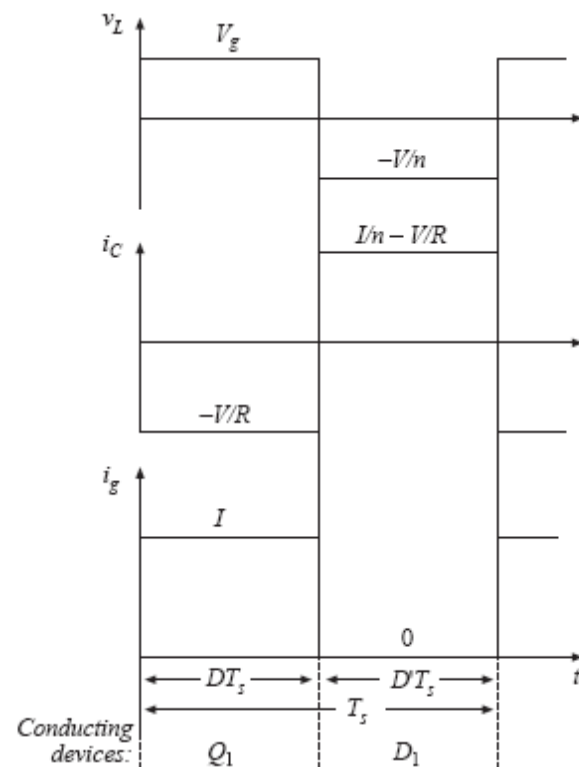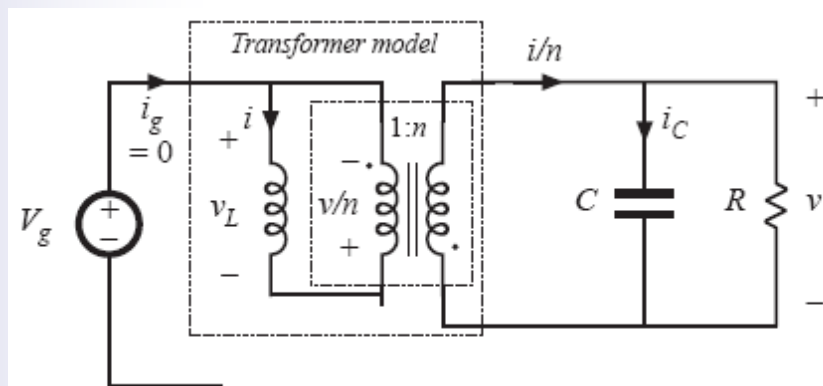

Características

- Widely used in low power and/or high voltage applications
- Low parts count
- Multiple outputs are easily obtained, with minimum additional parts
- Cross regulation is inferior to buck-derived isolated converters
- Often operated in discontinuous conduction mode
- DCM analysis: DCM buck-boost with turns ratio


- A wide variety of boost-derived isolated dc-dc converters can be derived, by inversion of source and load of buck-derived isolated converters:
 - full-bridge and half-bridge isolated boost converters
 - inverse of forward converter: the “reverse” converter
 - push-pull boost-derived converter

Of these, the full-bridge and push-pull boost-derived isolated converters are the most popular, and are briefly discussed here.




Puente completo derivado del boost

Características

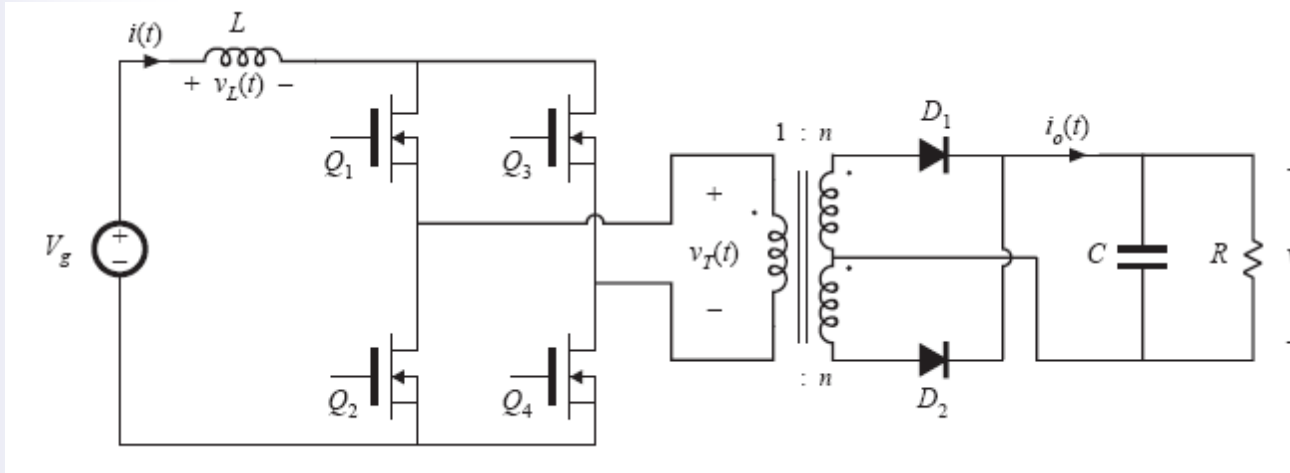

Puente completo derivado del boost

Reset del transformador

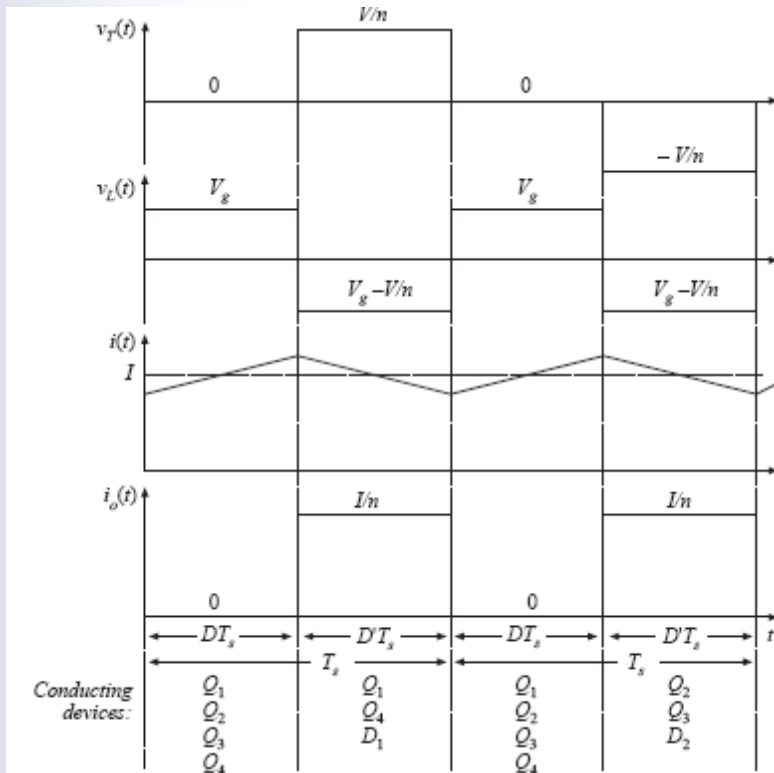


- As in full-bridge buck topology, transformer volt-second balance is obtained over two switching periods.
- During first switching period: transistors Q_1 and Q_4 conduct for time DT_s , applying volt-seconds VDT_s to secondary winding.
- During next switching period: transistors Q_2 and Q_3 conduct for time DT_s , applying volt-seconds $-VDT_s$ to secondary winding.



Puente completo derivado del boost

Relación de conversión

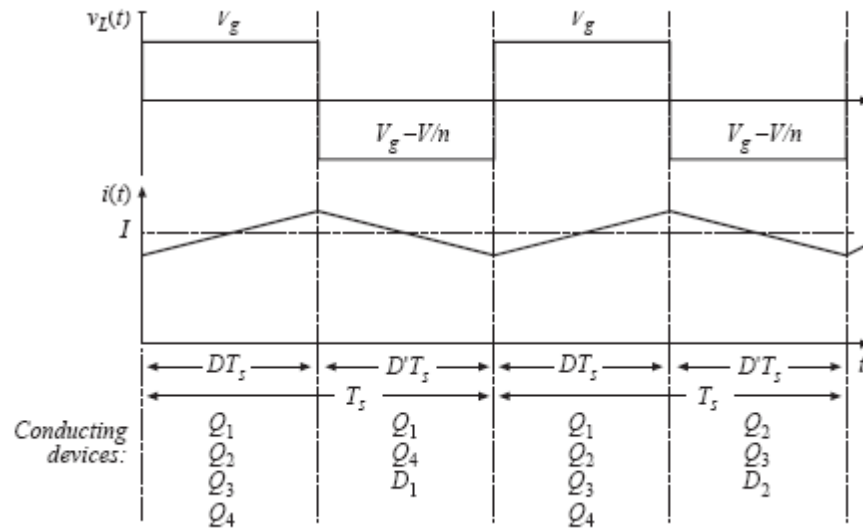

Application of volt-second balance to inductor voltage waveform:

$$\langle v_L \rangle = D(V_g) + D'(V_g - \frac{V}{n}) = 0$$

Solve for $M(D)$:

$$M(D) = \frac{V}{V_g} = \frac{n}{D'}$$

—boost with turns ratio n