



**CEI**UPM

Centro de  
Electrónica  
Industrial

[cei@upm.es](mailto:cei@upm.es)

# Reguladores de CA

**Monofásicos**

UNIVERSIDAD POLITÉCNICA DE MADRID



POLITÉCNICA


# Problema

## PROBLEMA 3. (2 puntos)


En el regulador de alterna de la figura, dibujar la tensión y la corriente en la carga para un ángulo de disparo  $\alpha=60^\circ$  en los siguientes casos:

a) Carga resistiva pura.

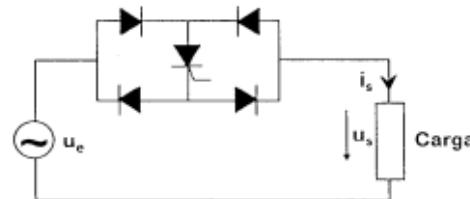b) Carga R-L siendo  $\text{arctg} \frac{\omega L}{R} = 30^\circ$




a)

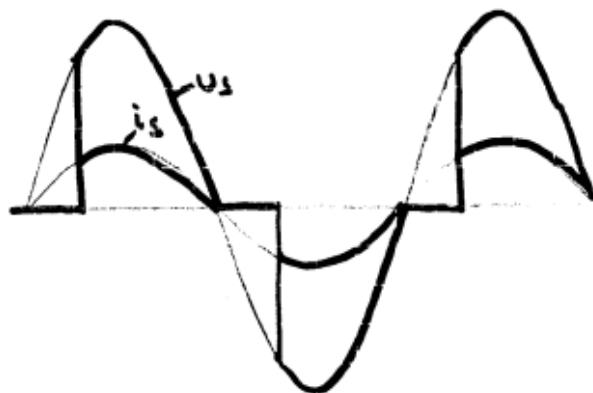

- b) Este regulador no se puede emplear con una carga inductiva ya que el tiristor no es capaz de bloquear la tensión directa cuando debe se cierre.

# Problema


**CUESTIÓN 2. (2 puntos)**

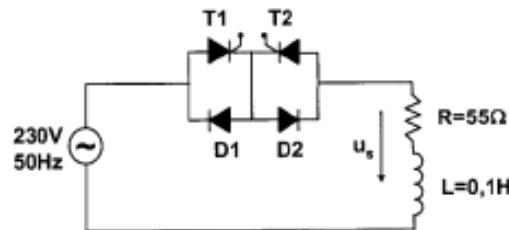

Los tiristores del regulador de la figura se disparan con un ángulo de retraso de  $60^\circ$  respecto al paso por cero de la tensión de red. Se pide:

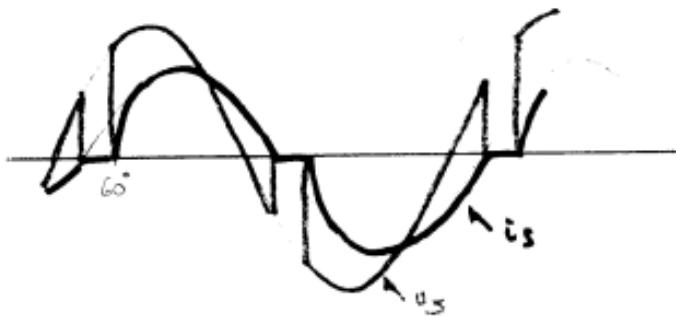- a) Dibujar la forma de onda de tensión y corriente en la carga.  
 b) Indicar la máxima tensión inversa y directa soportada por los tiristores.

$$\varphi = \arctg \frac{wL}{R} = 29'7^\circ \approx 30^\circ$$



$$U_{T, \text{DIR, MAX}} = E_p \cdot \sin 60^\circ = 231 \text{ V.}$$


$U_{i, INV, MAX} = 0$  you give there an idea in anticipate

# Problema
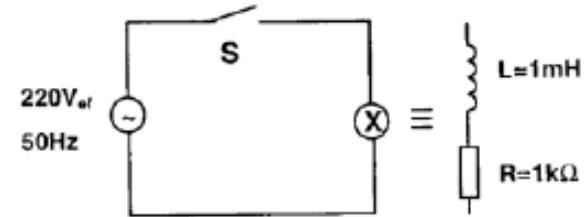
## CUESTION 4

El regulador de alterna de la figura alimenta una bombilla cuyo equivalente es una resistencia ( $R=1k\Omega$ ) en serie con una inductancia ( $L=1mH$ ). Se pide:

- Calcular el ángulo de retraso  $\alpha$  en el disparo del interruptor  $S$  para que la potencia entregada sea de 30W.
- Dibuje las formas de onda de tensión e intensidad en la carga.
- ¿Qué dispositivo utilizaría como interruptor?



# Problema

CUESTIÓN 4



Calculemos la constante de tiempo:

$$\tau = \frac{L}{R} = \frac{1\text{mH}}{1\text{k}\Omega} = 1\text{ms} \ll 10\text{ms}, \text{ que es el semiperíodo de la seni.}$$

Podemos asumir que el transitorio que se produce en cada conexión de S es despreciable en el tiempo.

$$P = \frac{U_{ef}^2}{R} = 30\text{W} \Rightarrow U_{ef} = 30 \cdot 1\text{k} = 30.000 \text{ V}^2$$

$$U_{ef} = 173.2$$

$$U_{ef}^2 = \frac{1}{\pi} \int_{\alpha}^{\pi} (220 \cdot \sqrt{2} \cdot \sin \omega t)^2 d\omega t$$


$$= \frac{220^2 \cdot 2}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d\omega t$$

$$= \frac{220^2}{\pi} \cdot \left[ (\pi - \alpha) + \frac{\sin 2\alpha - \sin 2\pi}{2} \right] = 30.000$$

$$(\pi - \alpha) + \frac{\sin 2\alpha}{2} = 1'947$$

$$\sin 2\alpha = -2'38 + 2\alpha \Rightarrow \underline{\alpha \approx 78'9^\circ}$$

gráficamente:

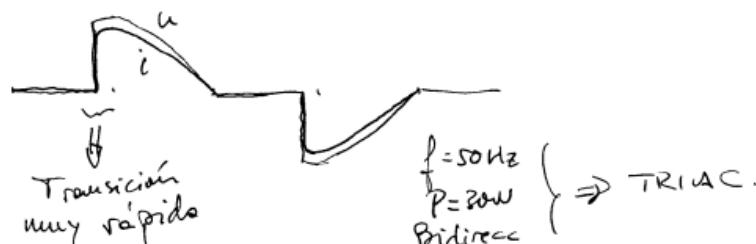



**CEI**UPM

Centro de  
Electrónica  
Industrial

[cei@upm.es](mailto:cei@upm.es)


# Cicloconvertidores

UNIVERSIDAD POLITÉCNICA DE MADRID



POLITÉCNICA

# AC to AC

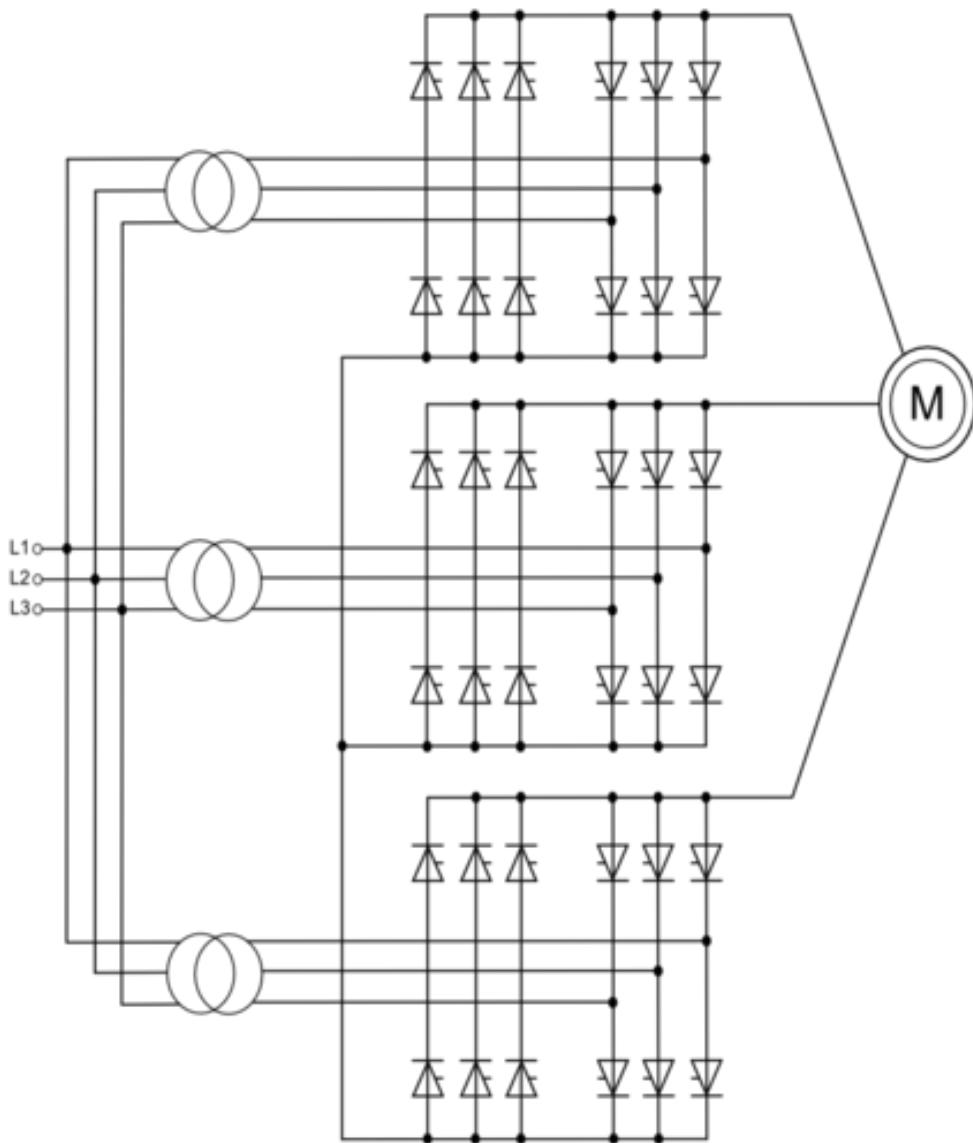

MW

- The AC output is SYNTHESIZED modulating a Rectifier
  - Similar to INVETERS, though the input is AC instead of DC....
  - And the frequencies are far smaller

# Cycloconverter

From Wikipedia, the free encyclopedia

For the rotating electrical machine, see [Rotary converter](#)

A **cycloconverter** (CCV) or a **cycloinverter** converts a constant voltage, constant frequency **AC waveform** to another AC waveform of a lower **frequency** by synthesizing the output waveform from segments of the AC supply without an intermediate DC link ([Dorf 1993](#), pp. 2241–2243 and [Lander 1993](#), p. 181). There are two main types of CCVs, circulating current type or blocking mode type, most commercial high power products being of the blocking mode type.<sup>[2]</sup>

## Contents [hide]

- 1 Characteristics
- 2 Applications
- 3 Harmonics
- 4 References


## Characteristics [edit]

Whereas phase-controlled SCR switching devices can be used throughout the range of CCVs, low cost, low-power **TRIAC**-based CCVs are inherently reserved for resistive load applications. The amplitude and frequency of converters' output voltage are both variable. The output to input frequency ratio of a three-phase CCV must be less than about one-third for circulating current mode CCVs or one-half for blocking mode CCVs. ([Lander 1993](#), p. 188)<sup>[3]</sup> Output waveform quality improves as the *pulse number* of switching-device bridges in phase-shifted configuration increases in CCV's input. In general, CCVs can be with 1-phase/1-phase, 3-phase/1-phase and 3-phase/3-phase input/output configurations, most applications however being 3-phase/3-phase.<sup>[1]</sup>
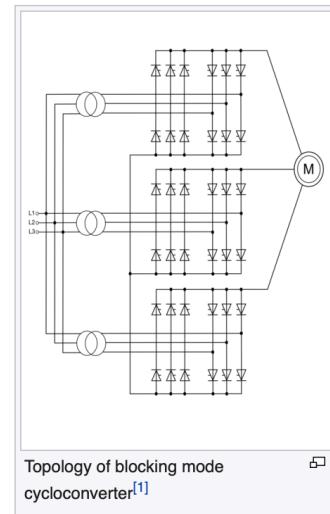
## Applications [edit]


The competitive power rating span of standardized CCVs ranges from few megawatts up to many tens of megawatts. CCVs are used for driving **mine hoists**, rolling mill main motors,<sup>[4]</sup> **ball mills** for ore processing, **cement kilns**, **ship propulsion** systems,<sup>[5]</sup> slip power recovery wound rotor induction motors (i.e., Scherbius drives) and aircraft 400 Hz power generation.<sup>[6]</sup> The variable-frequency output of a cycloconverter can be reduced essentially to zero. This means that very large motors can be started on full load at very slow revolutions, and brought gradually up to full speed. This is invaluable with, for example, **ball mills**, allowing starting with a full load rather than the alternative of having to start the mill with an empty barrel then progressively load it to full capacity. A fully loaded "hard start" for such equipment would essentially be applying full power to a stalled motor. Variable speed and reversing are essential to processes such as hot-rolling steel mills. Previously, SCR-controlled DC motors were used, needing regular brush/commutator servicing and delivering lower efficiency. Cycloconverter-driven synchronous motors need less maintenance and give greater reliability and efficiency. Single-phase bridge CCVs have also been used extensively in **electric traction** applications to for example produce 25 Hz power in the U.S. and 16 2/3 Hz power in Europe.<sup>[7][8]</sup>

Whereas phase-controlled converters including CCVs are gradually being replaced by faster **PWM** self-controlled converters based on IGBT, GTO, IGCT and other switching devices, these older classical converters are still used at the higher end of the power rating range of these applications.<sup>[3]</sup>




Topology of blocking mode cycloconverter<sup>[1]</sup>

B.K. Bose

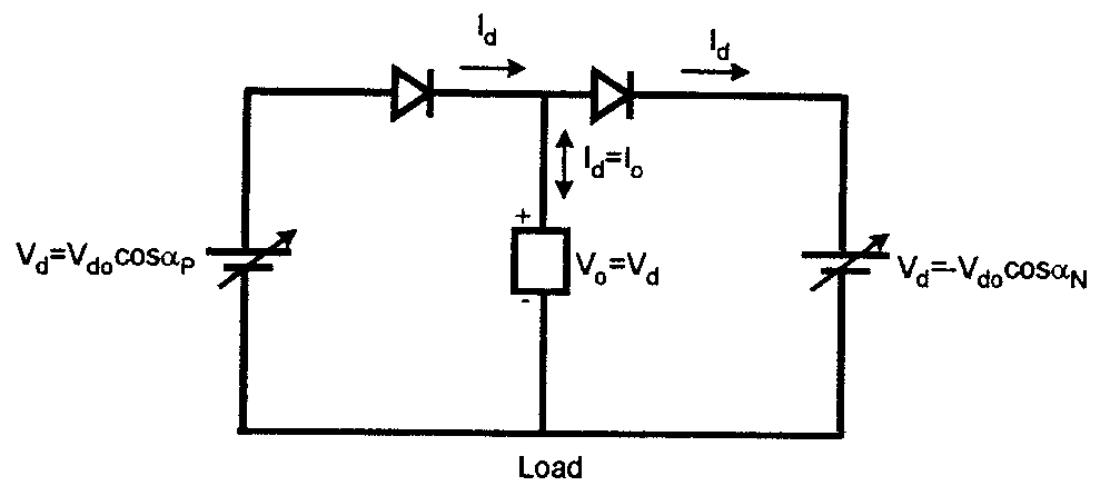

**Figure 4.8** Thevenin-equivalent circuit of dual converter

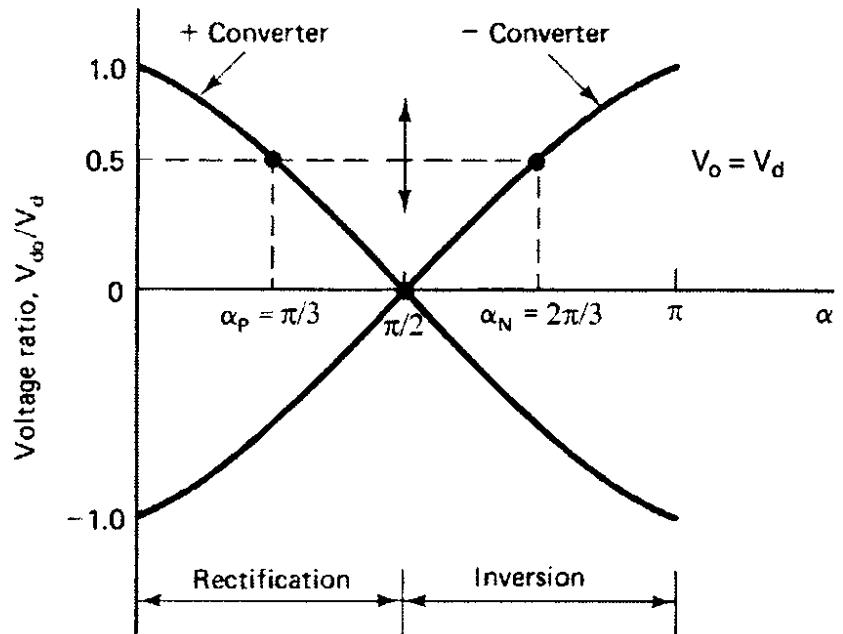


**Figure 4.9** Voltage-tracking control in dual converter showing firing angle relations
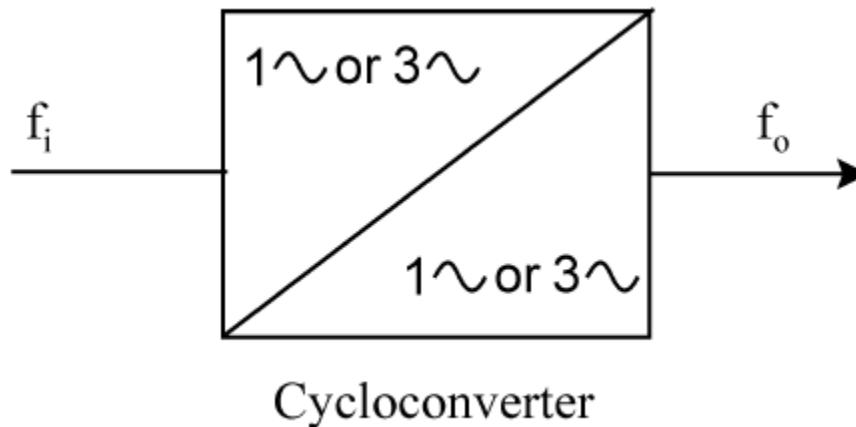
# CYCLOCONVERTERS

Burak Ozpineci, Leon M. Tolbert  
Department of Electrical and Computer Engineering  
University of Tennessee-Knoxville  
Knoxville, TN 37996-2100


# Introduction





Some applications of cycloconverters are:

- Cement mill drives
  - Ship propulsion drives
  - Rolling mill drives
  - Scherbius drives
  - Ore grinding mills
  - Mine winders


# Concept

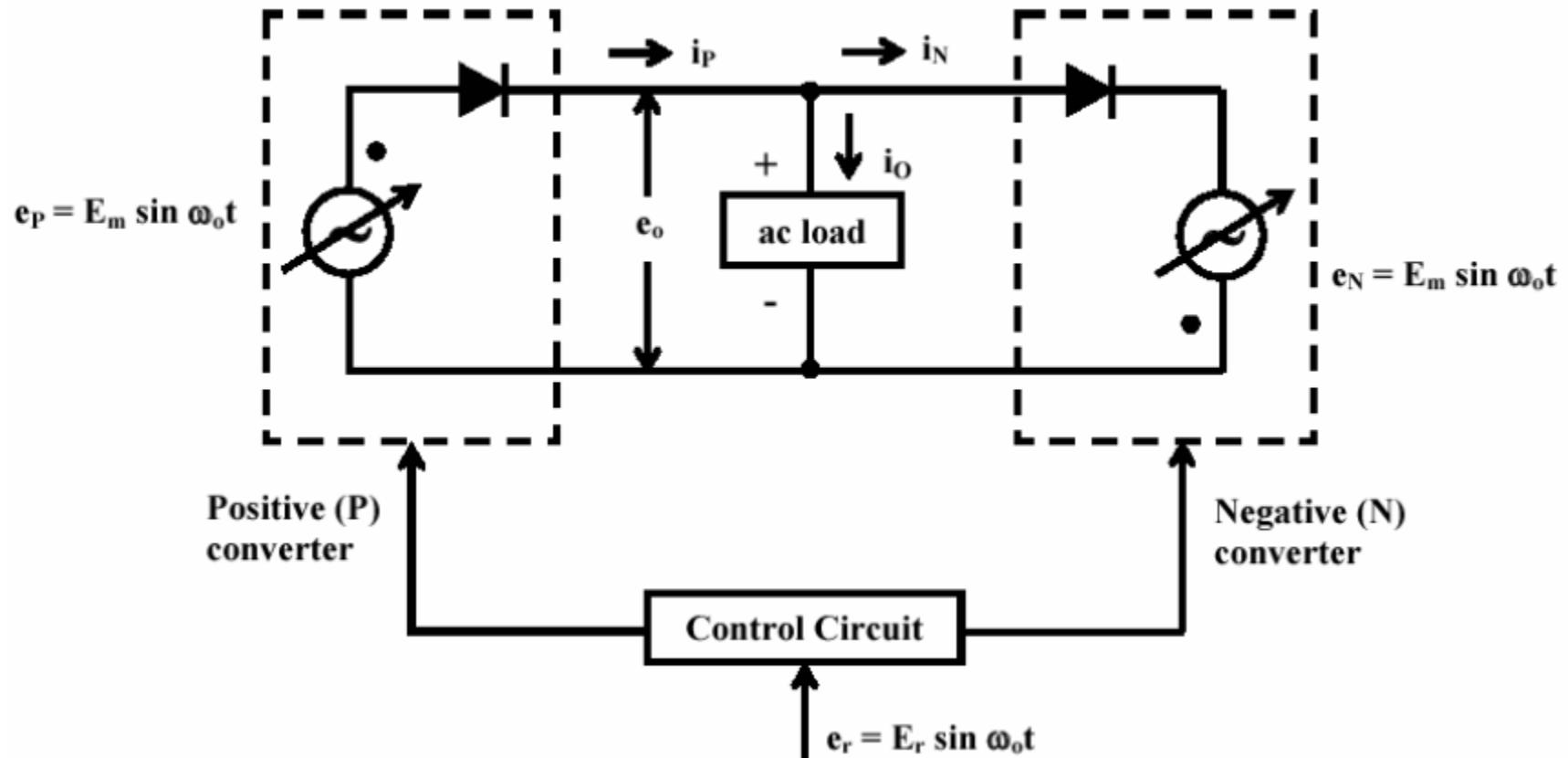

# Concept

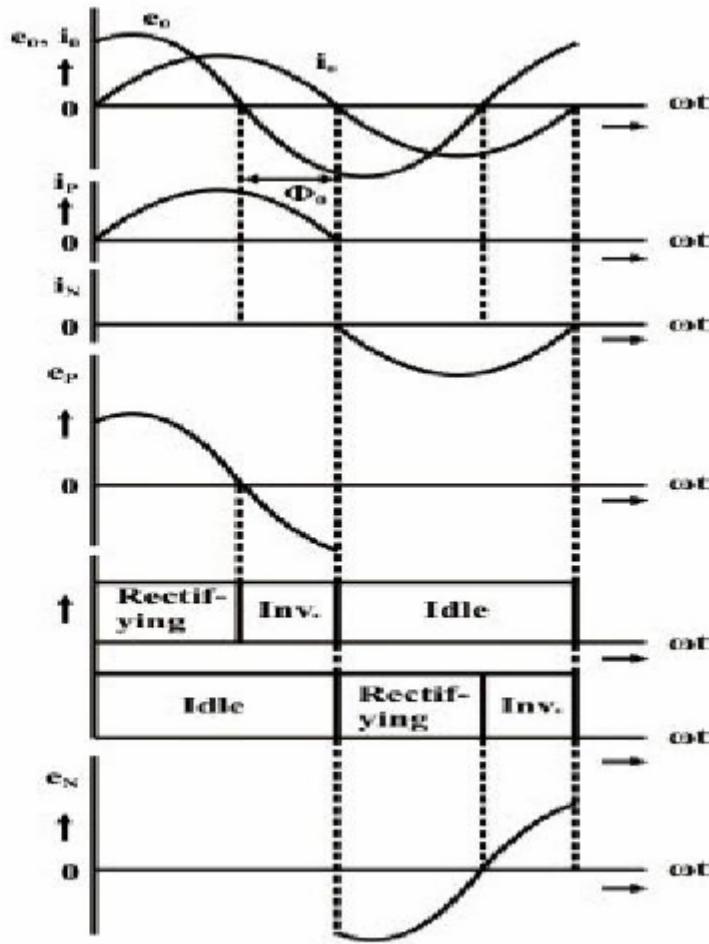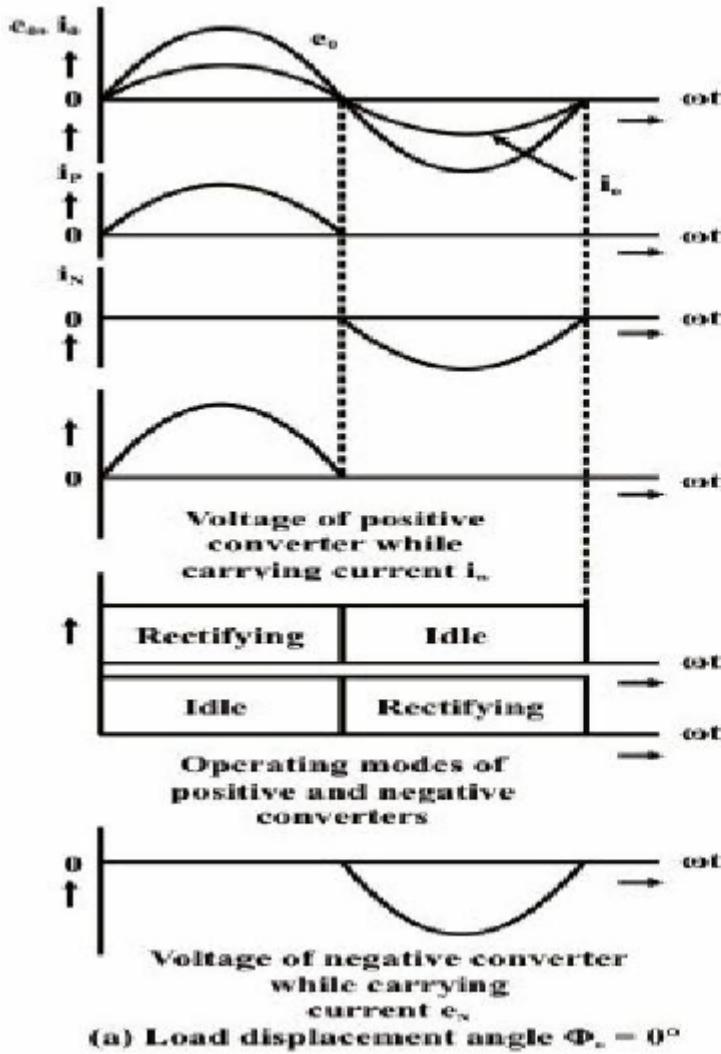


# Concept: 1 phase – 1 phase

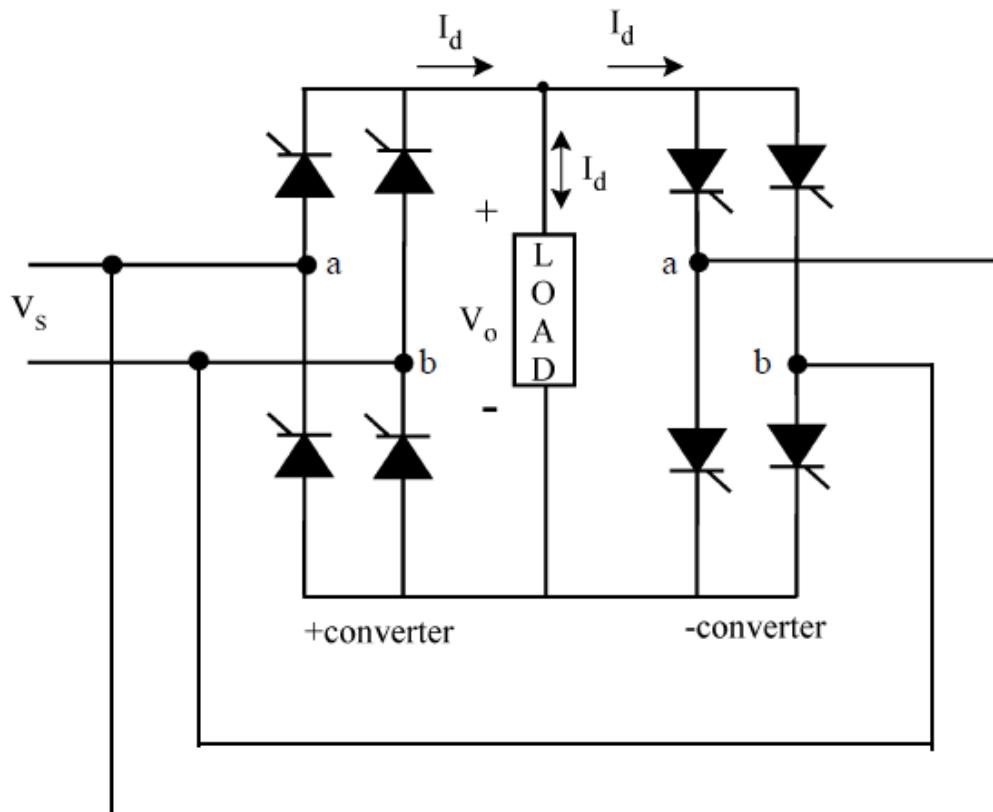

**Fig. 2** Single-phase to single-phase cycloconverter


# Concept

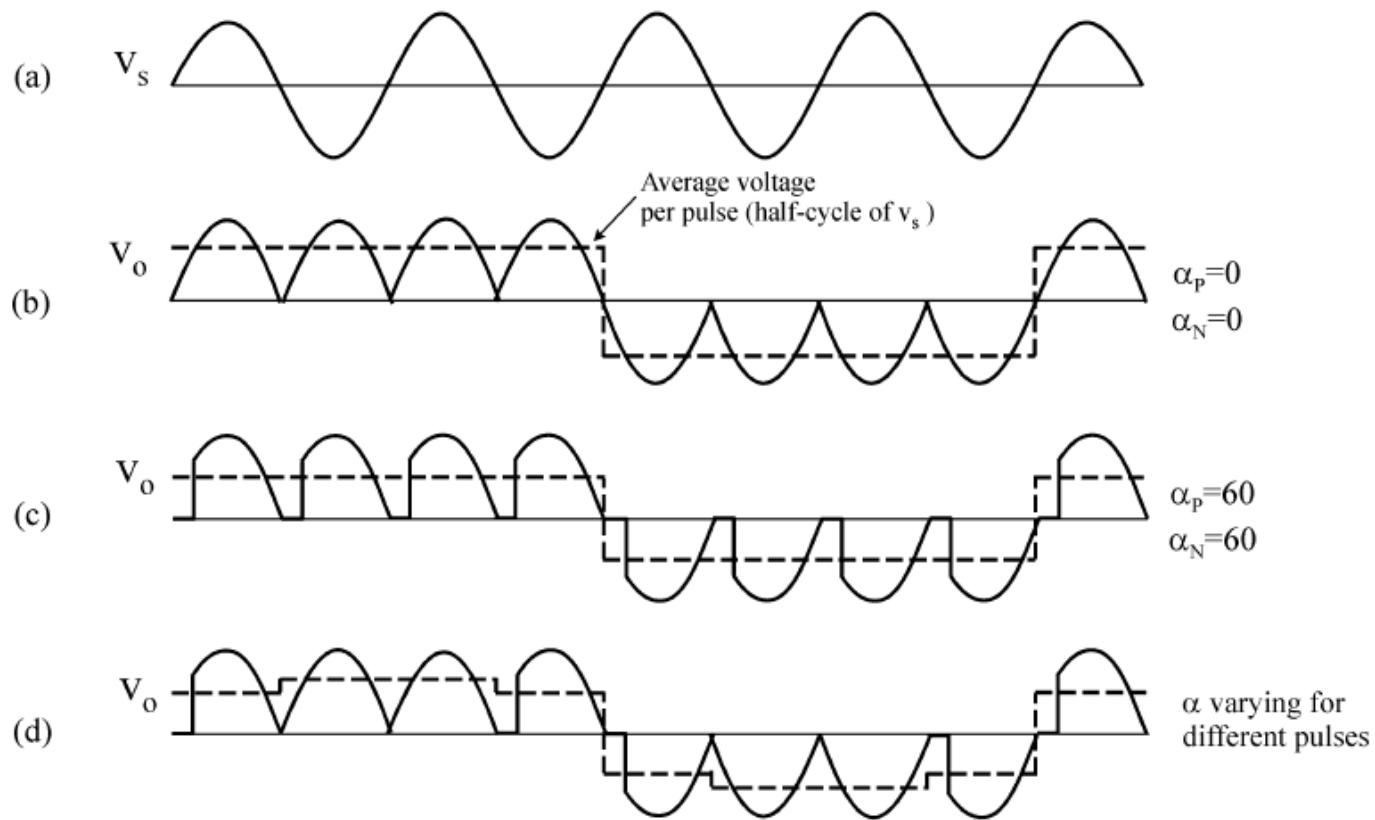

**Fig. 3** Single-phase to single-phase cycloconverter waveforms


- a) input voltage
  - b) output voltage for zero firing angle
  - c) output voltage with firing angle  $\pi/3$  rad.
  - d) output voltage with varying firing angle

# 3-phase 1-phase

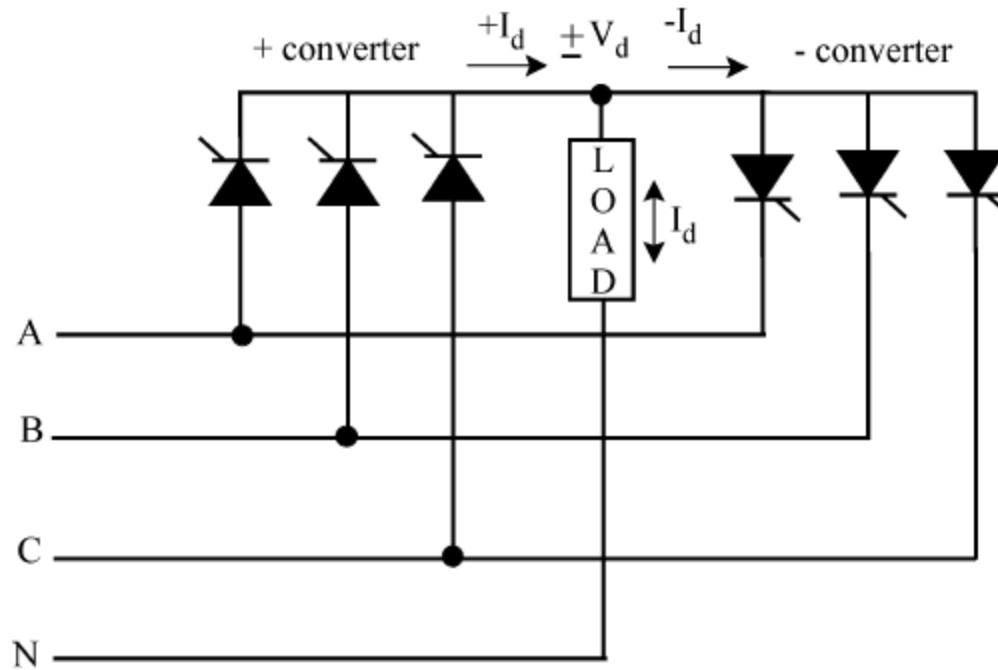


**Fig. 4** 3φ-1φ half-wave cycloconverter

# 3-phase 1-phase

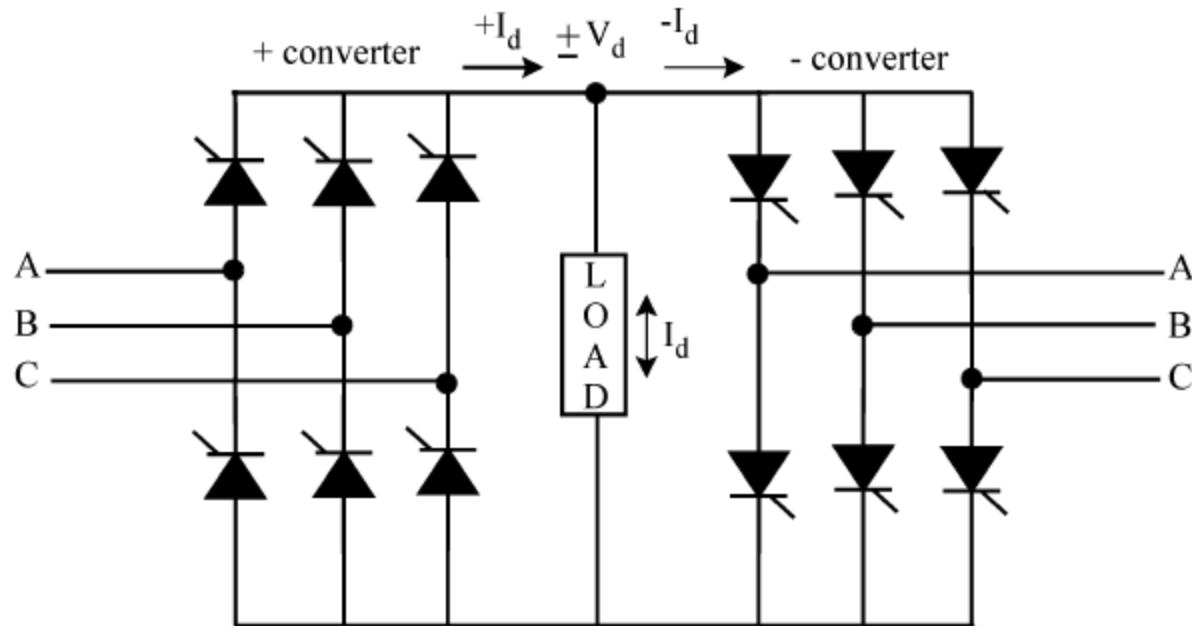


**Fig. 5** 3 $\phi$ -1 $\phi$  bridge cycloconverter

# 3-phase 1-phase

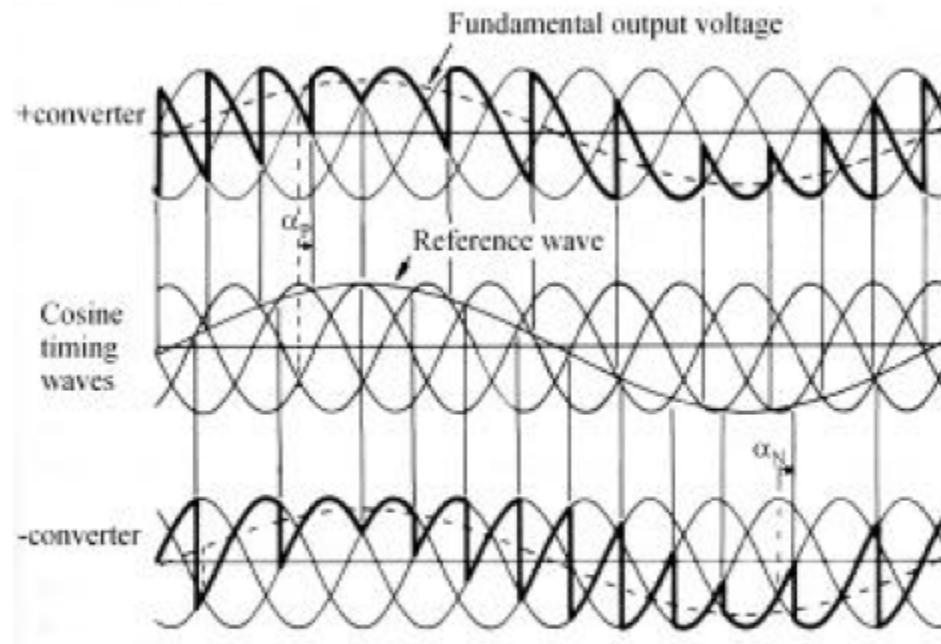


**Fig. 6** 3 $\phi$ -1 $\phi$  half-wave cycloconverter waveforms  
 a) + converter output voltage  
 b) cosine timing waves  
 c) - converter output voltage

# 3-phase – 3-phase

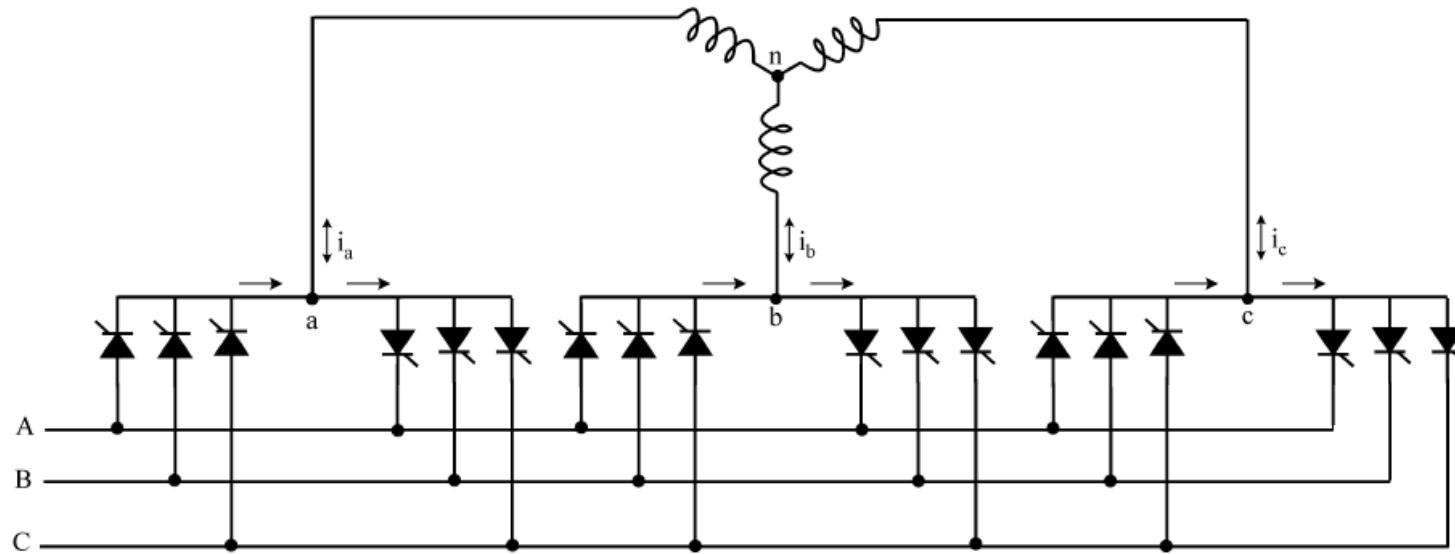


**Fig. 7** 3φ-3φ half-wave cycloconverter

# 3-phase – 3-phase

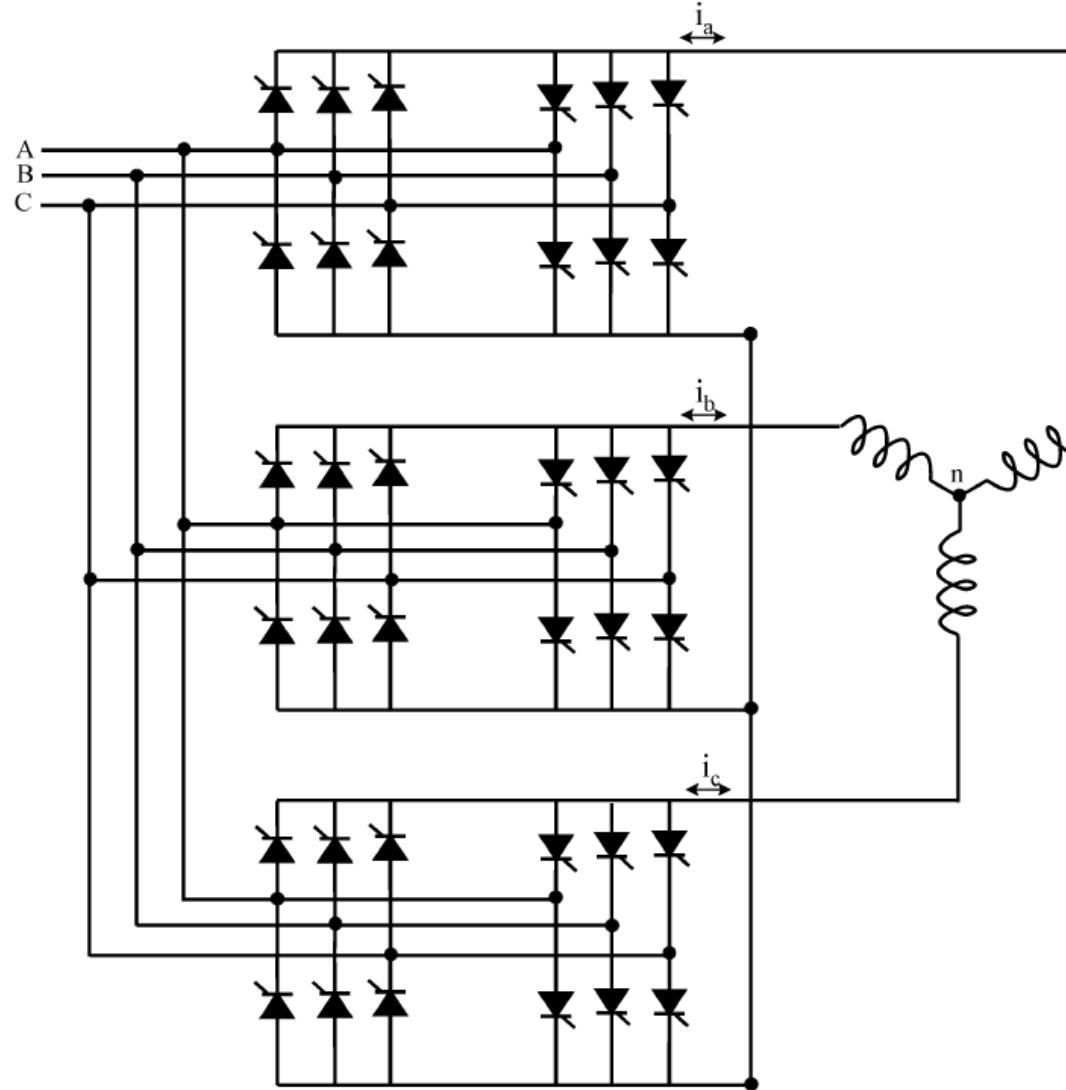


**Fig. 8** 3φ-3φ bridge cycloconverter

# Intergroup Reactor

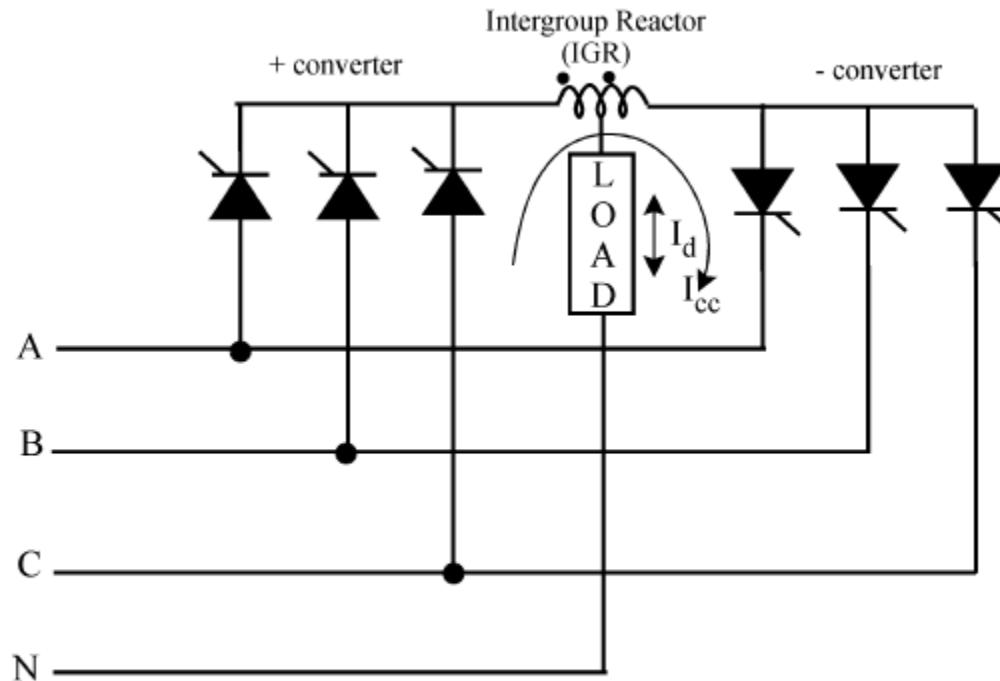

**Fig. 9** Circulating current and IGR

## Matrix converters

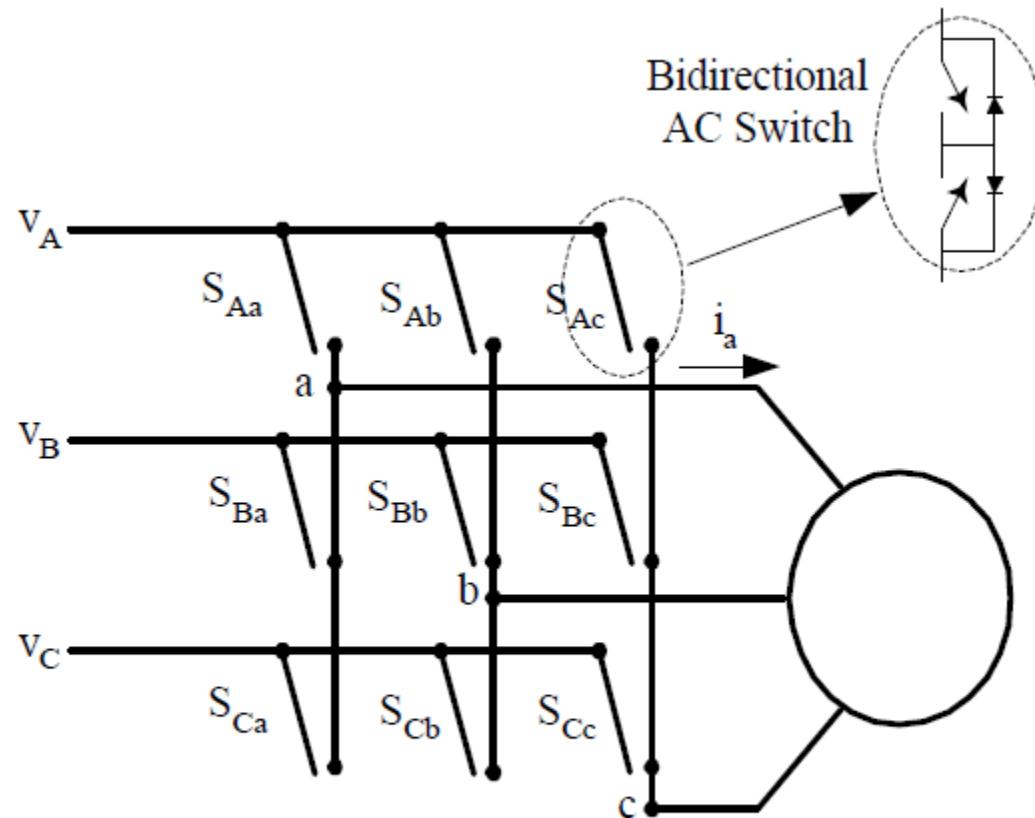

**Fig. 12** Matrix converter