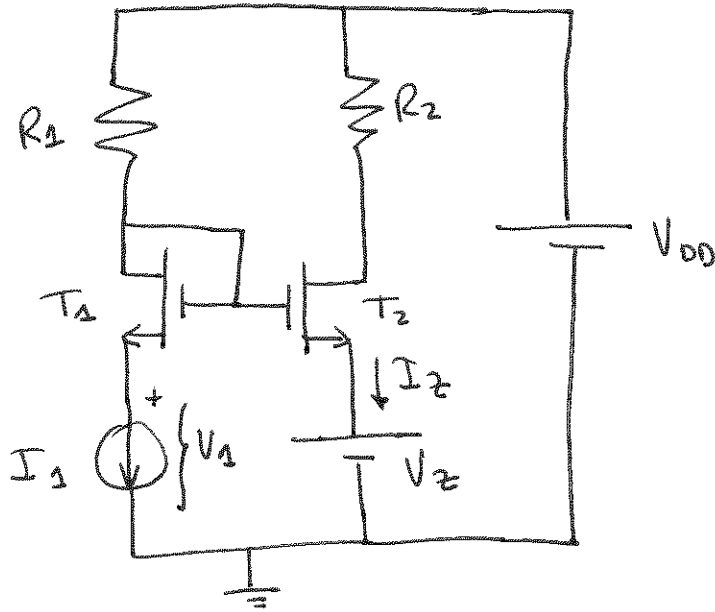


a) DC



Suponemos:

T_1 en saturación

T_2 en saturación

Zener en ruptura

$$I_{DS1} = \frac{K}{2} \frac{W}{L} (V_{GS1} - V_{TH})^2 = I_1 = 8 \text{ mA} \rightarrow V_{GS1} = 5 \text{ V}$$

MALLA GS1 $\rightarrow V_{DD} = R_1 \cdot I_1 + V_{GS1} + V_1 \rightarrow V_1 = 4 \text{ V}$

MALLA GS2 $\rightarrow V_{DD} = R_1 \cdot I_1 + V_{GS2} + V_2 \rightarrow V_{GS2} = 3.4 \text{ V}$

$$I_2 = I_{DS2} = \frac{K}{2} \frac{W}{L} (V_{GS2} - V_{TH})^2 = 2.88 \text{ mA} \rightarrow I_2 > 0 \quad \underline{\underline{OK}}$$

MALLA DS1 $\rightarrow V_{DD} = R_1 I_1 + V_{DS1} + V_1 \rightarrow V_{DS1} = 5 \text{ V} > V_{GS1} - V_{TH} \quad \underline{\underline{OK}}$

MALLA DS2 $\rightarrow V_{DD} = R_2 I_{DS2} + V_{DS2} + V_2 \rightarrow V_{DS2} = 6.52 \text{ V} > V_{GS2} - V_{TH} \quad \underline{\underline{OK}}$


b) $I_2 = 2.88 \text{ mA}$ $\left\{ \begin{array}{l} > I_{Z, \text{min}} = 2.5 \text{ mA} \quad \underline{\underline{OK}} \\ P_2 = 2.88 \text{ mA} \cdot 5.6 \text{ V} = 16.1 \text{ mW} < 50 \text{ mW} = P_{Z, \text{max}} \quad \underline{\underline{OK}} \end{array} \right.$

c) AC

Garancia máxima $\Rightarrow R_S = 0, R_L = \infty$

$$g_m = \sqrt{2K \frac{W}{L} I_{DQ}}$$
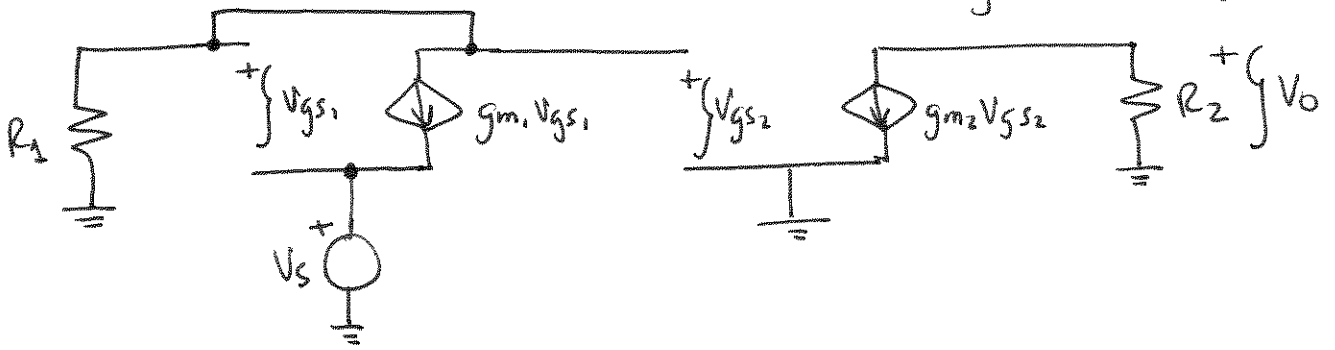
$$g_{m1} = 4 \text{ mA/V}^2 \quad g_{m2} = 2^4 \text{ mA/V}^2$$




$$V_o = -g_{m2} V_{gs2} R_2 \quad \leftarrow +g_{m2} R_2 \cdot g_{m1} R_1 V_{gs1}$$

$$g_{m1} V_{gs1} R_1 + V_{gs2} = 0$$

$$g_{m1} V_{gs1} R_1 + V_{gs1} + V_s = 0 \rightarrow V_s = -(g_{m1} R_1 + 1) V_{gs1}$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{g_{m2} R_2 g_{m1} R_1}{g_{m1} R_1 + 1} = -1.8$$

d)

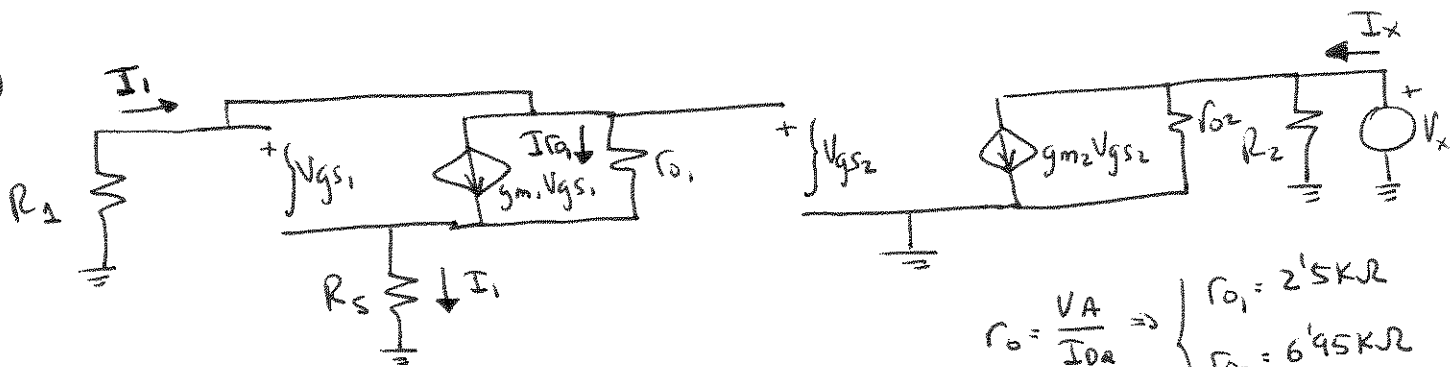

$$r_o = \frac{V_A}{I_{DQ}} \Rightarrow \begin{cases} r_{o1} = 2.5 \text{ k}\Omega \\ r_{o2} = 6.95 \text{ k}\Omega \end{cases}$$


$$I_{r_{o1}} = \frac{V_{gs1}}{r_{o1}} \Rightarrow I_1 = g_{m1} V_{gs1} + \frac{V_{gs1}}{r_{o1}} = \left(g_{m1} + \frac{1}{r_{o1}} \right) V_{gs1}$$

$$\rightarrow R_1 \cdot I_1 + V_{gs1} + R_S I_1 = 0 \rightarrow \left[(R_1 + R_S) \left(g_{m1} + \frac{1}{r_{o1}} \right) + 1 \right] V_{gs1} = 0 \rightarrow$$

$$\rightarrow V_{gs1} = 0 \rightarrow V_{gs2} = -I_1 R_1 = -R_1 \cdot \left(g_{m1} + \frac{1}{r_{o1}} \right) V_{gs1} = 0 \rightarrow$$

$$\rightarrow I_x = \frac{V_x}{R_2} + \frac{V_x}{r_{o2}} \rightarrow R_{out} = \frac{V_x}{I_x} = \left(\frac{1}{R_2} + \frac{1}{r_{o2}} \right)^{-1} = 874.1 \Omega$$

e) DC

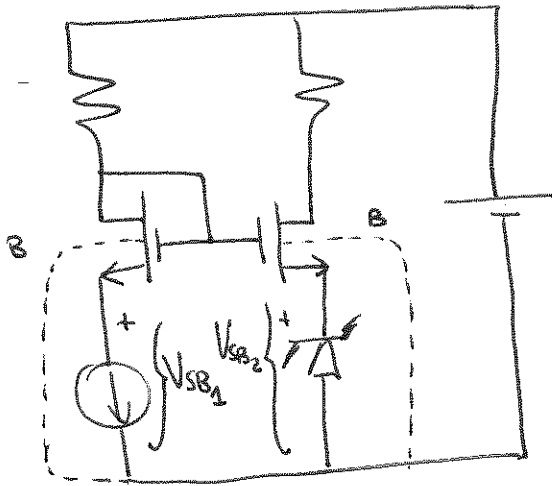


$$V_{SB1} = V_{\Omega} = 4V$$

$$V_{SB2} = V_{\Xi} = 5.6V$$

$V_{TH} \uparrow$ si $V_{SB} \uparrow$

$V_{TH2} > V_{TH1}$

AC

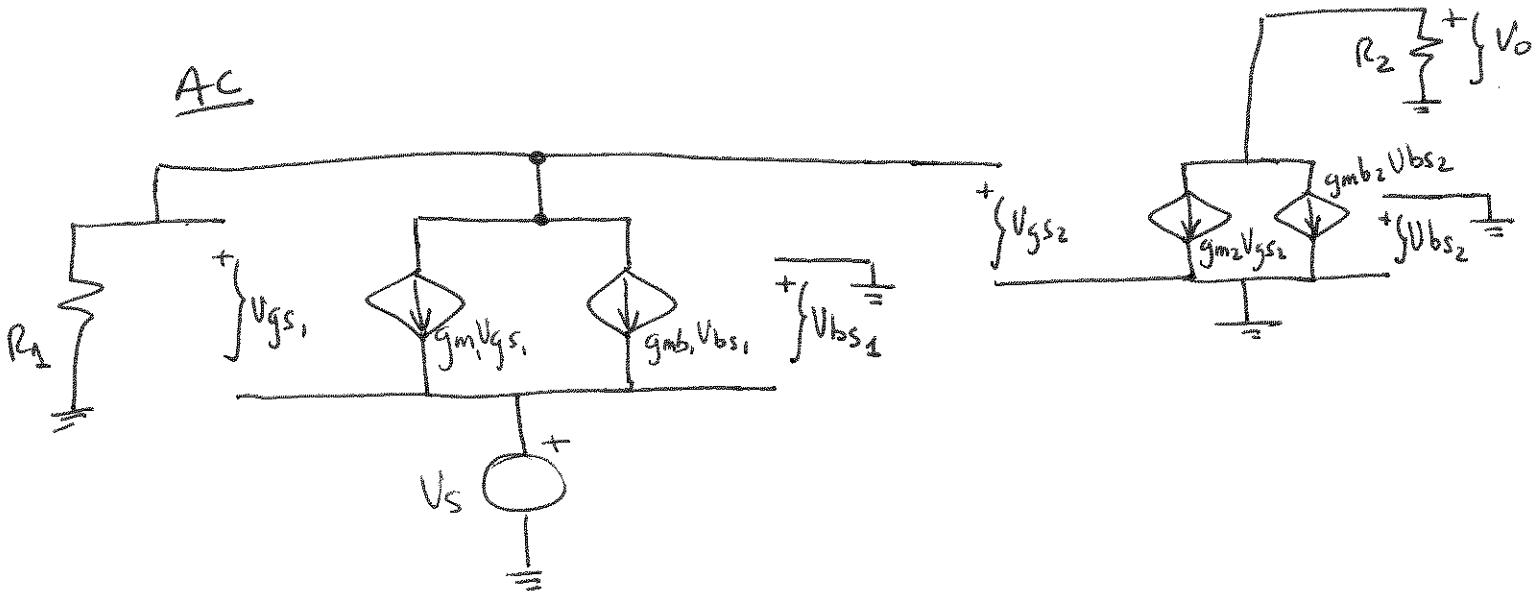

$V_{bs2} = 0 \rightarrow$ No le afecta el efecto body a T_2
 $V_{bs1} = -V_s \rightarrow$ Si le afecta el efecto body a T_1