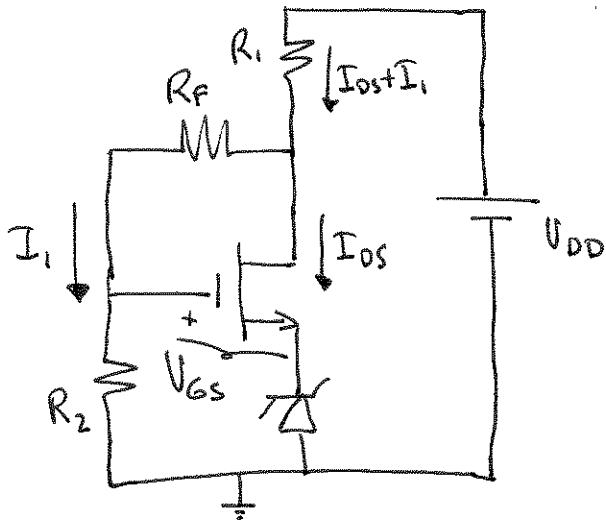


Solución Ejercicio Refuerzo MOS 4

a) Circuito en DC



Supongo Zener en ruptura:

$$\text{Zener} \equiv \frac{1}{T} |V_z|$$

Supongo NMOS en saturación:

$$I_{DS} = \frac{k}{2} \frac{W}{L} (V_{GS} - V_T)^2 \quad \text{①}$$

$$V_{DS} > V_{GS} - V_T$$

$$V_{GS} > V_T$$

MDLA G-S $V_{DD} = (I_1 + I_{DS}) R_1 + I_1 R_F + V_{GS} + V_z$

$$I_1 R_2 = V_{GS} + V_z \quad \rightarrow \quad V_{DD} = \left(\frac{V_{GS} + V_z}{R_2} + I_{DS} \right) R_1 + \frac{V_{GS} + V_z}{R_2} R_F + V_{GS} + V_z \rightarrow$$

$$\rightarrow 18 = \frac{5}{3} V_{GS} + I_{DS} \quad \left\{ \begin{array}{l} 0.4 V_{GS}^2 + \frac{13}{15} V_{GS} - 17.6 = 0 \end{array} \right.$$

$$\text{①} \rightarrow I_{DS} = 0.4 (V_{GS} - 1)^2$$


$$\Rightarrow V_{GS} = \begin{cases} 5.64 \text{ V} & \rightarrow I_{DS} = 8.6 \text{ mA} \\ -7.8 < V_T & \times \end{cases} \quad I_1 = \frac{V_{GS} + V_z}{R_2} = 3.08 \text{ mA}$$

MDLA D-S $V_{DD} = (I_{DS} + I_1) R_1 + V_{DS} + V_z$

$$\rightarrow V_{DS} = 8.72 \text{ V} > V_{GS} - V_T \quad \text{OK SATURACIÓN}$$

$$b) \quad I_z = I_{DS} = 8.6 \text{ mA} \quad \left\{ \begin{array}{l} > I_{z, \min} = 4 \text{ mA} \\ < I_{z, \max} = \frac{P_{\max}}{|V_z|} = 27.8 \text{ mA} \end{array} \right. \quad \underline{\underline{\text{OK}}}$$

c)

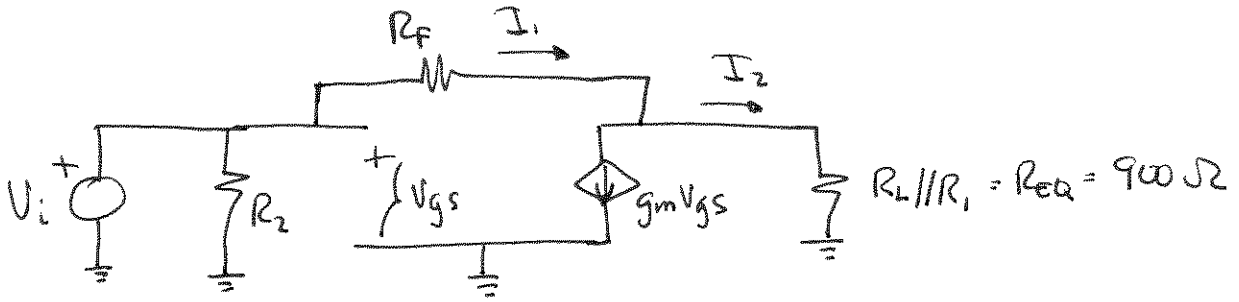

d) $V_{gs} = V_i$

$$I_1 = g_m V_{gs} + I_2 \rightarrow \frac{V_i - V_o}{R_F} = g_m V_i + \frac{V_o}{R_{EQ}} \rightarrow$$

$$\rightarrow V_i \left(\frac{1}{R_F} - g_m \right) = V_o \left(\frac{1}{R_F} + \frac{1}{R_{EQ}} \right) \rightarrow$$

$$\rightarrow \frac{V_o}{V_i} = \frac{\frac{1}{R_F} - g_m}{\frac{1}{R_F} + \frac{1}{R_{EQ}}} = \frac{1 - g_m R_F}{1 + \frac{R_F}{R_{EQ}}} = -1.28$$

$$g_m = \sqrt{2K \frac{W}{L} I_{D5}} = 3.71 \text{ mA/V}$$