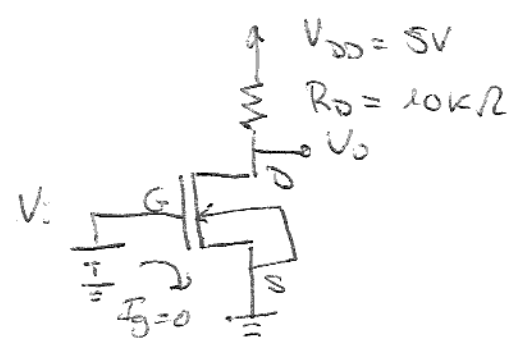


Ejercicios MOSFET.



$$V_G = 5V$$

$$V_T = 1V$$

$$\frac{W}{L} = 2$$

$$K = 20 \cdot 10^{-6} \frac{A}{V^2}$$

$$V_{GS}$$

$$V_{DS}$$

$$I_{DS}$$

Al tener el NMOS un condensador en la puerta la corriente $I_G = 0$ (C.C.)

* Hallar Puerta-Fuente

$$V_G = V_{GS} = 5V > 1V = V_T \rightarrow \text{No estar en corte.}$$

* Hallar Drenador-Fuente

$$V_{DD} = I_{DS} \cdot R_D + V_{DS}$$

* Suponemos saturación ($V_{DS} \geq V_{GS} - V_T$)

$$I_{DS} = \frac{K}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{20 \cdot 10^{-6} A}{2} \cdot 2 \cdot (5 - 1)^2 = 0.32 mA$$

$$V_{DS} = V_{DD} - I_{DS} \cdot R_D = 1.8V$$

$$V_{DS} = 5V - 0.32mA \cdot 10k\Omega$$

$$V_{GS} - V_T > V_{DS}$$

$$5 - 1 > 1.8 \rightarrow \text{TRIODO}$$


* Suponemos Triodo.

$$I_{DS} = \frac{K}{2} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] = 40 \cdot 10^6 \left[4 V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$V_{DS} + 13 V_{DS} + 25 = 0$$


$$V_{DS} = 2.35 \text{ V } (\checkmark)$$

$$10.65 \text{ V } (\times)$$

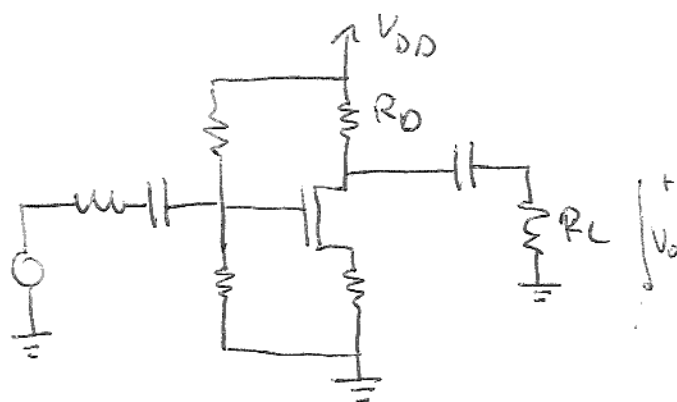

$$\begin{aligned} V_{DD} &= 20V \\ R_D &= 10k\Omega \\ R_S &= 5k\Omega \\ R_{b1} &= 15k\Omega \\ R_{b2} &= 12.3k\Omega \end{aligned}$$

① Pdo polarización

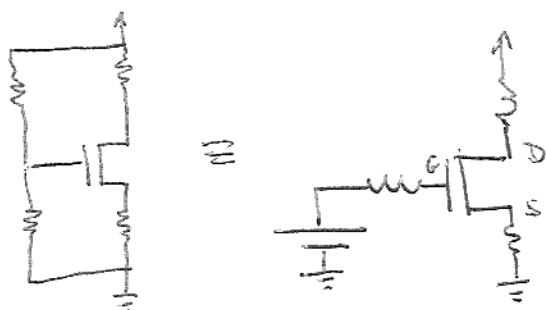

$$V_{TH} = \frac{V_{DD}}{R_{b1} + R_{b2}} \cdot R_{b2}$$

$$R_{eq} = \frac{R_{b1} \cdot R_{b2}}{R_{b1} + R_{b2}}$$

$$* V_{TH} = I_G \cdot R_{eq} + V_{GS} + I_D \cdot R_S \quad \text{with } I_G = 0$$

* Suponemos saturación

$$I_D = \frac{k}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow V_{GS}^2 - 17 = 0 \quad \begin{cases} \rightarrow 4.12V \quad (\checkmark) \\ \rightarrow -4.12V \quad (\times) \end{cases}$$


$I_D = 0.9mA$

Hay error porque $V_{GS} = 4.12 > V_T = 1V$ no está en corte

$$* V_{DD} = I_D R_D + V_{DS} + I_D R_S \Rightarrow \underline{V_{DS} = 5.4V}$$

$$V_{DS} \geq V_{GS} - V_T ? \Rightarrow 5.4 \geq 4.12 - 1 \Rightarrow \underline{\text{Saturación}}$$

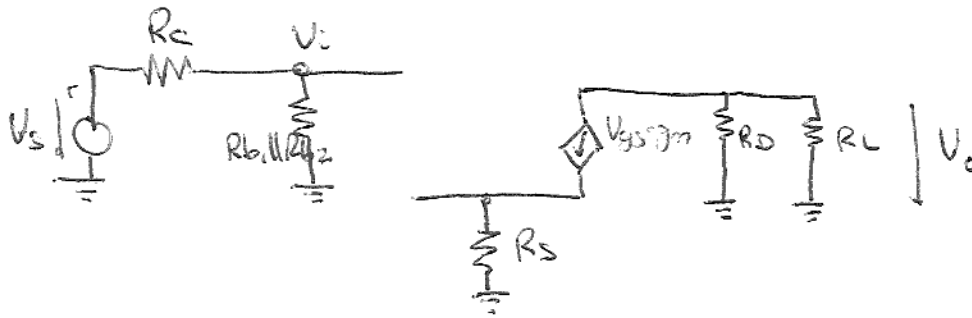$I_D = 0.9 \text{ mA}$ (g_m de pequeña señal)




$$V_i = V_{gs} + I_{R_s} \cdot R_s \quad \left\{ \begin{array}{l} V_i = V_{gs} (1 + g_m R_s) \\ I_{R_s} = V_{gs} \cdot g_m \end{array} \right.$$


$$V_o = (R_D \parallel R_L) \cdot g_m V_{gs}$$

$$\frac{V_o}{V_i} = \frac{(R_D \parallel R_L) g_m \cancel{V_{gs}}}{\cancel{V_{gs}} (1 + g_m R_s)}$$

(3)

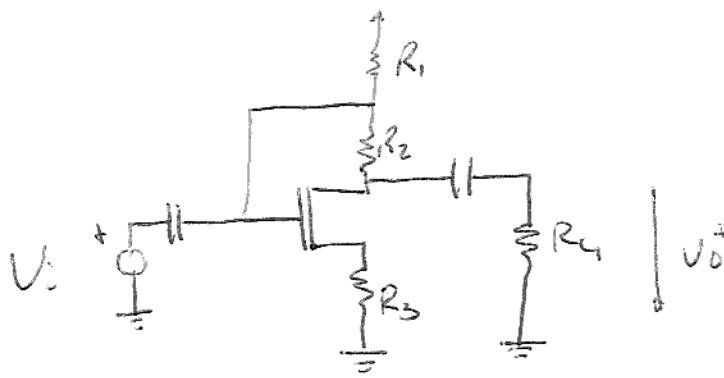

④ Polarización

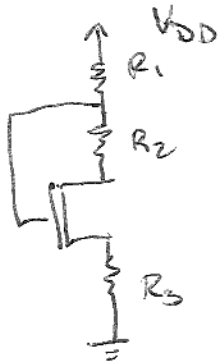

$$* V_{DD} = I_D (R_1 + R_3) + V_{GS} \quad (1)$$

$$* V_{DD} = I_D (R_1 + R_2 + R_3) + V_{DS} \quad (2)$$

$$* \text{Saturación} \quad V_{DS} \geq V_{GS} - V_T$$

$$I_D = \frac{1}{2} \frac{\mu C W}{L} (V_{GS} - V_T)^2 \quad (3)$$

(1)(3) $V_{GS} \rightarrow 3V \quad (\checkmark) > V_T = 1V \Rightarrow$ No está en corte.
 $\rightarrow -1.3V \quad (\times)$

Para que haya canal, $V_{GS} > V_T$


$$I_D = \frac{V_{DD} - V_{GS}}{R_1 + R_3} = 1.2 \cdot 10^{-3} A$$

$$(2) \quad V_{DS} = V_{DD} - I_D (R_1 + R_2 + R_3) = 2.4V$$

$$V_{DS} = 2.4V, 3V - 1V \Rightarrow \text{Saturado}$$

② Required find.

$$I_D = 1.2 \text{ mA}$$

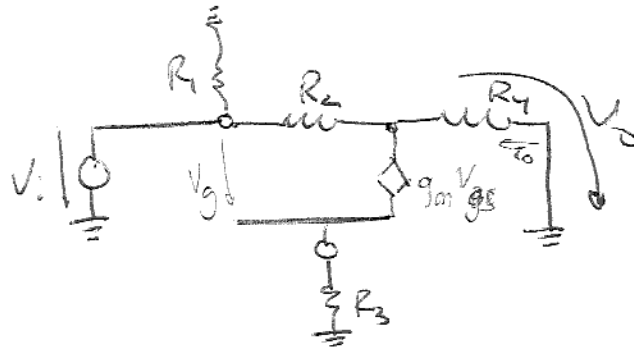

$$V_i = V_g$$

$$V_o = -i_o \cdot R_4 = -\left(g_m V_{gs} + \frac{V_i - V_o}{R_2}\right) R_4$$


$$I R_2 = \frac{V_i - V_o}{R_2}$$

$$V_{gs} = V_g - V_s = V_i - R_3 g_m V_{gs}$$

$$V_{gs} = \frac{V_i}{1 + R_3 g_m}$$

$$I_D = g_m V_{gs} + I R_2$$
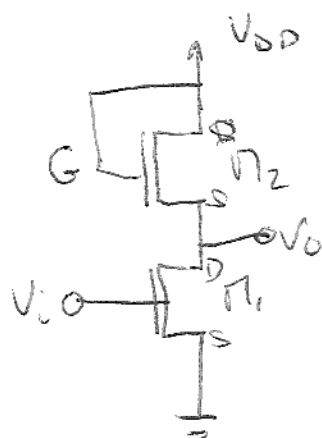
$$\frac{V_o}{V_i} = \frac{\left(\frac{1}{R_2} - \frac{g_m}{1 + g_m R_3}\right)}{\left(\frac{1}{R_2} + \frac{1}{R_4}\right)}$$



$$V_{DD} = 5V$$

$$V_T = 1V$$

$$\mu = 20 \cdot 10^6$$

$$\frac{W}{L} = 2$$

$$V_G = V_D \Rightarrow V_{GS} = V_{DS} \Rightarrow$$

$$V_{DS} \geq V_{GS} - V_T \Rightarrow$$

Siempre en saturación o
corte

Inverso en saturación

$$V_i = 0V$$

$$V_{GS} = V_i = 0V < V_T \Rightarrow \text{Corte}$$

$$I_{D1} = 0 \Rightarrow I_{D2} = 0$$

$$V_{DS} = V_T \Rightarrow I_D = 0 = \frac{1}{2} \frac{\mu W}{L} (V_{DS} - V_T)^2$$

$$V_{DD} = V_{DS2} + V_{DS1} \Rightarrow V_0 = V_{DD} - V_{DS2}$$

$$V_i = 5V$$

$$V_{GS1} = 5V = V_i > V_T \Rightarrow M_2 \text{ saturado}$$

$$I_{D1} = I_{D2} \Rightarrow \text{Hay canal}$$

* Suponemos Triodo.

$$V_{GS1} = 5V \quad V_{GS2} = V_{DS2}$$

$$V_{DS1} = V_0$$

$$I_D = \frac{\mu}{2} \frac{W}{L} (V_{DD} - V_0 - V_T)^2 = \frac{\mu}{2} \frac{W}{L} [(V_i - V_0) \cdot V_0 - \frac{V_0^2}{2}]$$

I_{D1}

I_{D2}

$$V_0 = \begin{cases} 1.17V & (\checkmark) \\ 6.82V & (X) \end{cases}$$

