

Electrical Systems

Lecture 4: Alternating current (AC) circuits II



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering


Last revised: March 9, 2021

Outline


- 1 A two-port element: magnetic coupling
- Analysis of mixed-frequency AC circuits
- Electric resonance
- Exercises and solutions

A two-port element: magnetic coupling

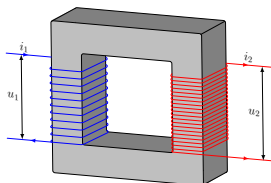A magnetic coupling is a two-port element that relates the voltages and currents of ports 1, 2 connected through a magnetic circuit.



Magnetic coupling

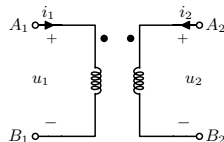

Circuit representation

A two-port element: magnetic coupling


Using the Faraday's Law

$$u_j(t) = \frac{d\Psi_j}{dt}$$

and the relationships among the flux linkage, Ψ , number of coils, N_j , and magnetic flux, ϕ_j , given by

$$\Psi_j(t) = N_j \phi_j(t), \quad \phi_j(t) = \phi(t) + \phi_{dj}(t),$$
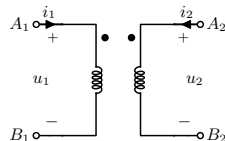
$$\phi_{dj}(t) = \frac{N_j}{\mathcal{R}_{dj}} i_j(t), \quad \phi(t) = \frac{N_1 i_1(t) + N_2 i_2(t)}{\mathcal{R}}$$



Magnetic coupling equations


$$u_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$u_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

where $L_j = \frac{N_j^2}{\mathcal{R}} + \frac{N_j^2}{\mathcal{R}_{dj}}$ and $M = \frac{N_1 N_2}{\mathcal{R}}$.

A two-port element: magnetic coupling

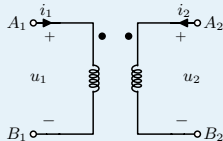
Dots in the circuit representation determine how the magnetic flux is related with the currents (wiring direction of coils)



Magnetic fluxes with the same directions

$$u_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
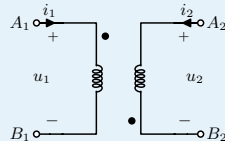
$$u_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



Magnetic fluxes with opposite directions

$$u_1(t) = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$u_2(t) = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

A two-port element: magnetic coupling

From the instantaneous power definition, $p(t) = u(t)i(t)$, we get

$$\begin{aligned} p(t) &= p_1(t) + p_2(t) = \\ &= \left(L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) i_1(t) + \left(M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \right) i_2(t) \\ &= \frac{d}{dt} \left(\frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2 \right) \\ &= \frac{d}{dt} w(t) \end{aligned}$$

where $w(t)$ is the stored energy in the magnetic coupling

$$w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2.$$

The physical constraint $w(t) > 0$ implies that

$$L_1 L_2 - M^2 \geq 0.$$

The case

$$L_1 L_2 = M^2$$

is known as a perfect coupling.

A two-port element: magnetic coupling

In steady-state, a magnetic coupling can be written with phasors as

$$\underline{U}_1 = j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2$$

$$\underline{U}_2 = j\omega M \underline{I}_1 + j\omega L_2 \underline{I}_2$$

In a matrix form,

$$\begin{bmatrix} \underline{U}_1 \\ \underline{U}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

or, using the reactance definitions

Magnetic coupling equation


$$\begin{bmatrix} \underline{U}_1 \\ \underline{U}_2 \end{bmatrix} = \begin{bmatrix} jX_1 & jX_M \\ jX_M & jX_2 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

A two-port element: magnetic coupling

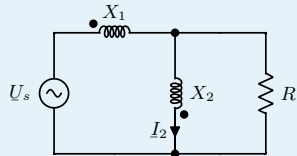Exercise 1

Calculate the current flowing through inductor X_2 , $\underline{I}_2$, for the following cases:

- 1 No magnetic coupling ($X_M = 0$)
- 2 Magnetic coupling ($X_1 X_2 - X_M^2 \geq 0$)
and short-circuit ($R = 0$)
- 3 Perfect coupling ($X_M^2 = X_1 X_2$)
- 4 Perfect coupling and $R = 0$
- 5 General case



Outline

- 1 A two-port element: magnetic coupling
- 2 Analysis of mixed-frequency AC circuits**
- 3 Electric resonance
- 4 Exercises and solutions

Analysis of mixed-frequency AC circuits

Linearity

An electrical circuit is linear if satisfies both additivity and homogeneity properties:

- Additivity: $f(x + y) = f(x) + f(y)$.
- Homogeneity: $f(kx) = kf(x)$, for all k .

An electrical circuit linear if only if is only composed by linear elements. Its analysis results in a set of linear equations.

Superposition principle

From the additivity property of a circuit the superposition principle can be derived.


The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or currents through) that element due to each independent source acting alone.

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.

Analysis of mixed-frequency AC circuits

Analysis of a circuit using the superposition principle. Steps:

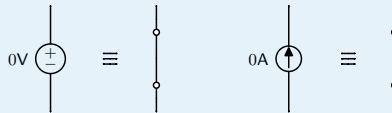- 1 Turn off all independent sources except one source (independent voltage sources are replaced by short circuit and independent current sources are replaced by open circuit).



- 2 Find the circuit voltages or currents due to that active source using nodal or mesh analysis.
- 3 Repeat step 1 for each of the other independent sources.
- 4 Find the total contribution by adding algebraically all the contributions due to the independent sources.

Analysis of mixed-frequency AC circuits

The analysis of mixed-frequency AC circuits can be done by using the Superposition Principle.


For example, consider a voltage source with harmonic content

$$u(t) = \sqrt{2} \sum_{k=1}^n U_k \cos(k\omega t + \phi_k),$$

connected to a circuit with linear elements. The current flowing through the source, $i(t)$, can be obtained as

$$i(t) = \sum_{k=1}^n i_k(t),$$

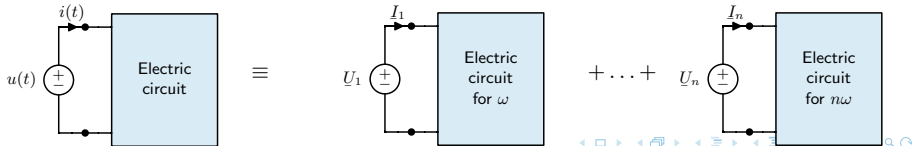
where $i_k(t)$ is the current due to the k -th term in $u(t)$.



Analysis of mixed-frequency AC circuits

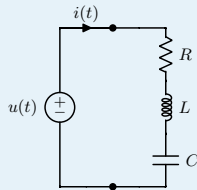Exercise 2

Consider the circuit below, where $R = 1\Omega$, $L = 1/2H$, $C = 2/3F$ and the voltage source contain a third harmonic, and takes the form $u(t) = 100\cos(t) + 100\cos(3t)$. Calculate the current absorbed by the RLC load, $i(t)$.




Outline

- 1 A two-port element: magnetic coupling
- 2 Analysis of mixed-frequency AC circuits
- 3 Electric resonance**
- 4 Exercises and solutions

Electric resonance

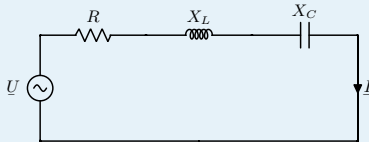Exercise 3

Motivating example: Consider a series RLC circuit with $R = 2\Omega$, $L = 150\text{mH}$ and a 100V , 50Hz , AC voltage source. Calculate the capacitance such that the imaginary part of the series impedance is zero.



Electric resonance

Electric resonance

In a series impedance, resonance occurs when, at a particular resonant frequency, the capacitive and inductive reactances of circuit elements cancel each other, i.e.,


$$\text{Im}\{\underline{Z}(R, L, C, \omega)\} = 0.$$

Consequences of series resonance


- In series resonant circuits, input voltage and currents are in phase
- Resonant circuits can generate very high voltages
- In particular, if $R = 0 \rightarrow I = \infty$, the impedance behaves as a short-circuit
- The frequency $\omega = \frac{1}{\sqrt{LC}}$, is known as the resonance frequency.

Electric resonance

Exercise 4

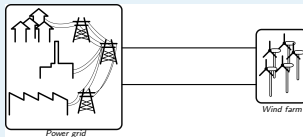

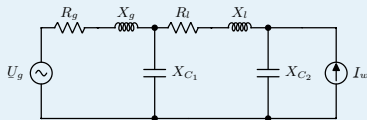The circuit below represents the behaviour of a transmission line connecting a wind farm to a power grid.



Using $R_g = 0.04\Omega$, $X_g = 0.3\Omega$, $R_l = 0.8\Omega$, $X_l = 4\Omega$ and $X_C = 770\Omega$ at 50Hz, find:

- the voltage across capacitor C_2 (parametrized by $\underline{U}_g$ and $\underline{I}_w$), and
- the resonance frequencies of the circuit.

Electric resonance

The voltage across the capacitor C_2 is

$$U_{C_2} = -jX_{C_2}Y_A U_g + Z_B I_w$$

where

$$Y_A = \frac{X_{C_1}}{Z_g(X_{C_1} + X_{C_2}) + Z_l X_{C_1} + j(Z_l Z_g - X_{C_1} X_{C_2})}$$

$$Z_B = \frac{Z_g Z_l X_{C_2} + j(Z_l + Z_g) X_{C_1} X_{C_2}}{Z_g(X_{C_1} + X_{C_2}) + Z_l X_{C_1} + j(Z_g Z_l - X_{C_1} X_{C_2})}$$


Resonance occurs at ω_r when

$$\text{Im}\{Y_A(\omega_r)\} = 0 \text{ or } \text{Im}\{Z_B(\omega_r)\} = 0.$$

Replacing $Z_l = R_l + j\omega L_l$, $Z_g = R_g + j\omega L_g$,
 $X_{C_1} = \frac{1}{\omega C_1}$ and $X_{C_2} = \frac{1}{\omega C_2}$, where L_l , L_g ,
 C_1 and C_2 are obtained from the reactances at
 50 Hz, we get



$$\omega_r = 4192.84 \text{ rad/s}$$

$$\omega_r = 16543.3 \text{ rad/s}$$

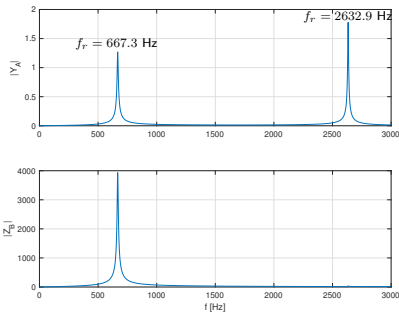

Electric resonance

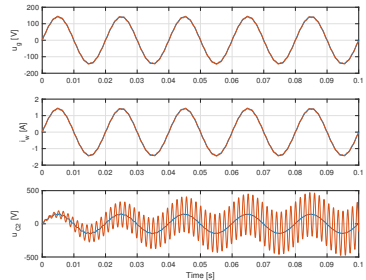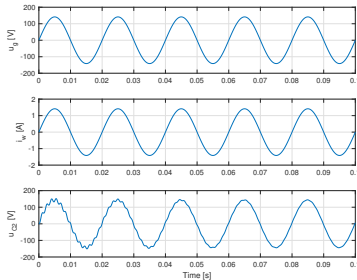Simulation results with $\underline{U}_g = 100 \text{ V}$, $\underline{I}_w = 1 \text{ A}$: (left) without higher frequencies, and (right) with additional noise/disturbance in the voltage and current, at the resonance frequency, $f_r = 667.3 \text{ Hz}$, with 3% amplitude.



The resonance effect dramatically affect to the performance of the transmission line.

Outline


- 1 A two-port element: magnetic coupling
- 2 Analysis of mixed-frequency AC circuits
- 3 Electric resonance
- 4 Exercises and solutions**

Exercises I

Exercise 5

[CM30] Consider the circuit on the right. Find the measure of L_1 :


- 1 if inductors X_1, X_2 are magnetically decoupled and L_1 is a voltmeter.
- 2 if inductors X_1, X_2 are magnetically coupled and L_1 is a voltmeter.
- 3 if inductors X_1, X_2 are magnetically coupled and L_1 is an ammeter.

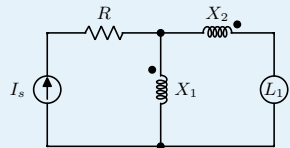

Exercises II

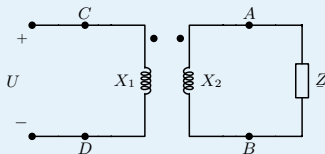Exercise 6

[CM51] Given the circuit below with a magnetic coupling the following parameters $X_1 = 50\Omega$, $X_2 = 5\Omega$, and $\underline{Z} = 2 + j1\Omega$



Assuming perfect coupling, find:


- 1 The reactance of the capacitor that, connected between A and B, improves the power factor seen from A, B up to one.
- 2 The reactance of the capacitor that, connected between C and D, improves the power factor seen from C, D up to one.

Exercises III

Exercise 7

[CM52] The circuit on the right have the following parameters: $U = 220\text{V}$, $R = 5\Omega$, $X_1 = 2\Omega$ and $X_2 = 3\Omega$. Assuming that:

- 1 X_1, X_2 are not coupled, calculate the supplied current and the equivalent impedance seen from the voltage source.
- 2 X_1, X_2 are perfectly coupled, calculate the supplied current and the equivalent impedance seen from the voltage source.
- 3 X_1, X_2 are not coupled, calculate the value of the required capacitor that connected in parallel, ensures a unitary power factor.
- 4 X_1, X_2 are perfectly coupled, calculate the value of the required capacitor that connected in parallel, ensures a unitary power factor.

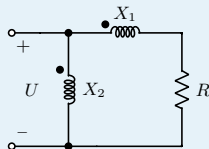

Solutions I

Solution to Exercise 1

$$\textcircled{1} \quad I_2 = \frac{R}{j((R+jX_2)X_1+RX_2)} U_s$$

$$\textcircled{3} \quad I_2 = \frac{R+jX_M}{jR(X_1+X_2-2X_M)} U_s$$

$$\textcircled{2} \quad I_2 = -\frac{jX_M}{X_1X_2-X_M^2} U_s$$

$$\textcircled{4} \quad I_2 = 0$$

$$\textcircled{5} \quad I_2 = \frac{R+jX_M}{j((R+jX_2)(X_1-X_M)+(R+jX_M)(X_2-X_M))} U_s$$

Solution to Exercise 2

$$i(t) = 50\sqrt{2}\cos(t + 45^\circ) + 50\sqrt{2}\cos(3t - 45^\circ)$$

Solutions II

Solution to Exercise 5

- 1 $L_1 = X_1 I_s$
- 2 $L_1 = (X_1 + X_m) I_s$
- 3 $L_1 = \frac{X_1 + X_m}{X_1 + X_2 + 2X_m} I_s$

Solution to Exercise 6

- 1 $X_C = 5\Omega$
- 2 $X_C = 25\Omega$

Solution to Exercise 7

- 1 $\underline{Z}_{eq} = 0.9 + j2.1\Omega, \underline{I} = 37.93 - j88.50\text{A}$
- 2 $\underline{Z}_{eq} = 0.06 + j2.99\Omega, \underline{I} = 1.48 - j73.33\text{A}$
- 3 $X_C = 2.486\Omega$
- 4 $X_C = 3\Omega$

Solutions III

Solution to Exercise 3

$$C = 67.55\mu\text{F}, \quad U_L = U_C = 2356.2\text{V}$$


The voltage and current phasors are

$$\underline{I} = 50\text{A}$$

$$\underline{U}_R = 100\text{V}$$

$$\underline{U}_L = 0 + j2356.19\text{V}$$

$$\underline{U}_C = 0 - j2356.19\text{V}$$

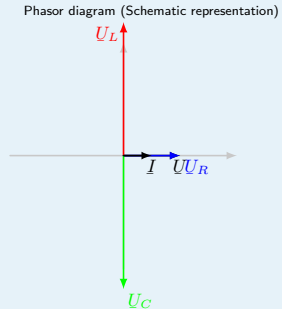

Solutions IV

Solution to Exercise 4

- 1 $\underline{U}_{C_2} = (1.006 - j0.0012)\underline{U}_g + (1.849 + j4.323)\underline{I}_w$
- 2 Resonance frequencies at:
 $\omega = 4192.84 \text{ rad/s}, \omega = 16543.3 \text{ rad/s}$

Electrical Systems

Lecture 4: Alternating current (AC) circuits II



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering

Last revised: March 9, 2021