

Electrical Systems

Lecture 8: Electrical power in three-phase circuits



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering

Last revised: April 27, 2021

Outline

- 1 **Instantaneous electrical power**
- 2 Electrical power in three-phase circuits
- 3 Electrical power in balanced three-phase loads
- 4 Power factor correction in balanced three-phase circuits
- 5 Exercises and solutions

Instantaneous electrical power

Instantaneous three-phase electrical power

$$p(t) = p_A(t) + p_B(t) + p_C(t)$$

Given the three-phase load above, where

$$u_{AN}(t) = U_{AN}\sqrt{2}\cos(\omega t + \phi_{Au})$$

$$u_{BN}(t) = U_{BN}\sqrt{2}\cos(\omega t + \phi_{Bu})$$

$$u_{CN}(t) = U_{CN}\sqrt{2}\cos(\omega t + \phi_{Cu})$$


$$i_A(t) = I_A\sqrt{2}\cos(\omega t + \phi_{Ai})$$

$$i_B(t) = I_B\sqrt{2}\cos(\omega t + \phi_{Bi})$$

$$i_C(t) = I_C\sqrt{2}\cos(\omega t + \phi_{Ci})$$

electrical power is
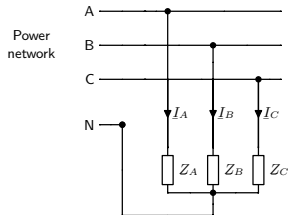
$$p(t) = u_{AN}(t)i_A(t) + u_{BN}(t)i_B(t) + u_{CN}(t)i_C(t)$$




Instantaneous electrical power

Numeric example, with $Z_A = Z_B = Z_C = \frac{3}{2} \angle 30^\circ \Omega$:

$$u_{AN}(t) = \cos(100\pi t) \text{ V}$$

$$u_{BN}(t) = 0.8 \cos(100\pi t - 2\pi/3) \text{ V}$$
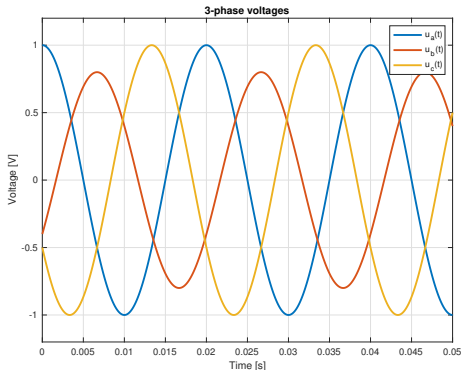
$$u_{CN}(t) = \cos(100\pi t + 2\pi/3) \text{ V}$$



Instantaneous electrical power

Numeric example, with $Z_A = Z_B = Z_C = \frac{3}{2} \angle 30^\circ \Omega$:

$$u_{AN}(t) = \cos(100\pi t) \text{ V}$$


$$u_{BN}(t) = 0.8 \cos(100\pi t - 2\pi/3) \text{ V}$$

$$u_{CN}(t) = \cos(100\pi t + 2\pi/3) \text{ V}$$

$$i_A(t) = 2/3 \cos(100\pi t - \pi/6) \text{ A}$$

$$i_B(t) = 0.8 \cdot 2/3 \cos(100\pi t - 2\pi/3 - \pi/6) \text{ A}$$

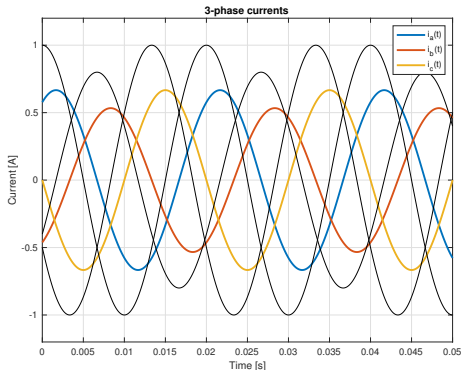
$$i_C(t) = 2/3 \cos(100\pi t + 2\pi/3 - \pi/6) \text{ A}$$



Instantaneous electrical power


Numeric example, with $\underline{Z}_A = \underline{Z}_B = \underline{Z}_C = \frac{3}{2} \angle 30^\circ \Omega$:
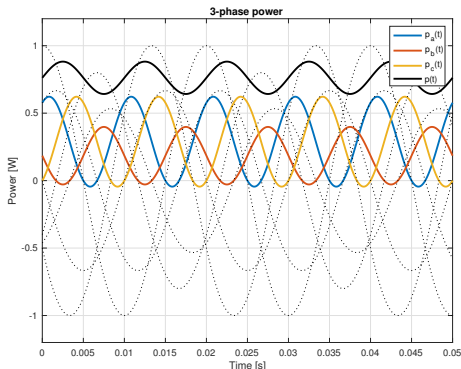
$$\begin{aligned}
 p(t) &= p_A(t) + p_B(t) + p_C(t) \\
 &= 1/3(\cos(200\pi t) + 0.64\cos(200\pi t - 2\pi/3) + \cos(200\pi t + 2\pi/3)) + \sqrt{3}/3(1.32) \\
 &= 0.762 - 0.12\cos(200\pi t - 2\pi/3) \text{ W}
 \end{aligned}$$



Instantaneous electrical power

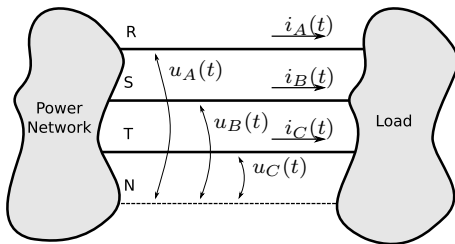Consider now a balanced three-phase system



$$u_{AN}(t) = U_P \sqrt{2} \cos(\omega t)$$

$$u_{BN}(t) = U_P \sqrt{2} \cos\left(\omega t - \frac{2\pi}{3}\right)$$

$$u_{CN}(t) = U_P \sqrt{2} \cos\left(\omega t + \frac{2\pi}{3}\right)$$

$$i_A(t) = I \sqrt{2} \cos(\omega t - \phi)$$

$$i_B(t) = I \sqrt{2} \cos\left(\omega t - \phi - \frac{2\pi}{3}\right)$$

$$i_C(t) = I \sqrt{2} \cos\left(\omega t - \phi + \frac{2\pi}{3}\right)$$

Instantaneous electrical power

Instantaneous electrical power in three-phase systems

$$p(t) = p_A(t) + p_B(t) + p_C(t)$$

$$p(t) = 2U_P I (\cos(\omega t)\cos(\omega t - \phi) + \cos(\omega t - 120^\circ)\cos(\omega t - \phi - 120^\circ) + \cos(\omega t + 120^\circ)\cos(\omega t - \phi + 120^\circ))$$

Hint:

$$\cos(a)\cos(b) = \frac{1}{2}(\cos(a + b) + \cos(a - b)) \quad \cos(a) + \cos(a - 120^\circ) + \cos(a + 120^\circ) = 0$$

Instantaneous electrical power in balanced three-phase systems

$$p(t) = 3U_P I \cos(\phi)$$


Instantaneous electrical power

Numeric example, with $\underline{Z}_A = \underline{Z}_B = \underline{Z}_C = \frac{3}{2} \angle 30^\circ \Omega$:

$$u_{AN}(t) = \cos(100\pi t) \text{ V}$$

$$u_{BN}(t) = \cos(100\pi t - 2\pi/3) \text{ V}$$
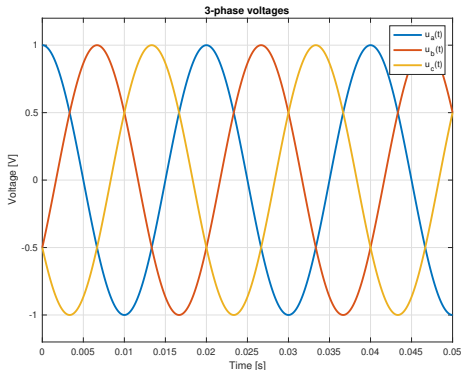
$$u_{CN}(t) = \cos(100\pi t + 2\pi/3) \text{ V}$$



Instantaneous electrical power

Numeric example, with $Z_A = Z_B = Z_C = \frac{3}{2} \angle 30^\circ \Omega$:

$$u_{AN}(t) = \cos(100\pi t) \text{ V}$$


$$u_{BN}(t) = \cos(100\pi t - 2\pi/3) \text{ V}$$

$$u_{CN}(t) = \cos(100\pi t + 2\pi/3) \text{ V}$$

$$i_A(t) = 2/3 \cos(100\pi t - \pi/6) \text{ A}$$

$$i_B(t) = 2/3 \cos(100\pi t - 2\pi/3 - \pi/6) \text{ A}$$

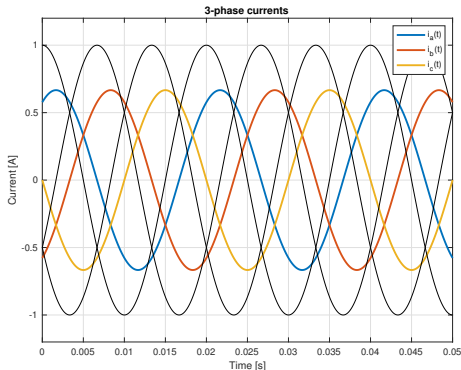
$$i_C(t) = 2/3 \cos(100\pi t + 2\pi/3 - \pi/6) \text{ A}$$



Instantaneous electrical power

Numeric example, with $Z_A = Z_B = Z_C = \frac{3}{2} \angle 30^\circ \Omega$:
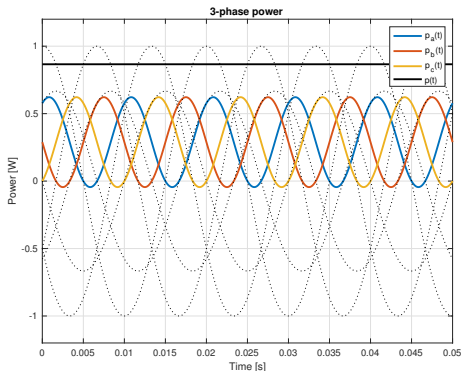
$$\begin{aligned}
 p(t) &= 1/3 (\cos(200\pi t) + \cos(\pi/6)) \\
 &+ 1/3 (\cos(200\pi t - 2\pi/3) + \cos(\pi/6)) \\
 &+ 1/3 (\cos(200\pi t + 2\pi/3) + \cos(\pi/6)) = 0.86\text{W}
 \end{aligned}$$



Instantaneous electrical power

Summarizing

- The instantaneous electrical power in three phase systems is the sum of the instantaneous powers in each phase.
- The instantaneous electrical power in **balanced three phase systems** is **constant**.

Outline

- 1 Instantaneous electrical power
- 2 Electrical power in three-phase circuits**
- 3 Electrical power in balanced three-phase loads
- 4 Power factor correction in balanced three-phase circuits
- 5 Exercises and solutions

Electrical power in three-phase circuits

Total active power and per phase powers

It can be shown that the total active power is the sum of the phase active powers

$$P = P_A + P_B + P_C$$

where

$$P_i = \operatorname{Re}(\underline{U}_i \underline{I}_i^*) = U_i I_i \cos \phi_i, \quad i = A, B, C$$

The per phase reactive powers are defined as

$$Q_i = \operatorname{Im}(\underline{U}_i \underline{I}_i^*) = U_i I_i \sin \phi_i, \quad i = A, B, C$$

and the phase apparent powers become

$$S_i = U_i I_i = \sqrt{P_i^2 + Q_i^2}, \quad i = A, B, C$$

Electrical power in three-phase circuits

Arithmetic apparent power

The arithmetic apparent power is defined as

$$S_{Ar} = S_A + S_B + S_C$$

that implies

$$PF_{Ar} = \frac{P}{S_{Ar}}.$$

Vector apparent power

The vector apparent power is defined as

$$S_V = |\underline{S}_V|$$

where


$$\underline{S}_V = P_A + P_B + P_C + j(Q_A + Q_B + Q_C) = P + jQ$$

that implies

$$PF_V = \frac{P}{S_V}.$$

Electrical power in three-phase circuits

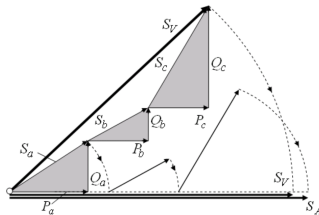A geometrical interpretation of arithmetic and vector apparent powers, S_{Ar} (labeled as S_A in the figure) and S_V , respectively. Figure extracted from IEEE Standard definitions 1459-2010.




In balanced three-phase systems, both definitions give identical results. However, under unbalanced conditions one has $S_{Ar} \geq S_V$ which implies $PF_{Ar} \leq PF_V$.

Note:

IEEE Standard definitions 1459-2010 recommends to renounce to the arithmetic and vector apparent power definitions and replace them with the effective apparent power. However, for simplicity, **the vector apparent power is adopted in this course.**

Electrical power in three-phase circuits

Exercise 1

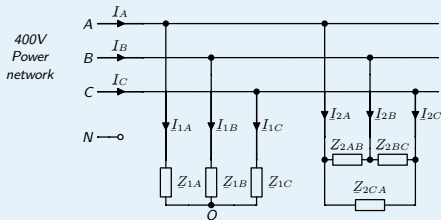

$$\begin{aligned} Z_{1A} &= 10\Omega, \\ Z_{1B} &= 10 - j10\Omega, \\ Z_{1C} &= 5 + j10\Omega, \\ Z_{AB} &= 20\Omega, \\ Z_{BC} &= j20\sqrt{3}\Omega, \\ Z_{CA} &= -j20\sqrt{3}\Omega. \end{aligned}$$

Given the circuit above, find:

- 1 the power grid currents (I_A, I_B, I_C), and
- 2 the grid powers (P, Q and S).

Outline

- 1 Instantaneous electrical power
- 2 Electrical power in three-phase circuits
- 3 Electrical power in balanced three-phase loads**
- 4 Power factor correction in balanced three-phase circuits
- 5 Exercises and solutions

Electrical power in balanced three-phase loads

The power for each i -phase (where $\alpha_A = 0$, $\alpha_B = -120^\circ$, $\alpha_C = 120^\circ$)

$$p_i(t) = 2U_P I (\cos(\omega t + \alpha_i) \cos(\omega t - \phi + \alpha_i))$$

can be split into a DC term plus and an oscillating term

$$p_i(t) = U_P I \cos(\phi) + U_P I \cos(2\omega t - \phi + 2\alpha_i),$$

or, alternatively,

$$p_i(t) = U_P I \cos(\phi) (1 + \cos(2\omega t + 2\alpha_i)) + U_P I \sin(\phi) \sin(2\omega t + 2\alpha_i)$$

Hint:

$$\cos(a - b) = \cos(a)\cos(b) + \sin(a)\sin(b)$$

Then

$$p(t) = 3U_P I \cos(\phi) + U_P I \sin(\phi) \underbrace{(\sin(2\omega t) + \sin(2\omega t + 120^\circ) + \sin(2\omega t - 120^\circ))}_{=0}$$

Electrical power in balanced three-phase loads

Active power in balanced three-phase loads

$$P = 3U_P I \cos(\phi)$$

where U_P is the phase voltage and I is the line current, or using the line voltage $U = \frac{1}{\sqrt{3}}U_P$,

$$P = \sqrt{3}UI \cos(\phi).$$

Reactive power in balanced three-phase loads

$$Q = 3U_P I \sin(\phi) = \sqrt{3}UI \sin(\phi).$$

Apparent power in balanced three-phase loads


$$S = 3U_P I = \sqrt{3}UI.$$

Power factor in balanced three-phase loads

$$PF = \frac{P}{S}.$$

Electrical power in balanced three-phase loads

Exercise 2

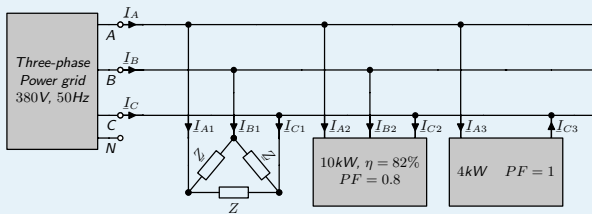

From the electrical installation above, where $Z = 20 + j20\Omega$, find:

- 1 the power grid currents (I_A , I_B , I_C), and
- 2 the grid powers (P , Q and S).

Outline

- 1 Instantaneous electrical power
- 2 Electrical power in three-phase circuits
- 3 Electrical power in balanced three-phase loads
- 4 Power factor correction in balanced three-phase circuits**
- 5 Exercises and solutions


PF correction in balanced three-phase circuits

Exercise 3

Motivating example: A three-phase 4.5kV transmission line connects a the power grid with a 5MW load placed 100m far from the power substation. If the resistivity of the line is $4.5 \cdot 10^{-4} \Omega m^{-1}$. Calculate for $PF=0.8$ and $PF=1$:

- the power losses, and
- the annual cost of the losses (Consider 5c€/kWh).

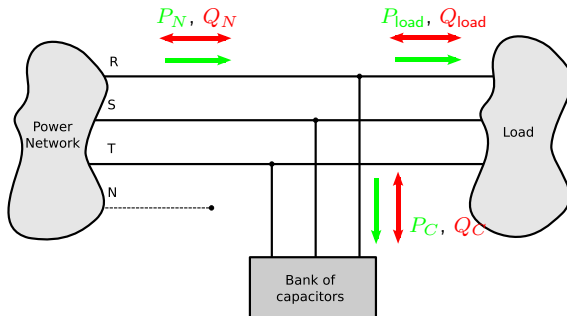PF correction in balanced three-phase circuits



P and Q of a 3-phase load

$$P_{load} = 3U_P I_{load} \cos\phi_{load}$$

$$Q_{load} = 3U_P I_{load} \sin\phi_{load}$$

The total 3-phase power

$$\underline{S}_N = P_N + jQ_N$$

$$= P_{load} + P_C + j(Q_{load} + Q_C)$$

PF correction in balanced three-phase circuits

P and Q of a Y-bank of capacitors

$$P_{CY} = 0$$
$$Q_{CY} = -3\omega C_Y U_P^2$$

Total reactive power

$$Q_N = Q_{\text{load}} + Q_{CY}$$
$$= Q_{\text{load}} - 3\omega C_Y U_P^2$$

Capacitance of the Y-bank

$$C_Y = \frac{P(\tan \phi_{\text{load}} - \tan \phi_N)}{3\omega U_P^2}$$
$$= \frac{P(\tan \phi_{\text{load}} - \tan \phi_N)}{\omega U_L^2}$$

P and Q of a Δ -bank of capacitors

$$P_{C\Delta} = 0$$
$$Q_{C\Delta} = -3\omega C_{\Delta} U_L^2$$

Total reactive power

$$Q_N = Q_{\text{load}} + Q_{C\Delta}$$
$$= Q_{\text{load}} - 3\omega C_{\Delta} U_L^2$$

Capacitance of the Δ -bank

$$C_{\Delta} = \frac{P(\tan \phi_{\text{load}} - \tan \phi_N)}{3\omega U_L^2}$$
$$= \frac{P(\tan \phi_{\text{load}} - \tan \phi_N)}{9\omega U_P^2}$$

Outline

- Instantaneous electrical power
- Electrical power in three-phase circuits
- Electrical power in balanced three-phase loads
- Power factor correction in balanced three-phase circuits
- 5** ● Exercises and solutions

Exercises I

Exercise 4

CT1: An electrical installation with 18 devices is connected to a symmetric and balanced 400V 50Hz power network. See table below.

Num.	Conn.	Unitary P [kW]	Unitary Q [kvar]	Unitary S [kVA]	PF
3	D	20	–	–	0.6(i)
10	Y	4	2.5	–	–
5	Y	–	–	4	1

- 1 Calculate the line currents.
- 2 Calculate the bank of capacitors required to set the power factor up to 0.96(i). Which is the new absorbed current?

Exercises II

Exercise 5

CT2: A company has the following (balanced) three-phase loads connected to a 380V power grid

- a) $P = 50\text{kW}$, $\cos\varphi = 0.8(i)$, Y-connected load
- b) $P = 24\text{kW}$, $Q = 12\text{kvar}$, Δ -connected load
- c) $S = 20\text{kVA}$, $\cos\varphi = 0.96(i)$, Δ -connected load
- d) $P = 20\text{kW}$, $\cos\varphi = 1$, Y-connected load

- 1 Calculate the line currents.
- 2 Calculate equivalent impedances for each load.
- 3 With the obtained impedances, sketch the electrical circuit of the installation.

Solutions I

Solution to Exercise 1

- $\underline{I}_{A1} = 5.13 \angle -49.36^\circ \text{A}$, $\underline{I}_{A2} = 30.55 \angle 40.89^\circ \text{A}$, $\underline{I}_A = 30.95 \angle 31.36^\circ \text{A}$
 $\underline{I}_{B1} = 27.84 \angle -97.65^\circ \text{A}$, $\underline{I}_{B2} = 30.55 \angle -160.89^\circ \text{A}$, $\underline{I}_B = 49.74 \angle -130.91^\circ \text{A}$
 $\underline{I}_{C1} = 31.49 \angle 89.33^\circ \text{A}$, $\underline{I}_{C2} = 11.55 \angle -60^\circ \text{A}$, $\underline{I}_C = 22.35 \angle 74.05^\circ \text{A}$
- $P_1 = 12.97 \text{kW}$, $Q_1 = 2.16 \text{kvar}$, $S_1 = 13.15 \text{kVA}$
 $P_2 = 8 \text{kW}$, $Q_2 = 0 \text{kvar}$, $S_2 = 8 \text{kVA}$
 $P = 20.97 \text{kW}$, $Q = 2.16 \text{kvar}$, $S = 21.08 \text{kVA}$

Solutions II

Solution to Exercise 2

- $\underline{I}_{A1} = 23.27\angle -45^\circ \text{A}$, $\underline{I}_{B1} = 23.27\angle -165^\circ \text{A}$, $\underline{I}_{C1} = 23.27\angle 75^\circ \text{A}$
 $\underline{I}_{A2} = 23.16\angle -36.87^\circ \text{A}$, $\underline{I}_{B2} = 23.16\angle -156.87^\circ \text{A}$, $\underline{I}_{C2} = 26.47\angle 83.13^\circ \text{A}$
 $\underline{I}_{A3} = \underline{I}_{C3} = 10.52\angle -30^\circ \text{A}$, $\underline{I}_{B3} = 0 \text{A}$
 $\underline{I}_A = 56.68\angle -38.92^\circ \text{A}$, $\underline{I}_B = 46.31\angle -160.94^\circ \text{A}$, $\underline{I}_C = 50.74\angle 90.36^\circ \text{A}$
- $P_1 = 10.83 \text{kW}$, $Q_1 = 10.83 \text{kvar}$, $S_1 = 15.3159 \text{kVA}$,
 $P_2 = 12.1951 \text{kW}$, $Q_2 = 9.1463 \text{kvar}$, $S_2 = 15.2439 \text{kVA}$,
 $P_3 = 4 \text{kW}$, $Q_3 = 0 \text{kvar}$, $S_3 = 4 \text{kVA}$
 $P = 27.0251 \text{kW}$, $Q = 19.9763 \text{kvar}$, $S = 33.6067 \text{kVA}$

Solution to Exercise 3

	Current [A]	Losses [kW]	Annual cost [€]
PF=0.8	801.9	86.8	38021.2
PF=1	641.5	55.6	24333.3

Solutions III

Solution to Exercise 4

- 1 $I = 230\text{A}$
- 2 $Q_c = 70\text{kvar}$, $I = 180.4\text{A}$

Solution to Exercise 5

- 1 $\underline{I}_A = 191.28 \angle -25.95^\circ \text{A}$, $\underline{I}_B = a^2 \underline{I}_A \text{A}$, $\underline{I}_C = a \underline{I}_A \text{A}$,
- 2 $\underline{Z}_a = 1.848 + j1.386\Omega$, $\underline{Z}_b = 14.440 + j7.220\Omega$, $\underline{Z}_c = 20.794 + j6.065\Omega$,
 $\underline{Z}_d = 7.220\Omega$

Electrical Systems

Lecture 8: Electrical power in three-phase circuits



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering

Last revised: April 27, 2021