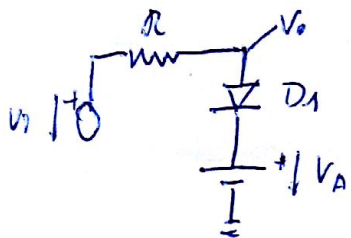



EJERCICIOS
ELECTRÓNICA

1

6) $V_A = 4V$, $I_{max} = 25mA$, $R = 1K\Omega$



a) Suprimiendo D_1 on, $I_0 = 0$

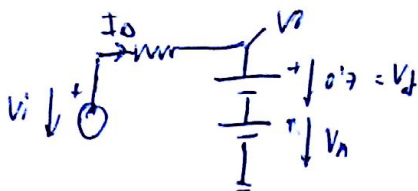


$$V_i - I_0 R - 0.7 - 4 = 0$$

$$V_i = 4.7V$$


Si $V_i < 4.7 \rightarrow D_1$ off

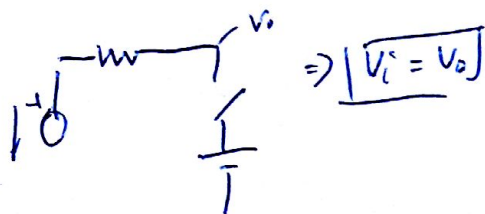Si $V_i \geq 4.7 \rightarrow D_1$ ON
Si $V_i < 4.7 \rightarrow D_1$ off



$$\Rightarrow V_i = V_o$$

Si $V_i \geq 4.7 \rightarrow D_1$ ON

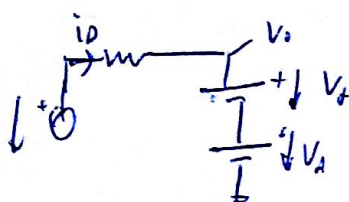

$$i_D = \frac{V_i - 0.7 - 4}{R}$$

$$V_o = V_i - I \cdot R = V_i - \frac{V_i - 0.7 - 4}{R} R =$$

$$V_o = 4.7$$

c) $i_D < 25mA$

$$i_D = \frac{V_i - 0.7 - 4}{R} < 25mA \Rightarrow V_i - 0.7 - 4 < 25mA \cdot 1K$$

$$V_i < 25 + 4.7 \Rightarrow V_i \leq 29.7V$$


Si $V_i > 29.7 \rightarrow D_1$ Arde.

Cartagena99


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

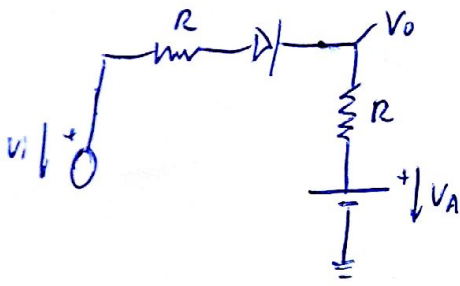⑦ $V_A = 6V$; $I_{max} = 25mA$, $R = 1k\Omega$



a) Suponiendo diodo on, $I_D = 0$

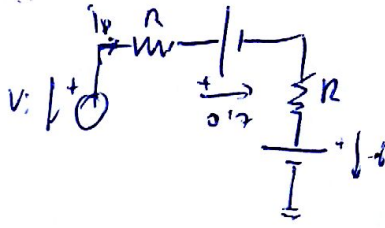


$$V_i - \frac{i_D R}{0} - 0.7 - \frac{i_D R}{0} - 6 = 0$$

$$V_i = 6.7$$


$$\text{Si } \left\{ \begin{array}{l} V_i > 6.7 \rightarrow D_1 \text{ on} \\ V_i < 6.7 \rightarrow D_1 \text{ off} \end{array} \right.$$

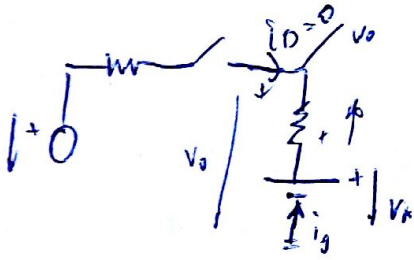b) Si $V_i < 6.7 \rightarrow D_1 \text{ off}$



$$\boxed{V_o = V_A = 6V}$$

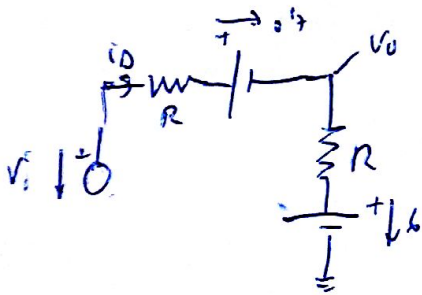Si $V_i > 6.7 \rightarrow D_1 \text{ on}$



$$i_D = \frac{V_i - 0.7 - 6}{2R} = \frac{V_i - 6.7}{2R}$$

$$V_o = i_D R + 6 = 6 + \frac{V_i - 6.7}{2R} \cdot R \Rightarrow V_o = \frac{V_i + 5.3}{2}$$


$$\boxed{V_o = \frac{V_i + 5.3}{2}}$$

Cartagena99


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

③ $V_A = 3V$

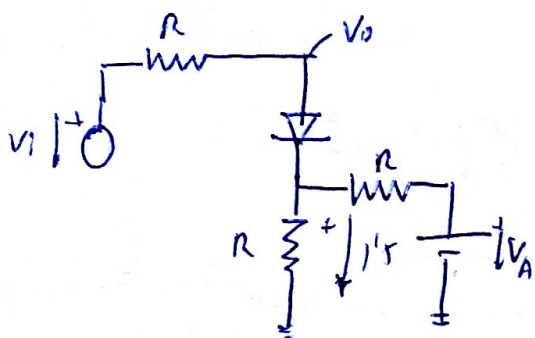

a) Suponemos D_1 ON, $I_{D2} = 0$

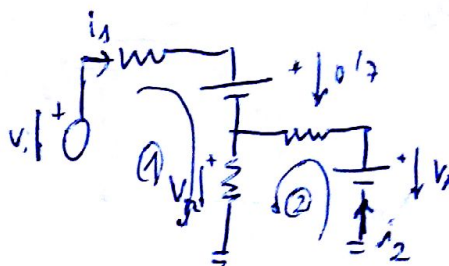

$$V_A = V_A \frac{R}{2R} = \frac{V_A}{2} = \frac{3}{2} = 1.5$$

① $V_i - i_1 R - 0.7 - i_2 R = 0$

$V_i - 0.7 - i_2 R = 0 \Rightarrow V_i - 0.7 - \frac{V_A}{2R} R = 0$

② $V_A - i_2 R - i_2 R = 0$

$V_A - 2i_2 R = 0$

$i_2 = \frac{V_A}{2R}$


$V_i - 0.7 - \frac{3}{2} = 0$

$V_i = 2.2$


Si $V_i > 2.2 \rightarrow D_1$ ON
 $V_i < 2.2 \rightarrow D_2$ OFF

b) Si $V_i < 2.2 \rightarrow D_1$ OFF

Si $V_i > 2.2 \rightarrow D_1$ ON

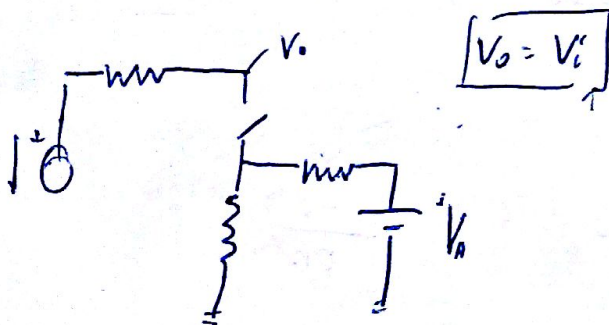

$V_o = V_i - i_1 R$

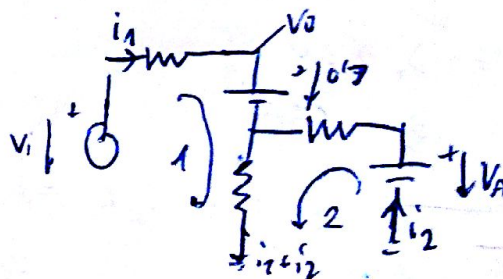

① $V_i - i_1 R - 0.7 - (i_1 + i_2) R = 0$


② $V_A - i_2 R - (i_1 + i_2) R = 0$

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70



2

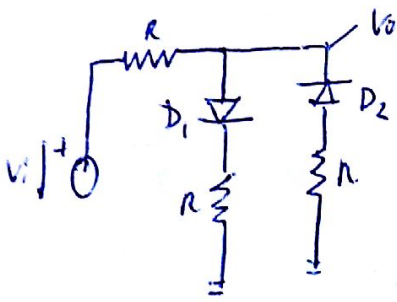

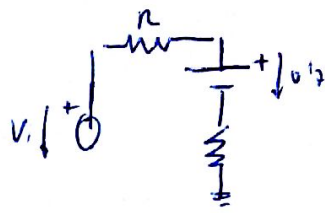
1) a) Supongamos D_1 ON $\rightarrow i_D = 0$



$$V_i - i_D R - 0.7 - i_D R = 0$$

$$V_i = 0.7$$

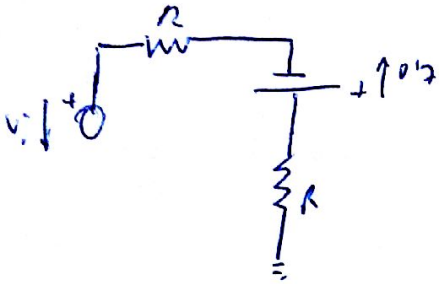Si $V_i \geq 0.7 \rightarrow D_1$ ON
 $V_i < 0.7 \rightarrow D_1$ OFF




$$V_i = i_D R - 0.7 + i_D R$$

$$V_i = -0.7$$

Si $V_i \leq -0.7 \rightarrow D_2$ ON
 $V_i > -0.7 \rightarrow D_2$ OFF

4) HIPOTESIS $\rightarrow D_1 D_2$ OFF

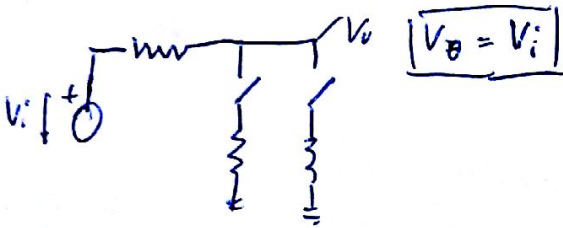


Comprobamos

D_1 OFF $\rightarrow V_i < 0.7 \rightarrow$ ~~ON~~

D_2 OFF $\rightarrow V_i > -0.7$

Si $-0.7 < V_i < 0.7 \rightarrow D_1$ OFF D_2 OFF

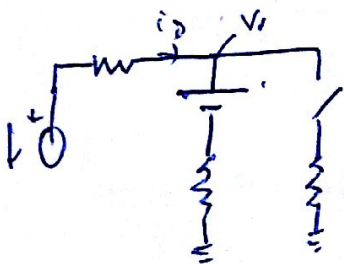Si $\rightarrow V_i \geq 0.7 \rightarrow D_1 \rightarrow$ ON
 $D_2 \rightarrow$ OFF



$$V_0 = 0.7 + i_D R \Rightarrow V_0 = 0.7 + \frac{V_i - 0.7 R}{2R}$$

$$V_i = V_i \quad i_D = \frac{V_i - 0.7}{2R}$$

$$V_0 = \frac{V_i + 0.7}{2}$$

Si $V_i \leq -0.7 \rightarrow D_1$ OFF

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

Cartagena99


$$V_0 = V_i + \frac{-V_i - 0.7}{2R} R$$

$$V_0 = \frac{V_i - 0.7}{2}$$


Continuación 2

V_i	D_1	D_2	V_o
$V_i \leq -0.7$	OFF	ON	$\frac{V_i - 0.7}{2}$
$-0.7 < V_i < 0.7$	OFF	OFF	V_i
$V_i \geq 0.7$	ON	OFF	$\frac{V_i + 0.7}{2}$

8) $|V_o| = 7.5V, I_{max} = 100mA, P_{2,max} = 600mW, R = 1k\Omega$

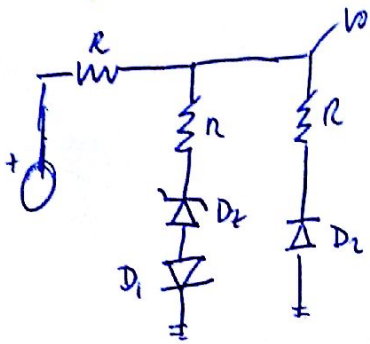

a) Suponemos D_2 ON $I_D = 0$

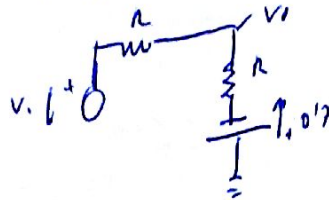

$$V_i = I_D R - I_{D0} R + 0.7 =$$


$$V_i = -0.7$$

Si $V_o \leq -0.7$ D_1 ON
 Si $V_o > -0.7$ D_2 OFF

$$V_i = -0.7 + 0.7 = 0$$

Si $V_o \geq 7.2$ D_2 y D_1 ON
 Si $V_o < 7.2$ OFF OFF

HIPO D_1 OFF
 D_2 OFF
 D_L OFF

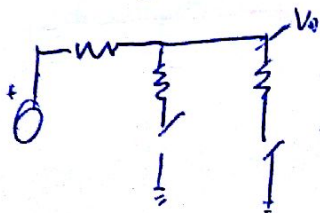

$V_o = V_i$

Comprobamos

D_2 ON, OFF $\rightarrow V_o < 7.2$

D_2 OFF $\rightarrow V_i > -0.7$ D_2 OFF

$-0.7 < V_i < 7.2$ D_1, D_2, D_L OFF

... $V_i > -0.7$ D_2 ON D_1 OFF


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

$$V_i = -2i_D R - 0.7$$

$$-V_i = 0.7$$

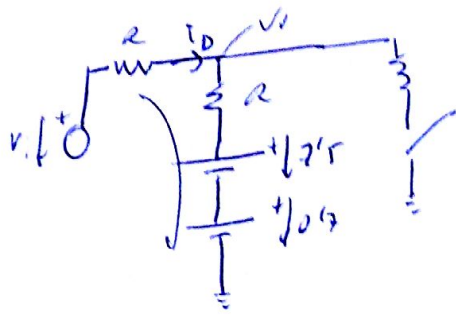Si $V_i > 8'2 \rightarrow D_2$ RUPT D_1 ON
 P_2 OFF



$$i_D = \frac{V_i - 7'5 - 0'7}{2R} = \frac{V_i - 8'2}{2R}$$

$$V_o = V_i - i_D R$$

$$V_o = V_i - \left(\frac{V_i - 8'2}{2R} \right) R = \frac{V_i + 8'2}{2}$$

$$\boxed{V_o = \frac{V_i + 8'2}{2}}$$

V_i	D_1	D_2	D_3	V_o
$V_i < -0'7$	OFF	ON	OFF	$V_i - V_i$ $\rightarrow \frac{V_i - 0'7}{2}$
$-0'2 V_i < 8'2$	OFF	OFF	OFF	V_i
$V_i > 8'2$	ON	OFF	RUPT	$\frac{V_i + 8'2}{2}$

b) Limitación Diodes $\rightarrow I_D < 100 \text{ mA}$

$$D_1 \rightarrow i_D = \frac{V_i - 7'2}{2R} < 100 \text{ mA} \Rightarrow V_i - 7'2 < 200$$

$$\boxed{V_i < 207'2 \text{ V}}$$

$$D_2 \rightarrow i_D = \frac{-0'7 - V_i}{2R} < 100 \text{ mA}$$

$$-0'7 - V_i < 200 \Rightarrow V_i > -200'7 \text{ V} \quad \boxed{-200'7 < V_i < 207'2}$$

$$\cancel{-V_i < 200'7} \quad \cancel{V_i >}$$


$$D_2 \rightarrow P_{\text{máx}} \rightarrow P = VI \Rightarrow I = \frac{P}{V} = \frac{600 \text{ mW}}{7'5 \text{ V}} = 80 \text{ mA}$$

Cartagena99


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

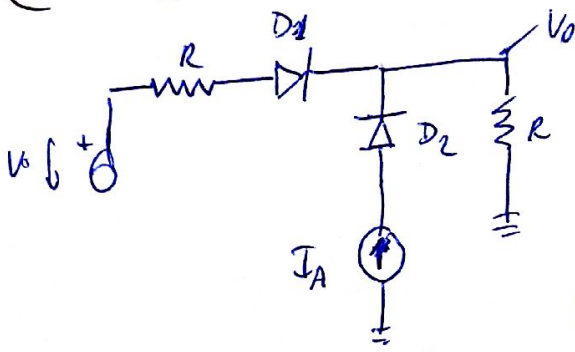(11) $I_A = 25\text{mA}$ $R = 1\text{k}\Omega$



Suponemos D_1 ON, $I_D = 0$

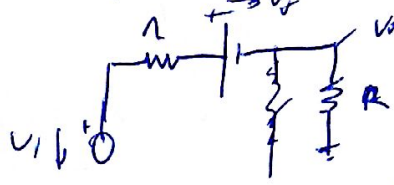

~~$V_i - i_D R - 0.7 - i_D R$~~


~~$V_i = 0.7$~~

~~$V_i - 0.7 - 0.7 - V_o$~~

$V_i - V_o \geq 0.7$

$$\left. \begin{aligned} S. \quad V_i - V_o \geq 0.7 \quad D_1 \text{ ON} \\ V_i - V_o < 0.7 \quad D_1 \text{ OFF} \end{aligned} \right\}$$


Suponemos D_2 ON, $I_D = 0$

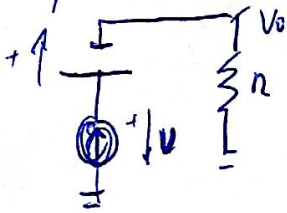

$U - 0.7 - V_o = 0$

$$\left. \begin{aligned} S. \quad U - V_o \geq 0.7 \quad D_2 \text{ ON} \\ U - V_o < 0.7 \quad D_2 \text{ OFF} \end{aligned} \right\}$$

HIP 1. D_1 OFF. D_2 ON

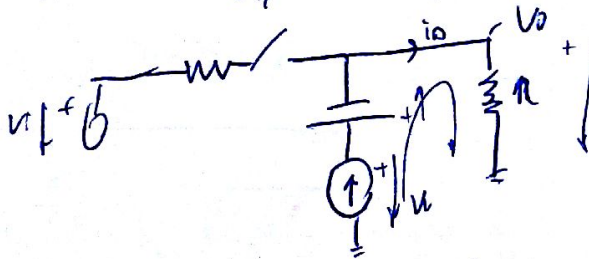

$I_D = 2.5\text{mA}$

~~$i_D = \frac{U - 0.7}{R}$~~

$V_o = 2.5\text{mA} \cdot 1\text{k}\Omega = 2.5\text{V}$

~~$V_o = 0.7 + U$~~

~~$V_o = i_D R = \frac{U - 0.7}{R} \cdot R = U - 0.7$~~

Comprobamos D_1 OFF $\rightarrow V_i - V_o < 0.7$
 $V_i - 2.5 \times 0.7$
 $V_i < 3.2$ ✓

HIP 2 $V_i \geq 3.2 \rightarrow D_1$ ON
 D_2 ON

$V_i - i_D R - 0.7 - (i_A + i_D) R = 0$



CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70




ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

$V_o = \left(\frac{V_i - 3.2}{2} + 2.5 \right) \cdot 1\text{k}$ $V_i \geq 3.2 \rightarrow V_o \geq 2.5$

V_i	D_1	D_2	V_o
$V_i \leq 3'2$	OFF	ON	$2'5$
$V_i > 3'2$	ON	ON	$(2'5 + \frac{V_i - 3'2}{2}) 1k$

(9) $V_{i2} = 7'5$ $I_{L, \min} = 4 \text{ mA}$, $P_{T, \max} = 600 \text{ mW}$, $R_L = 3 \text{ k}\Omega$ $R_F = 1 \text{ k}\Omega$

Suponemos D_2 ON , $I_D = 0$

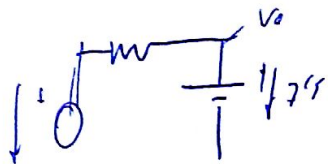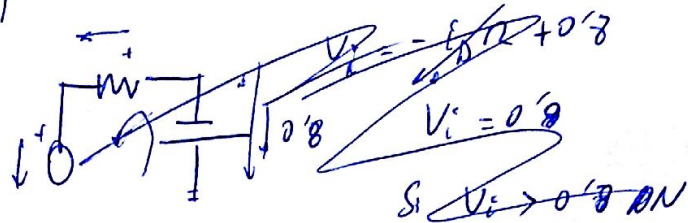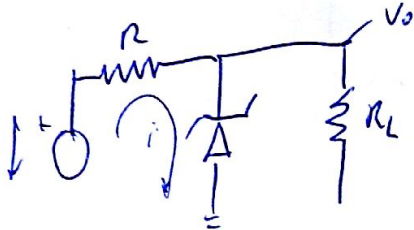

$$V_i - i_D R - 7'5 = 0$$

$$V_i = 7'5$$


$V_o > 7'5 \rightarrow D_2$ RUPTURA

$$V_o V_i = -\frac{V_o}{R} - 0'8$$


$$V_i \leq 0'8 \text{ ON}$$

$$V_o \leq -0'8$$

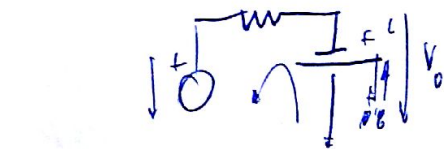$V_o \leq -0'8$ ON
 $-0'8 < V_o < 7'5$ OFF
 $V_o > 7'5$ RUPT.



HIPÓ $\rightarrow D_2$ OFF

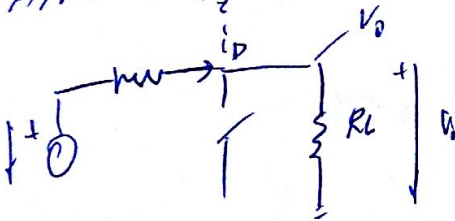


$$V_o = V_i \frac{3}{3+1} = V_i \frac{3}{4} \Rightarrow V_o = \frac{3}{4} V_i$$

$$D_2 \text{ OFF} \rightarrow -0'8 < \frac{3}{4} V_i < 7'5$$

$$-1'06 < V_i < 10$$

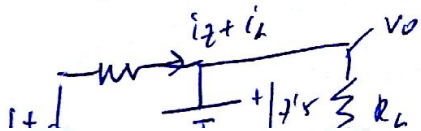Si $V_i > 10 \rightarrow V_o > 7'5$ Rupt.



$$V_o = i_D R$$

$$V_o = 7'5$$

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

Cartagena99

Continuación de (9)

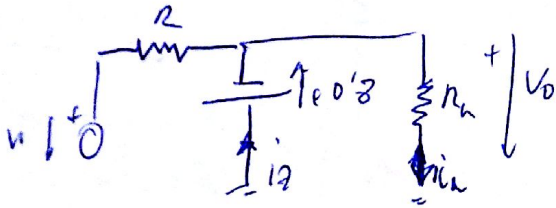(5)

$$\text{Si } V_o \leq -1'06 \rightarrow V_o \leq -0'8 \text{ ON}$$



$$V_o = -0'8 \quad V_o = -i_k \cdot R \rightarrow i_k = -\frac{V_o}{R} = -\frac{-0'8}{3} = 0'26$$

$$0 - 0'8 - (i_2 + i_k)R = V_i$$

$$i_2 = -V_i - 0'8 - 0'26$$

$$i_2 = -V_i - 1'06$$


Mirar en Hojas

Cartagena99


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

(13) $|V_2| = 5'6$

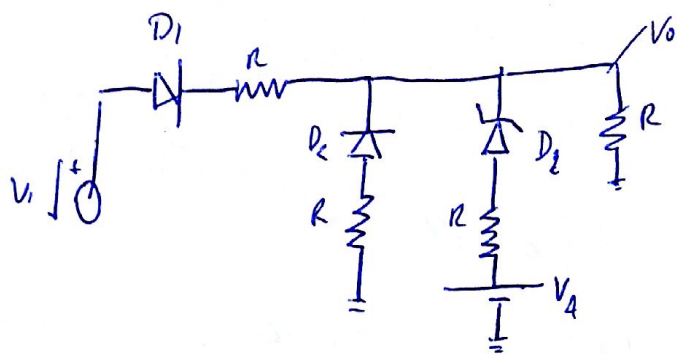

Suponemos D_3 ON, $I_D = 0$

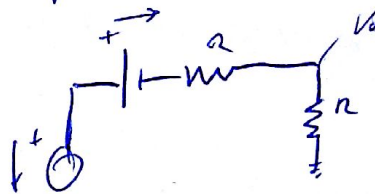


$$V_i - 0'7 - I_D R = 0$$

$$V_i - 0'7 = 0 \Rightarrow V_i = 0'7$$


$D_1 \rightarrow$ $\begin{cases} \text{Si } V_i > 0'7 \text{ ON} \\ \text{Si } V_i < 0'7 \text{ OFF} \end{cases}$

Suponemos D_2 ON, $I_D = 0$

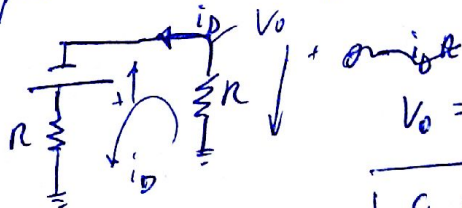

$$V_o = -0'7 + i_D R$$

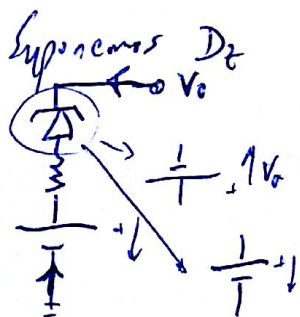$D_2 \rightarrow$ $\begin{cases} \text{Si } V_o \leq -0'7 \text{ ON} \\ \text{Si } V_o > -0'7 \text{ OFF} \end{cases}$



$$V_o = -0'8 - \frac{I_D}{2} R + V_A$$


$$V_o - V_A \leq -0'8 \text{ ON}$$

$$V_o = 5'6 + V_A$$

$$V_o - V_A > 5'6 \text{ Ruptura}$$

$D_3 \rightarrow$ $\begin{cases} \text{Si } V_o - V_A \leq -0'8 \text{ ON} \\ \text{Si } -0'8 < V_o - V_A < 5'6 \text{ OFF} \\ \text{Si } V_o - V_A > 5'6 \text{ RUPTURA} \end{cases}$

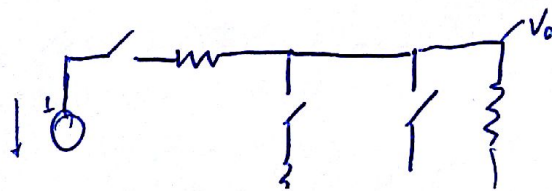HIPO $\rightarrow D_1$ OFF D_2 OFF D_3 OFF



$$V_o = V_i$$

$$V_D = 0$$

D_1 OFF $\rightarrow V_i - V_o < 0'7 \Rightarrow V_i < 0'7 \checkmark$

D_2 OFF $\rightarrow V_o > -0'7 \Rightarrow \checkmark$

D_3 OFF $\rightarrow -0'8 < -4 < 5'6 \checkmark$
 \downarrow
 $-4 \leq -0'8 \rightarrow \text{ON}$

HIPI $\rightarrow D_1$ OFF D_2 OFF D_3 ON

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70



Si $V_i > 2'3 \rightarrow D_1 ON$

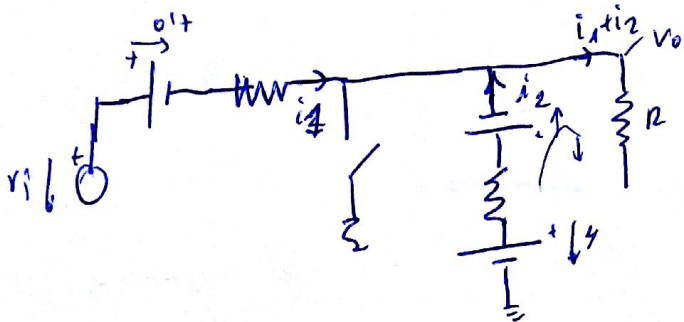(6)

HPP 2 $\rightarrow D_1 ON D_2 OFF D_2 ON$



$$V_0 = (i_1 + i_2)R \quad V_0 = V_i - 0'7 - i_1 R$$

$$\textcircled{1} V_i - 0'7 - i_1 R - (i_1 + i_2)R = 0$$

$$\textcircled{2} 4 - i_2 R - 0'7 - (i_1 + i_2)R = 0$$

$$\Rightarrow \begin{cases} (V_i - 0'7 - 2i_1 R - i_2 R = 0) \\ (3'2 - i_1 R - 2i_2 R = 0) \end{cases}$$

$$\Rightarrow \begin{cases} 2V_i - 1'4 - 3'2 - 3i_1 R = 0 \Rightarrow i_1 = \frac{2V_i - 4'6}{3R} \end{cases}$$

$$V_0 = V_i - 0'7 - \left(\frac{2V_i - 4'6}{3R} \right) R = \frac{V_i + 2'5}{3}$$

Comprobamos

$$D_2 OFF \rightarrow V_0 > -0'7$$

$$\frac{V_i + 2'5}{3} > -0'7 \rightarrow V_i > 2'3$$


Comprobamos

$$D_2 ON \rightarrow V_0 - 4 \leq -0'8 \Rightarrow V_0 \leq 3'2$$

$$\frac{V_i + 2'5}{3} \leq 3'2 \Rightarrow V_i \leq 7'1$$

Si $V_i > 7'1 \rightarrow$ Posiblemente $D_2 OFF$

HPP 3 $D_1 ON D_2 OFF D_2 OFF$

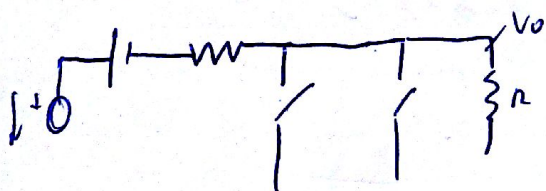

$$\begin{cases} V_i - 0'7 - i_D R = V_0 \\ i_D = \frac{V_i - 0'7}{2R} \end{cases} \Rightarrow V_0 = i_D R = \frac{V_i - 0'7}{2}$$

Comprobamos

$$D_1 ON \rightarrow V_i - V_0 > 0'7 \rightarrow V_i - \frac{V_i - 0'7}{2} > 0'7 \Rightarrow \frac{V_i + 0'7}{2} > 0'7 \rightarrow V_i > 7'1$$

$$D_2 OFF \rightarrow V_0 > -0'7 \rightarrow \frac{V_i - 0'7}{2} > -0'7 \rightarrow 3'2 > -0'7$$

$$D_2 OFF \rightarrow -0'8 < \left(\frac{V_i - 0'7}{2} - 4 \right) < 5'6 \quad \text{ERROR}$$




CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

HIP 4 Si $V_i > 19'4 \rightarrow D_2$ Repetido

D_1 ON

D_2 OFF

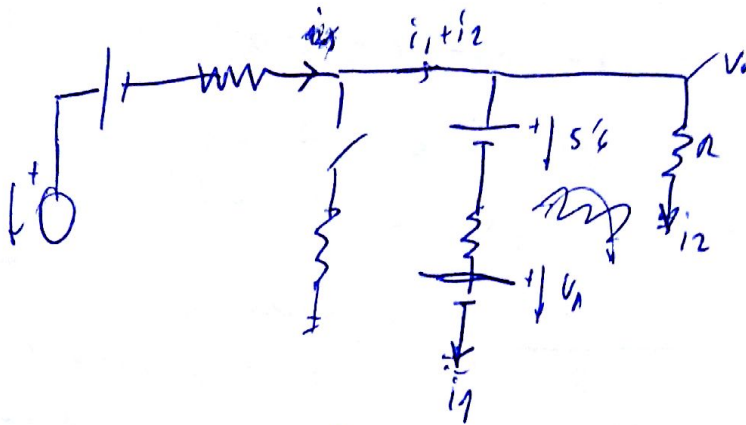

$$V_o = i_2 R$$

~~$$V_i - 0'7 =$$~~

$$(1) V_i - 0'7 - (i_1 + i_2)R - i_2 R = 0$$

$$(2) \text{ ~~} V_i - 0'7 = \text{~~$$

$$V_i - 0'7 - (i_1 + i_2)R - 5'6 - i_1 R - 4 = 0$$

$$\Rightarrow \begin{cases} (V_i - 0'7 - i_1 R - 2i_2 R = 0) \\ (V_i - 10'3 - 2i_1 R - i_2 R = 0) \end{cases} \Rightarrow \begin{cases} V_i + 8'9 - 3i_2 R = 0 \\ V_i - 10'3 - 2i_1 R - i_2 R = 0 \end{cases} \Rightarrow \boxed{i_2 = \frac{V_i + 8'9}{3R}}$$

$$\boxed{V_o = \frac{V_i + 8'9}{3}}$$

Comprobado

$$D_1 \text{ ON} \rightarrow V_i - V_o > 0'7 \rightarrow \text{OK} \checkmark$$

$$D_2 \text{ OFF} \rightarrow V_o > -0'7 \quad 9'6 > -0'7 \checkmark$$

$$D_2 \text{ OFF} \rightarrow V_o - V_A > 5'6 \rightarrow 9'6 - 4 > 5'6 \rightarrow 5'6 > 5'6 \checkmark$$

TABLA


V_i	D_1	D_2	D_2	V_o
$V_i < 2'3$	OFF	OFF	ON	1'6

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

Cartagena99


1) $V_A = 3.3$ $R = 2K$

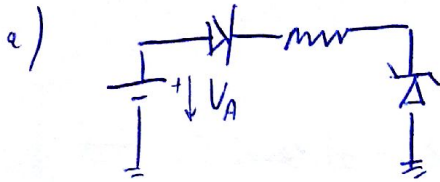

$V_A > 0.7 \rightarrow D_1 ON$


$V_A = 10; i_D = \frac{V_A - 0.7 - 3.3}{2} = 3mA$

Suponemos $D_1 ON$ $D_2 Rupt$ $I_D = 0$

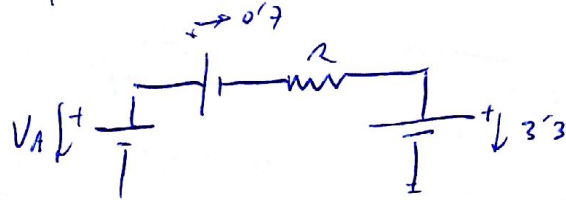


$V_A - 0.7 - I_D R - 3.3 = 0$

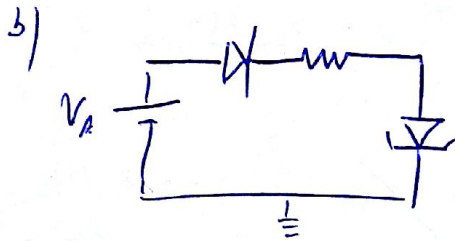$V_A = 4$ Si $V_A > 4 \rightarrow D_1 ON$ $D_2 Rupt$
 Si $V_A < 4 \rightarrow D_1 OFF$



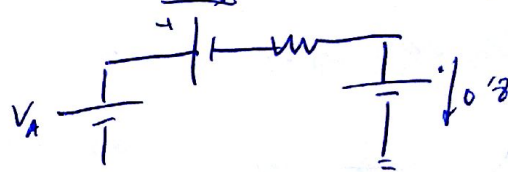
Para que circule $I > 0 \rightarrow D_1 ON$ $D_2 ON$




$V_A = 10; i_D = \frac{V_A - 0.7 - 0.7}{2} = 4.25mA$ $V_A - 0.7 - I_D R - 0.7 = 0$

$V_A = 1.5 \rightarrow$ Si $V_A > 1.5 \rightarrow D_1 ON$
 Si $V_A < 1.5 \rightarrow D_1 OFF$

4) $I_{max} = 5mA$, $R = 1K\Omega$

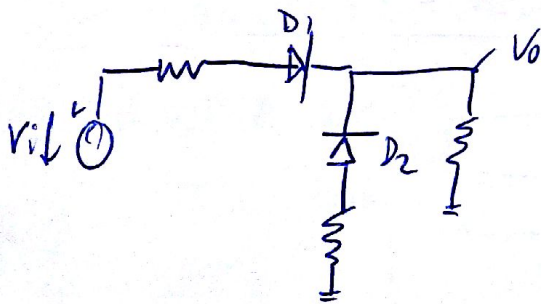

a) Suponemos $D_1 ON$, $I_D = 0$

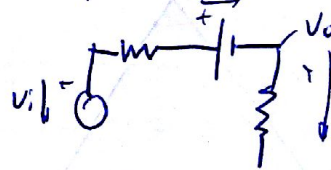

$V_i - \frac{i_D R}{R} - 0.7 = V_o$
 $V_i - V_o = 0.7$

Si $V_i - V_o > 0.7 \rightarrow D_1 ON$
 Si $V_i - V_o < 0.7 \rightarrow D_1 OFF$

b) Suponemos $D_2 ON$, $I_D = 0$




$V_o = -0.7$

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

Cartagena99

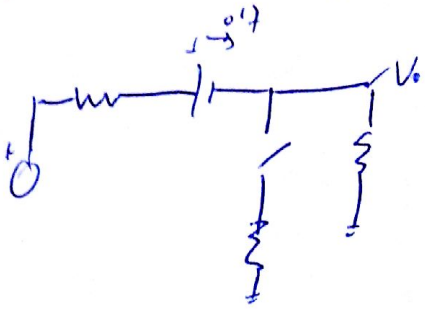Si $V_i > 0.7 \rightarrow D_1$ ON D_2 OFF



$$i_D = \frac{V_i - 0.7}{2R}$$

$$V_o = i_D R = \frac{V_i - 0.7}{2} \Rightarrow \boxed{V_o = \frac{V_i - 0.7}{2}}$$

Comprobamos

$$D_2 \text{ OFF} \rightarrow V_o > -0.7$$

$$\frac{V_i - 0.7}{2} > -0.7$$

$$D_1 \text{ ON} \rightarrow V_i - V_o > 0.7$$


$$\boxed{V_i > -0.7}$$

Si $-0.7 < V_i < 0.7 \rightarrow D_1$ OFF D_2 OFF

$$V_i - \frac{V_i - 0.7}{2} > 0.7$$

$$\frac{V_i + 0.7}{2} > 0.7$$

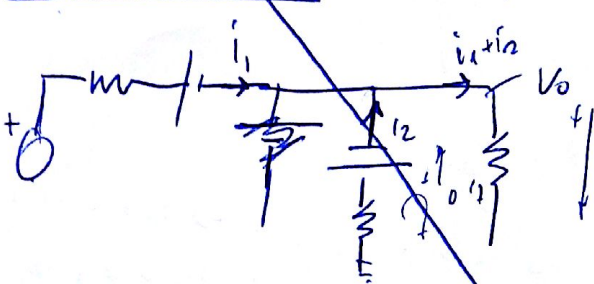Si $V_i \leq -0.7 \rightarrow D_2$ ON D_1 ON



$$V_o = V_i - 0.7 - i_1 R$$

$$V_i - i_1 R - 0.7 - (i_1 + i_2) R = 0$$

$$0 - i_2 R - 0.7 - (i_1 + i_2) R = 0$$

$$\Rightarrow \begin{cases} (V_i - 0.7 - 2i_1 R - i_2 R = 0) \\ -(-0.7 - i_1 R - 2i_2 R = 0) \end{cases} \Rightarrow \begin{cases} 2V_i - 1.4 + 0.7 - 3i_1 R = 0 \\ 0.7 + i_1 R + 2i_2 R = 0 \end{cases}$$

$$\boxed{I_1 = \frac{2V_i - 0.7}{3R}}$$

$$V_o = V_i - 0.7 - \left(\frac{2V_i - 0.7}{3R} \right) R = \boxed{V_o = \frac{V_i - 1.4}{3}}$$

Comprobamos

$$D_1 \text{ ON} \rightarrow V_i - V_o > 0.7 \Rightarrow V_i > 0.7 + V_o \Rightarrow \boxed{V_i > 0} \rightarrow D_1 \text{ ON}$$

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

Cartagena99


b)
$$D_1 \rightarrow \frac{V_i - 0.7}{2R} < 100 \mu A \rightarrow V_i - 0.7 < 100 \Rightarrow \boxed{V_i < 100.7 V}$$

~~Diagram~~

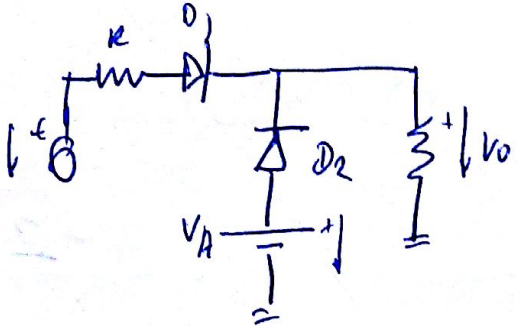5) $V_A = 2V, I_{max} = 50 \mu A, R = 1K$



a) Suponemos D_1 ON, $I_D = 0$

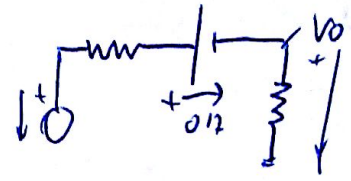


$$V_i - I_D R - 0.7 - V_o = 0$$

$$V_i - V_o = 0.7$$

$$D_1 \rightarrow \begin{cases} \text{Si } V_i - V_o > 0.7 \text{ ON} \\ V_i - V_o < 0.7 \text{ OFF} \end{cases}$$


b) Suponemos D_2 ON, $I_D = 0$

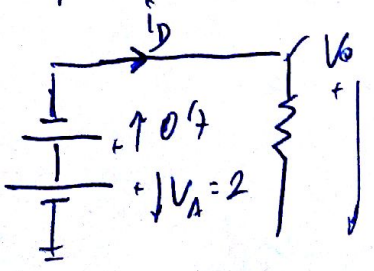

$$V_o = -0.7 + 2 = 1.3$$

$$D_1 \rightarrow \begin{cases} \text{Si } V_o > 1.3 \text{ ON} \\ V_o < 1.3 \text{ OFF} \end{cases}$$

HIPO + D_1 OFF D_2 OFF

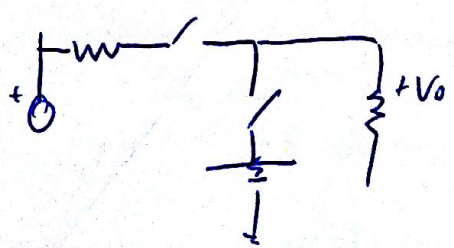

$$\begin{cases} V_o = 0 \\ V_o = V_i \end{cases}$$

Comprobamos

$$D_1 \text{ OFF} \rightarrow V_i - V_o < 0.7 \rightarrow V_i < 0.7 \checkmark$$

$$D_2 \text{ OFF} \rightarrow V_o < 1.3 \rightarrow 0 < 1.3 \checkmark$$

$$\text{Si } V_i > 0.7 \rightarrow D_1 \text{ ON}$$

Cartagena99

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70

Comprobamos $D_1 ON \rightarrow V_i - V_o > 0.7 \rightarrow V_i - \left(\frac{V_i - 0.7}{2}\right) > 0.7 \Rightarrow \frac{V_i + 0.7}{2} > 0.7 \Rightarrow$

$\Rightarrow V_i > 0.7 \checkmark$

$V_i > 3.3 \rightarrow D_2 ON$

HIP 2 $D_1 ON$ $D_2 ON$

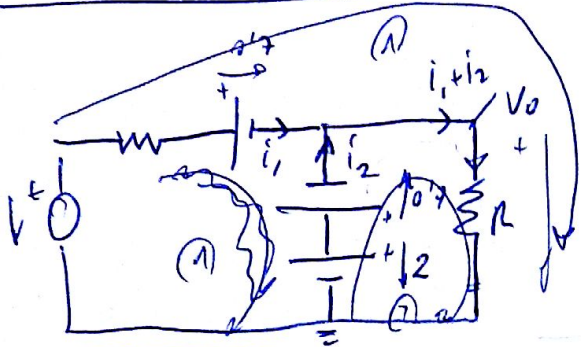

$V_o = -0.7 + 2 = 1.3$

① $V_i - i_1 R - 0.7 - (i_1 + i_2)R = 0$

② $0.2 - 0.7 - (i_1 + i_2)R = 0$
 $V_o = -0.7 + 2 + (i_1 + i_2)R + 0.7 - 2 = 0$

$\Rightarrow \begin{cases} V_i - 0.7 - 2i_1 R - i_2 R = 0 \\ -(1.3 - i_1 R - i_2 R) = 0 \end{cases}$

$V_i - 0.7 + 1.3 - i_1 R = 0 \Rightarrow i_1 = \frac{V_i + 0.6}{R}$

$V_o = -0.7 - i_1 R + V_i$

Comprobamos

~~$D_1 ON \rightarrow V_i - V_o > 0.7 \Rightarrow V_i > 2$~~

$V_o = V_i - 0.7 - \left(\frac{V_i + 0.6}{R}\right)R \Rightarrow V_o = -0.7 - 0.6 = -1.3 + 1.3$

Comprobamos

$D_1 ON \rightarrow V_i - V_o > 0.7 \rightarrow V_i > 1.0.7 + V_o \Rightarrow V_i > 2 \text{ " } 3.3 > 2 \checkmark$

$D_2 ON \rightarrow V_o > 1.3 \rightarrow 1.3 > 1.3 \checkmark$

TABLA

V_i	D_1	D_2	V_o
	ON	OFF	1.3

b) Para no saturar $D_1 \rightarrow$

$i_D = \frac{V_i - 0.7}{R} < 50 \text{ mA}$

Cartagena99

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
 LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
 CALL OR WHATSAPP: 689 45 44 70