

Electrical Systems

Lecture 5: Electric power in AC systems II



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering


Last revised: March 15, 2021

Outline

- 1 **Grid Thévenin equivalent and short-circuit power**
- 2 Power network and the Thévenin equivalent circuit
- 3 Maximum average power transfer Theorem
- 4 Counter-example on the reactive power definition
- 5 Exercises and solutions

Grid Thévenin equivalent and short-circuit power

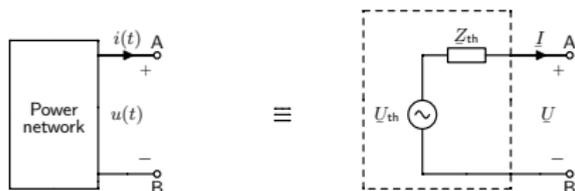A power network is often described by its short-circuit power. Consider the power network (left) that can be represented by its Thévenin equivalent circuit (right)



Short-circuit power of a network

Short-circuit power is the maximum power that a network (or source) is able to supply. The short-circuit power is defined as


$$S_{sc} = U_{th} I_{sc}$$

From the Thévenin equivalent circuit, it can be obtained as


$$S_{sc} = U_{th} I_{sc}^* = \frac{U_{th}^2}{Z_{th}^*}$$

and
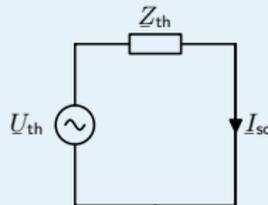
$$Z_{th} = \frac{U_{th}^2}{S_{cc}} \quad \left(\text{or } X_{th} = \frac{U_{th}^2}{S_{cc}} \text{ if only reactance is considered} \right)$$



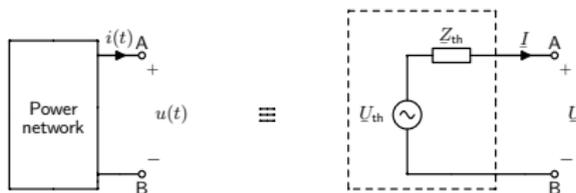Grid Thévenin equivalent and short-circuit power



Weak grids

A power grid is said to be weak if its equivalent impedance Z_{th} is high or, equivalently, if its short-circuit power is low.

In opposite...

Ideal power grid

An ideal power grid has zero equivalent impedance, $Z_{th} = 0$, and infinity short-circuit power.

Grid Thévenin equivalent and short-circuit power

Exercise 1

A load described by an impedance $\underline{Z}_L = 100 + j68\Omega$ is connected to a power grid 400V, with $S_{sc} = 16\text{kVA}$ and its equivalent impedance fulfils $R_{th} = X_{th}$.

- 1 Calculate the voltage at the connection point, the dissipated power in the transmission lines and the efficiency of the electrical transmission.
- 2 Repeat the calculations of the previous question assuming that $\underline{Z}_L = 100\Omega$.
- 3 Consider that power network is modified such that $S_{sc} = 32\text{kVA}$ and its equivalent impedance fulfils $R_{th} = X_{th}$. Calculate again the voltage at the end of the line, dissipated power and efficiency (assuming unitary power factor).


Outline

- 1 Grid Thévenin equivalent and short-circuit power
- 2 Power network and the Thévenin equivalent circuit**
- 3 Maximum average power transfer Theorem
- 4 Counter-example on the reactive power definition
- 5 Exercises and solutions

Power network and the Thévenin equivalent circuit


Thévenin equivalent scheme with a power defined load

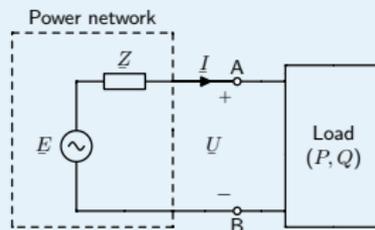Consider a load, operating at $S = P + jQ$, connected to a power grid represented by an Thévenin equivalent circuit with E and Z .



Which is the voltage across the load?

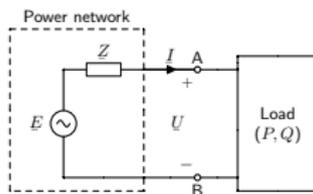Power network and the Thévenin equivalent circuit



Writing the KVL, using that $\underline{S}^* = \underline{U}^* \underline{I}$, and after some algebra we get

The voltage across a load connected to a power grid can be calculated using...

$$U^4 + (2RP + 2XQ - E^2) U^2 + (R^2 + X^2)(P^2 + Q^2) = 0$$

or


$$U^4 + (2\text{Re}(\underline{Z}\underline{S}^*) - E^2) U^2 + Z^2 S^2 = 0$$

Additionally, the equivalent impedance of the load, \underline{Z}_{PQ} , and its current and voltage (with respect to the voltage source) are, respectively,

$$\underline{Z}_{PQ} = \frac{U^2}{\underline{S}^*}, \quad \underline{I} = \frac{\underline{E}}{\underline{Z} + \underline{Z}_{PQ}}, \quad \underline{U} = \frac{\underline{Z}_{PQ}}{\underline{Z} + \underline{Z}_{PQ}} \underline{E} = \underline{Z}_{PQ} \underline{I}$$

Power network and the Thévenin equivalent circuit

Exercise 2

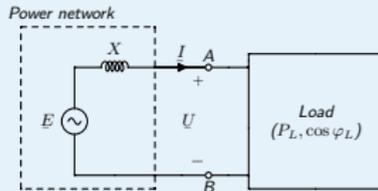

An electrical load is connected to a 230V power network.

- 1 Find the active power and power factor of the load if $X = 1.2\Omega$ and the power supplied by the generator is 2kW and a current measurement shows 10.87A.
- 2 Find the reactance of the power network if the measured voltage across the load is 223V and the power consumed by the load is 2kW with 0.8(i) power factor.


Outline

- 1 Grid Thévenin equivalent and short-circuit power
- 2 Power network and the Thévenin equivalent circuit
- 3 Maximum average power transfer Theorem**
- 4 Counter-example on the reactive power definition
- 5 Exercises and solutions


Maximum average power transfer Theorem

How we can maximize the amount of power transferred from a source to a load?

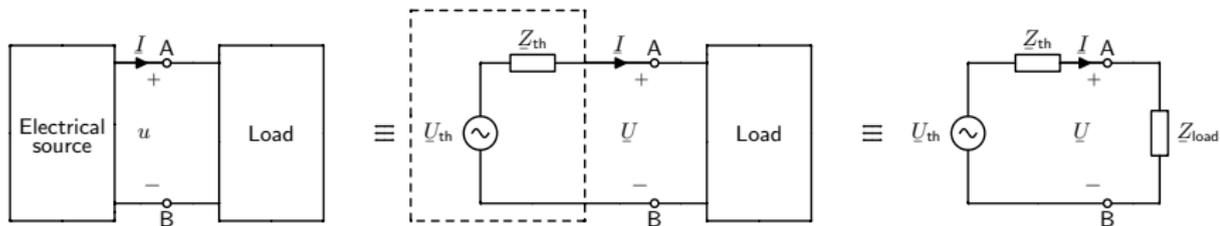Assume we have a load connected to a power network represented by its Thévenin equivalent circuit. The goal is to determine the value of the load impedance (Z_{load}) that permits the maximum power delivery to Z_{load} .



Maximum average power transfer Theorem

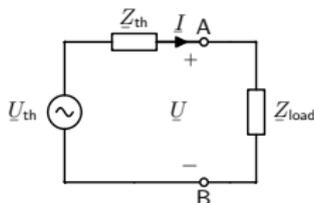

Where

$$\underline{Z}_L = Z_L \angle \phi_L = R_L + jX_L$$

$$\underline{Z}_{th} = Z_{th} \angle \phi_{th} = R_{th} + jX_{th}$$

$$\underline{U}_{th} = U_{th} \angle 0^\circ$$

The average power, or the active power, equation is given by

$$P_L = U_{Lrms} I_{Lrms} \cos \phi_L$$

and using

$$I_{Lrms} = \frac{1}{|\underline{Z}_{th} + \underline{Z}_L|} U_{th} \quad U_{Lrms} = \frac{|\underline{Z}_L|}{|\underline{Z}_{th} + \underline{Z}_L|} U_{th} \quad \cos \phi_L = \frac{R_L}{|\underline{Z}_L|}$$

where $|\underline{Z}_L| = \sqrt{R_L^2 + X_L^2}$ and $|\underline{Z}_{th} + \underline{Z}_L| = \sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}$

$$P_L = \frac{R_L}{(R_L + R_{th})^2 + (X_L + X_{th})^2} U_{th}^2$$

Maximum average power transfer Theorem

For one hand, the power

$$P_L = \frac{R_L}{(R_L + R_{th})^2 + (X_L + X_{th})^2} U_{th}^2$$

has a maximum if $X_L = -X_{th}$. Then

$$P_L = \frac{R_L}{(R_L + R_{th})^2} U_{th}^2$$

the maximum power transfer for resistive case is recovered, which has a maximum for $R_L = R_{th}$.

The maximum average power transfer is given by

$$\underline{Z}_L = R_L + jX_L = R_{th} - jX_{th} = \underline{Z}_{th}^*$$

If the load impedance is purely resistive, $\underline{Z}_L = R_L$, the condition is obtained by computing $\frac{dP_L}{dR_L}$ to

$$P_L = \frac{R_L}{(R_L + R_{th})^2 + (X_{th})^2} U_{th}^2$$


and

$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$

Maximum average power transfer Theorem

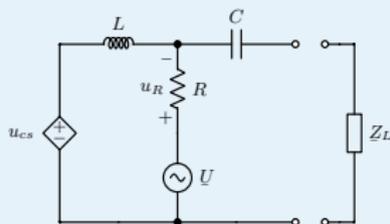Exercise 3

From the circuit below with $R = 2\Omega$, $X_L = 4\Omega$, $X_C = 2\Omega$, $U = 4V$ and $u_{cs}(t) = u_R(t)$,



Find the value of impedance load, Z_L , for maximum average power transfer, and the average power delivered to the load.

Outline


- 1 Grid Thévenin equivalent and short-circuit power
- 2 Power network and the Thévenin equivalent circuit
- 3 Maximum average power transfer Theorem
- 4 Counter-example on the reactive power definition**
- 5 Exercises and solutions

Counter-example on the reactive power definition

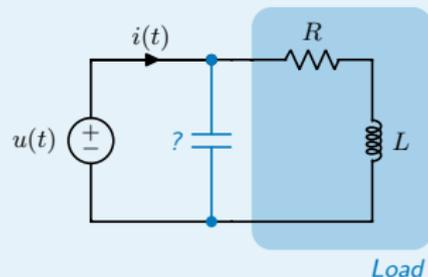Exercise 4

An RL load, with values $R = 1\Omega$ and $L = 2H$, is connected to a power grid with a voltage with the form $u(t) = 10\sqrt{2}\cos(t)$ V.

- 1 Calculate the active, apparent, reactive powers and power factor.
- 2 Find a parallel capacitor that fully compensates the reactive power.
- 3 If $u(t) = 10\sqrt{2}\cos(5t)$ V, calculate, with the designed capacitor from the previous question, the new active, apparent, reactive powers and power factor.




Counter-example on the reactive power definition

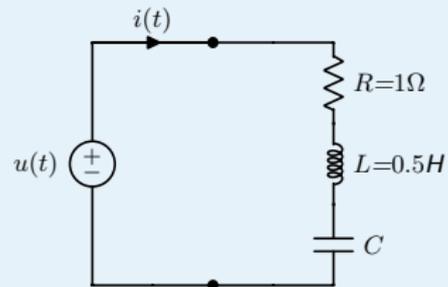Exercise 5

A series RLC load is connected to a power grid with a voltage source of the form $u(t) = 100\sqrt{2} \cos(t) + 100\sqrt{2} \cos(3t) \text{ V}$. Calculate the active, apparent, reactive powers and power factor, for both Loads A and B.

- 1 Load A: with $C = 2/3 \text{ F}$.
- 2 Load B: with $C = 2/7 \text{ F}$.




Hint: Active and apparent powers are $S = \sqrt{\sum_k U_k^2} \sqrt{\sum_k I_k^2}$ and $P = \sum_k U_k I_k \cos \phi_k$, respectively. The reactive power, from Budeanu's definition, is $Q = \sum_k U_k I_k \sin \phi_k$.

Outline

- Grid Thévenin equivalent and short-circuit power
- Power network and the Thévenin equivalent circuit
- Maximum average power transfer Theorem
- Counter-example on the reactive power definition
- 5** ● Exercises and solutions

Exercises I

Exercise 6

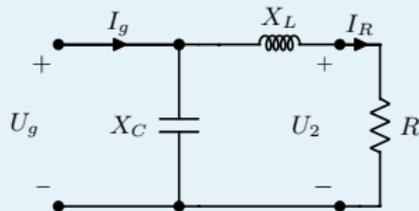

CM2: A bulb lamp with nominal values 150V, 1500W, is connected to a 250V power grid, in series with an inductive reactance such that the voltage across the lamp is 150V. Additionally, a capacitor is connected in parallel to achieve unitary power factor. Calculate:

- 1 Reactive power of the inductor and capacitor.
- 2 Lamp and grid currents.


Exercises II

Exercise 7

CM10: The voltage source in the Figure on the right has a series reactance of 1Ω . The load is consuming $P_L = 10\text{kW}$ with $PF = 0.8$ (inductive) and the voltage across the load terminals is 220V . The parallel capacitor is designed such that the source current is minimal.

Calculate:

- 1 The short circuit power of the voltage source.
- 2 The value of the capacitor that ensures minimal current supplied by the voltage source.
- 3 If the load is disconnected, which is the voltage across the capacitor?

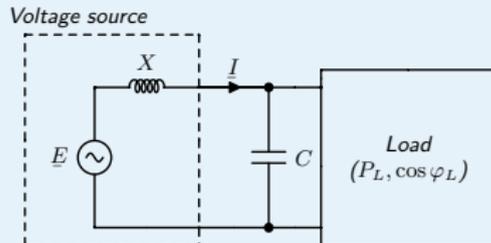

Exercises III

Exercise 8

CM16: A 2.4MW, 7.5kV load is connected to two voltage sources in parallel with the following properties:


- Voltage source 1: $\underline{U}_{01} = 7.5\angle 0^\circ \text{ kV}$, $\underline{Z}_{th1} = 8 + j15\Omega$
- Voltage source 2: $\underline{U}_{02} = 7.0\angle 10^\circ \text{ kV}$, $\underline{Z}_{th2} = 5.6 + j19.2\Omega$

Find:

- 1 The Thévenin equivalent circuit of the parallel voltage sources.
- 2 If the load voltage is 7.5kV, which is the total reactive power supplied by the sources?
- 3 The complex power supplied by each source.

Exercises IV

Exercise 9

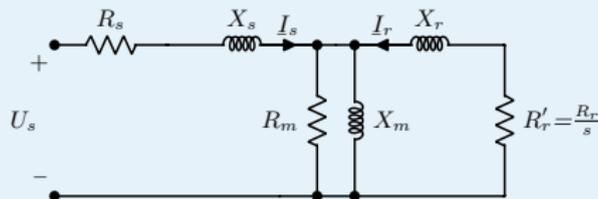

CM56: The circuit above represents an induction motor connected to a voltage source $U_s = 220 \text{ V}$, where s is the slip relating the current speed with the synchronous one. If the motor parameters are $R_s = R_r = X_s = X_r = 1 \ \Omega$, $R_m = 50 \ \Omega$ and $X_m = 100 \ \Omega$, find:

- 1 Stator and rotor currents (I_r, I_s) when starting ($s = 1$).
- 2 Consumed active and reactive powers when starting ($s = 1$).
- 3 The power consumed in the resistor R'_r is proportional to the torque produced by the motor. Calculate this power when starting ($s = 1$).
- 4 One wants to reduce the consumed current by reducing the supplied voltage U_g . Which is the required voltage if the desired current is 5 times less than the nominal one?

Solutions I

Solution to Exercise 1

- 1 $U = 369.91\text{V}$, $P_{\text{los}} = 66.16\text{W}$, $\eta = 93.39\%$
- 2 $U = 372.77\text{V}$, $P_{\text{los}} = 98.25\text{W}$, $\eta = 93.39\%$
- 3 $U = 386.12\text{V}$, $P_{\text{los}} = 52.70\text{W}$, $\eta = 96.58\%$

Solution to Exercise 2

- 1 $P = 2\text{kW}$, $PF = 0.827$
- 2 $X = 1.014\Omega$

Solution to Exercise 3

The equivalent Thévenin/Norton circuits are defined by

$$U_{\text{th}} = 3 + j\text{V}, I_N = 1 + j2\text{A}, Z_{\text{th}} = 1 - j1\Omega$$

Then, the load that maximises the consumed power is $Z_L = 1 + j1\Omega$.

Solutions II

Solution to Exercise 4

- 1 $P = 20\text{W}$, $S = 44.72\text{VA}$, $Q = 40\text{var}$, $PF = 0.4472$
- 2 $C = 0.4\text{F}$
- 3 $P = 0.99\text{W}$, $S = 190.1\text{VA}$, $Q = -190.1\text{var}$, $PF = 0.005$

Solution to Exercise 5

- 1 Load A: $P = 10\text{kW}$, $S = 14.14\text{kVA}$, $PF = 0.7071$, $Q = 0\text{var}$
- 2 Load B: $P = 10\text{kW}$, $S = 14.14\text{kVA}$, $PF = 0.7071$, $Q = 0\text{var}$

Solution to Exercise 6

- 1 $Q_L = Q_C = 2000\text{var}$
- 2 $I_R = 10\text{A}$, $I_g = 6\text{A}$

Solutions III

Solution to Exercise 7

- 1 $S_{sc} = 50.467\text{kVA}$
- 2 $C = 493.25\mu\text{F}$, $E = 22.465\text{V}$
- 3 $U_C = 265.85\text{V}$

Solution to Exercise 8

- 1 $U_{th} = 7.308\text{kV}$, $Z_{th} = 3.557 + j8.526\Omega$
- 2 $Q = -2.057\text{Mvar}$
- 3 $\underline{S}_1 = 1.117 - j0.970\text{MVA}$, $\underline{S}_2 = 1.283 - j1.087\text{MVA}$

Solutions IV

Solution to Exercise 9

- 1 $I_r = 76.631\text{A}$, $I_s = 78.934\text{A}$
- 2 $P = 12.338\text{kW}$, $Q = 12.22\text{kvar}$, $PF = 0.7105$
- 3 $P = 5.872\text{kW}$
- 4 $U_s = 44\text{V}$

Electrical Systems

Lecture 5: Electric power in AC systems II



Arnau Dòria-Cerezo

✉ arnau.doria@upc.edu

Dept. Electrical Engineering, and
Inst. of Industrial and Control Engineering

Last revised: March 15, 2021