
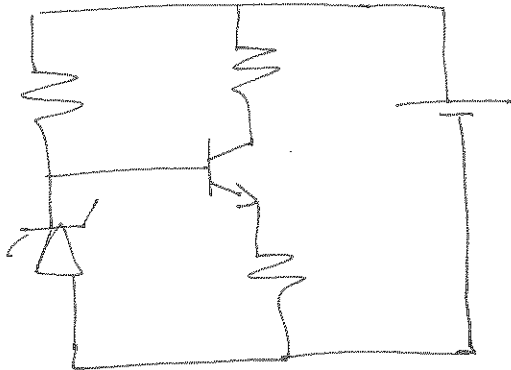


Solución:

a) Circuito DC

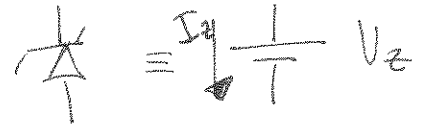

Zener en ruptura



Malla B-E

$$V_Z = V_{BE} + I_E R_3 \Rightarrow I_E = \frac{V_Z - V_{BE}}{R_3}$$

Si activa $\Rightarrow I_E = \frac{6.3 - 0.7}{2K} = 2.8 \text{ mA}$

$$I_B = \frac{2.8 \text{ mA}}{201} = 13.93 \mu\text{A} \quad I_C = 2.786 \text{ mA}$$


Malla C-E

$$V_{CE} = 15 - I_C R_2 - I_E R_3 = 2.43 \text{ V} > 0.2 \text{ V} \checkmark$$

Comprobamos $I_Z > 0$

$$I_Z = I_{R_1} - I_B = \frac{15 - 6.3}{R_1} - 13.93 \mu\text{A} = 7.236 \text{ mA} \checkmark$$

b)

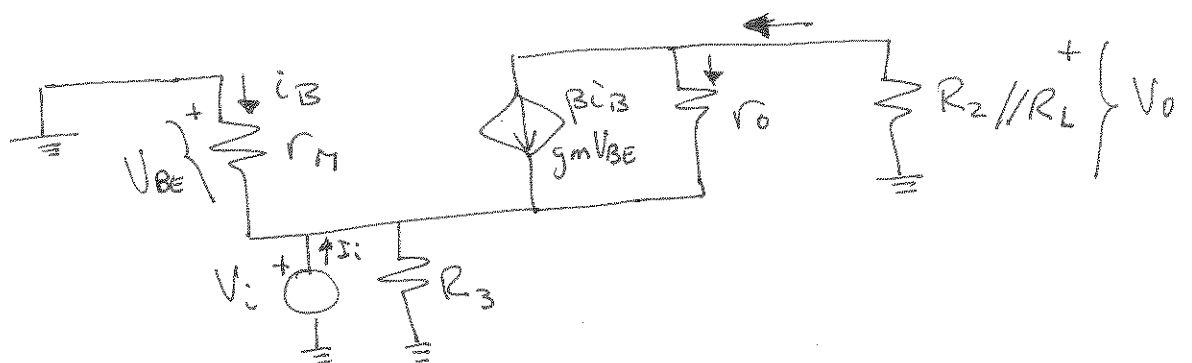

c) con efecto Early:

$$g_m = 108 \text{ m}\Delta/\text{V}$$

$$V_i = -V_{be}$$

$$R_2 // R_L = 2 \text{ K}\Omega$$

$$r_o = 8'97 \text{ K}\Omega$$

$$r_{\pi} = 1'85 \text{ K}\Omega$$

$$-\frac{V_o}{R_2 // R_L} = g_m V_{be} + \frac{V_o - V_i}{r_o} \Rightarrow$$

$$\left(g_m + \frac{1}{r_o}\right) V_i = \left(\frac{1}{R_2 // R_L} + \frac{1}{r_o}\right) V_o$$

Amplificador

No inversor


Base común

$$\Rightarrow \Delta v = \frac{V_o}{V_i} = \frac{g_m + \frac{1}{r_o}}{\frac{1}{R_2 // R_L} + \frac{1}{r_o}} = 176'8$$

sin efecto Early ($r_o \rightarrow \infty$) $\Rightarrow \Delta v = g_m (R_2 // R_L) = 216$

d) $R_{IN} = \frac{V_i}{I_i} = \frac{V_i}{\frac{V_i}{r_{\pi}} + \frac{V_i}{R_3} + g_m V_i} = \frac{1}{\frac{1}{r_{\pi}} + \frac{1}{R_3} + g_m} = 9'17 \Omega$

circuito para R_{out}

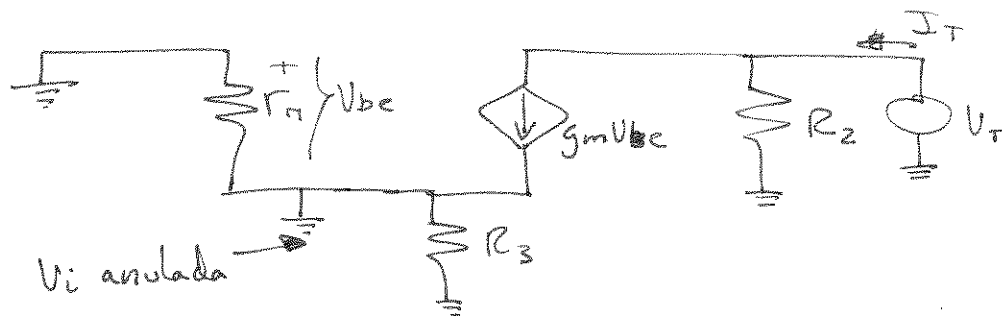

$$V_{be} = 0 \Rightarrow g_m V_{be} = 0 \Rightarrow R_{out} = \frac{V_T}{I_T} = R_2 = 2'5 \text{ K}\Omega$$

e) ① Límite activa-saturación: $\left. \begin{array}{l} U_{CE} = 0,2V \\ i_C = \beta i_B \end{array} \right\} i_E = (\beta + 1) i_B$

Malla C-E

$$15V = \beta i_B \cdot 2,5K + 0,2V + (\beta + 1) i_B \cdot 2K$$

$$\hookrightarrow i_B = \frac{15 - 0,2}{2,5K \beta + (\beta + 1) 2K} = 16,4 \mu A \Rightarrow I_C = 3,28 mA$$

Malla B-E

$$V_Z = U_{BE} + (\beta + 1) i_B \cdot 2K = 7,29V$$

Comprobamos I_Z

$$I_Z = I_R - I_B = \frac{15 - 7,29}{1,2K} - 16,4 \mu A = 6,4 mA$$

② estaremos en saturación

C-E: $15V = i_C \cdot 2,5K + 0,2 + i_E \cdot 2K$

B-E: $V_Z = 0,7V + i_E \cdot 2K$

OTRA: $15V = (4mA + i_B) \cdot 1,2K + V_Z$

KCL: $i_E = i_C + i_B$

$$15V = (i_E - i_B) \cdot 2,5K + 0,2 + i_E \cdot 2K = 4,5K i_E + 0,2 - i_B \cdot 2,5K$$

$$15V = (4mA + i_B) \cdot 1,2K + 0,7 + i_E \cdot 2K = 2K i_E + 0,7 + (4mA + i_B) \cdot 1,2K$$

$$\Rightarrow \begin{cases} 14,8 = 4,5K i_E - i_B \cdot 2,5K & (\times 1,2) \\ 9,5 = 2K i_E + i_B \cdot 1,2K & (\times 2,5) \end{cases}$$

~~$$41,51 = 10,4K i_E$$~~

$$\rightarrow i_E = 3,99 mA$$

$$\Rightarrow i_B = 1,26 mA$$

$$i_C = 2,73 mA$$

$$i_C < \beta i_B \checkmark$$

$$V_Z = 8,68V$$

// Diodo Zener ON $\Rightarrow \frac{1}{T} 0,7V \Rightarrow$ el transistor está en el límite corte-activa $\Rightarrow I_E = I_C = I_B = 0$