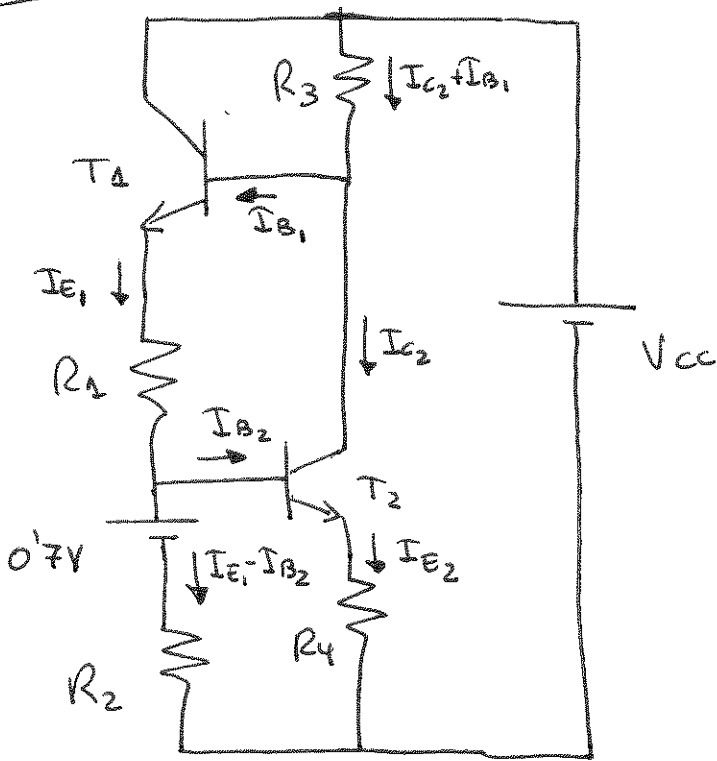


a) DC



Suponemos:

Diodes en directa

T₁ en activa

T₂ en activa

$$V_{BE1} = V_{BE2} = 0.7V$$

$$I_{C1} = \beta I_{B1}$$

$$I_{C2} = \beta I_{B2}$$

MALLA BE1: $V_{CC} = (I_{C2} + I_{B1}) R_3 + V_{BE1} + I_{E1} \cdot R_1 + 0.7 + (I_{E1} - I_{B2}) R_2 \Rightarrow$

MALLA BE2: $0.7 + (I_{E1} - I_{B2}) R_2 = V_{BE2} + I_{E2} \cdot R_4 \rightarrow$

$$\rightarrow (\beta + 1) I_{B1} R_2 = (\beta + 2) I_{B2} R_4$$

$$\Rightarrow V_{CC} = 1.4 + (\beta R_3 - R_2) I_{B2} + [R_3 + (\beta + 1) R_1 + (\beta + 1) R_2] I_{B1} =$$

$$= 1.4 + (\beta R_3 - R_2) \frac{(\beta + 1) R_2}{(\beta + 2) R_4} I_{B1} + [R_3 + (\beta + 1) (R_1 + R_2)] I_{B1} \rightarrow$$

$$\rightarrow I_{B1} = \frac{V_{CC} - 1.4}{(\beta R_3 - R_2) \frac{(\beta + 1) R_2}{(\beta + 2) R_4} + [R_3 + (\beta + 1) (R_1 + R_2)]} = 13.6 \mu A$$

$$\rightarrow I_{C1} = 3.4 mA$$

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

...

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

Corrientes positivas

Cartagena99

aprox. $\left\{ \begin{array}{l} I_{B1} \approx 0 \quad (I_{E1} \approx I_{C1}) \text{ porque } I_{R3} = I_{C2} - I_{B1} \approx I_{C2} \\ I_{B2} \approx 0 \quad (I_{E2} \approx I_{C2}) \text{ porque } I_{R2} = I_{E1} - I_{B2} \approx I_{E1} \end{array} \right.$

$\nearrow \gg I_{B1}, I_{B2}$ ya que $\beta = 250$

MALLA BE1 $V_{CC} = I_{C2}R_3 + V_{BE1} + I_{E1}R_1 + 0.7 + I_{E1}R_2$

MALLA BE2 $0.7 + I_{E1}R_2 = V_{BE2} + I_{E2}R_4 \rightarrow I_{E1} = I_{E2} \frac{R_4}{R_2} \approx I_{C2} \frac{R_4}{R_2}$

$\rightarrow V_{CC} = 1.4 + I_{C2}R_3 + (R_1 + R_2) I_{C2} \frac{R_4}{R_2} \rightarrow$

$\rightarrow I_{C2} = \frac{V_{CC} - 1.4}{R_3 + (R_1 + R_2) \frac{R_4}{R_2}} = 4.25 \text{ mA}$

$\rightarrow I_{C1} = I_{C2} \frac{R_4}{R_2} = 3.4 \text{ mA}$

MALLA CE1: $V_{CC} = V_{CE1} + I_{E1}R_1 + 0.7 + (I_{E1} - I_{B2})R_2 \rightarrow V_{CE1} = 10.9 \text{ V} > 0.2 \text{ V}$ OK

MALLA CE2: $V_{CC} = (I_{C2} + I_{B1})R_3 + V_{CE2} + I_{E2}R_4 \rightarrow V_{CE2} = 2.25 \text{ V} > 0.2 \text{ V}$ OK

DIODO ON si: $I_{E1} - I_{B2} > 0$ OK

$I_{E1} - I_{B2} \approx 3.4 \text{ mA} < I_{max} = 25 \text{ mA}$ OK


b) $V_{CE1} = V_{BE1} + (I_{C2} + I_{B1})R_3 > V_{BE1} > 0.2 \text{ V}$ NO



CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

c) AC

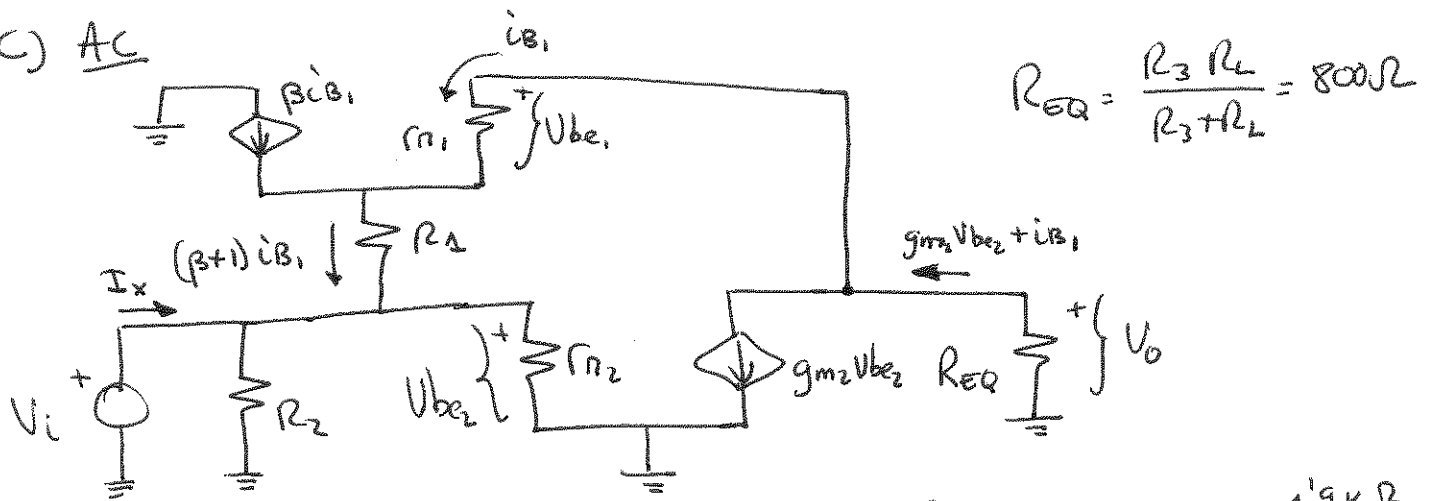

$$R_{EQ} = \frac{R_3 R_L}{R_3 + R_L} = 800 \Omega$$

$$g_{m1} = \frac{I_{CQ1}}{V_T} = 131.8 \text{ mA/V} \quad r_{\pi 1} = 1.9 \text{ k}\Omega$$

$$g_{m2} = \frac{I_{CQ2}}{V_T} = 164.7 \text{ mA/V} \quad r_{\pi 2} = 1.52 \text{ k}\Omega$$

$$V_o = -(g_{m2} V_{be2} + i_{B1}) R_{EQ} \Rightarrow$$

$$V_i = V_{be2}$$

$$(g_{m2} V_{be2} + i_{B1}) \cdot R_{EQ} + r_{\pi 1} \cdot i_{B1} + (\beta + 1) i_{B1} R_1 + V_{be2} = 0 \rightarrow$$

$$\rightarrow (g_{m2} R_{EQ} + 1) V_{be2} = - (R_{EQ} + r_{\pi 1} + (\beta + 1) R_1) i_{B1} \rightarrow$$

$$\rightarrow i_{B1} = - \frac{g_{m2} R_{EQ} + 1}{R_{EQ} + r_{\pi 1} + (\beta + 1) R_1} V_{be2}$$

$$\Rightarrow V_o = - \left[g_{m2} V_i + \left(- \frac{g_{m2} R_{EQ} + 1}{R_{EQ} + r_{\pi 1} + (\beta + 1) R_1} \right) V_i \right] R_{EQ} \Rightarrow$$

$$c4) \Rightarrow \frac{V_o}{V_i} = -g_{m2} R_{EQ} + \frac{(g_{m2} R_{EQ} + 1) R_{EQ}}{R_{EQ} + r_{\pi 1} + (\beta + 1) R_1} = -130.14$$

$$c5) \quad R_1 = \infty \rightarrow R_{EQ} = 2.4 \text{ k}\Omega \rightarrow \frac{V_o}{V_i} \text{ max} = -381.1$$

Cartagena99


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

$$c2) R_{out} = \frac{V_x}{I_x} = \left[\frac{1}{R_2} + \frac{1}{r_{\pi 2}} + \frac{(g_{m2} R_{EA} + 1)(\beta + 1)}{R_{EA} + r_{\pi 1} + (\beta + 1) R_A} \right]^{-1} = 1'95 \Omega$$

$$I_x = \frac{V_x}{R_2} + \frac{V_x}{r_{\pi 2}} - (\beta + 1) i_{B1} = \frac{V_x}{R_2} + \frac{V_x}{r_{\pi 2}} + (\beta + 1) \frac{g_{m2} R_{EA} + 1}{R_{EA} + r_{\pi 1} + (\beta + 1) R_A} V_x$$

c3) Comprobamos el cálculo de R_{out} :

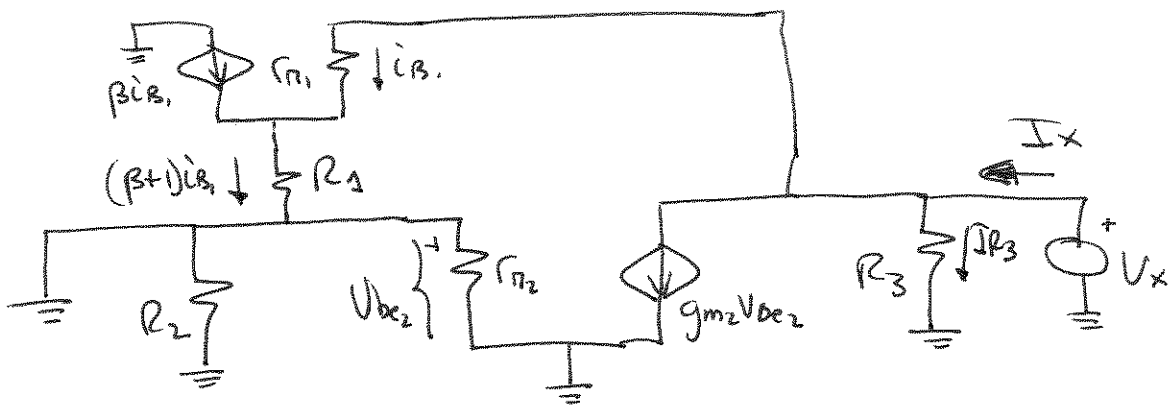

$$V_{be2} = 0 \rightarrow g_{m2} V_{be2} = 0 \rightarrow I_x = I_{R3} + i_{B1}$$

$$V_x = i_{B1} r_{\pi 1} + (\beta + 1) i_{B1} R_A = [r_{\pi 1} + (\beta + 1) R_A] i_{B1}$$

$$I_x = \frac{V_x}{R_3} + i_{B1} = \frac{V_x}{R_3} + \frac{V_x}{r_{\pi 1} + (\beta + 1) R_A}$$

$$\rightarrow R_{out} = \frac{V_x}{I_x} = \left[\frac{1}{R_3} + \frac{1}{r_{\pi 1} + (\beta + 1) R_A} \right]^{-1} = 2'314 \text{ K}\Omega \quad \underline{\underline{OK}}$$

Cartagena99

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70


ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

$$\text{Si } V_{be2} = 10 \text{ mV} \rightarrow V_{be1} = 305 \text{ mV}$$

$$\text{Si } V_{be1} = 10 \text{ mV} \rightarrow V_{be2} = 2'6 \text{ mV} < 10 \text{ mV} \quad \underline{\underline{OK}}$$

$$V_o = -130'14 V_i = -130'14 V_{be2} = \frac{130'14}{3'85} V_{be1} \approx 338mV$$

d) DC

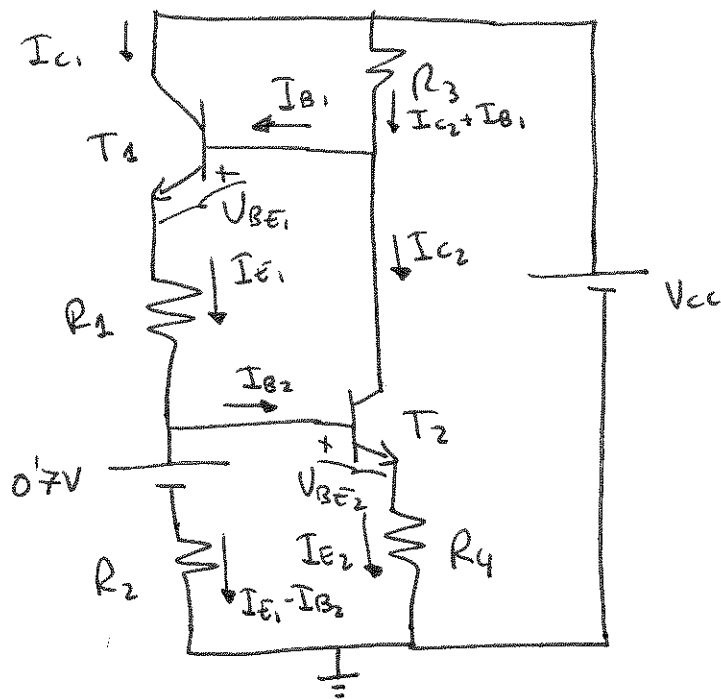

Malla en la parte superior izquierda:

$$0'7V + (I_{E1} - I_{B2})R_2 = V_{BE2} + I_{E2}R_4$$

Si T2 limite activa-corte:

$$V_{BE2} = 0'7V \quad I_{B2} = I_{E2} = 0$$

$$\hookrightarrow I_{E1} = 0 \quad T1 \text{ corte}$$

ambos transistores pasan a activa simultaneamente.

Ambos transistores limite corte-activa:

$$V_{BE1} = V_{BE2} = 0'7V$$

$$I_{B1} = I_{E1} = I_{C1} = I_{B2} = I_{C2} = I_{E2} = 0$$

$$\left. \begin{array}{l} V_{BE1} = V_{BE2} = 0'7V \\ I_{B1} = I_{E1} = I_{C1} = I_{B2} = I_{C2} = I_{E2} = 0 \end{array} \right\} V_{CC} = 0 \cdot R_3 + V_{BE1} + 0 \cdot R_1 + V_{BE2} + 0 \cdot R_4 = \underline{\underline{1'4V}}$$

aprox. valida si ambos transistores en activa

e) aprox. $\left\{ \begin{array}{l} I_{B2} \approx 0 \rightarrow I_{E2} \approx I_{C2} \\ I_{E1} \approx 0 \rightarrow I_{E1} \approx I_{C1} = I_{MAX} = 25mA \end{array} \right.$

$$I_{C2} = 31'25mA$$


CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70

Cartagena99

P1

DC

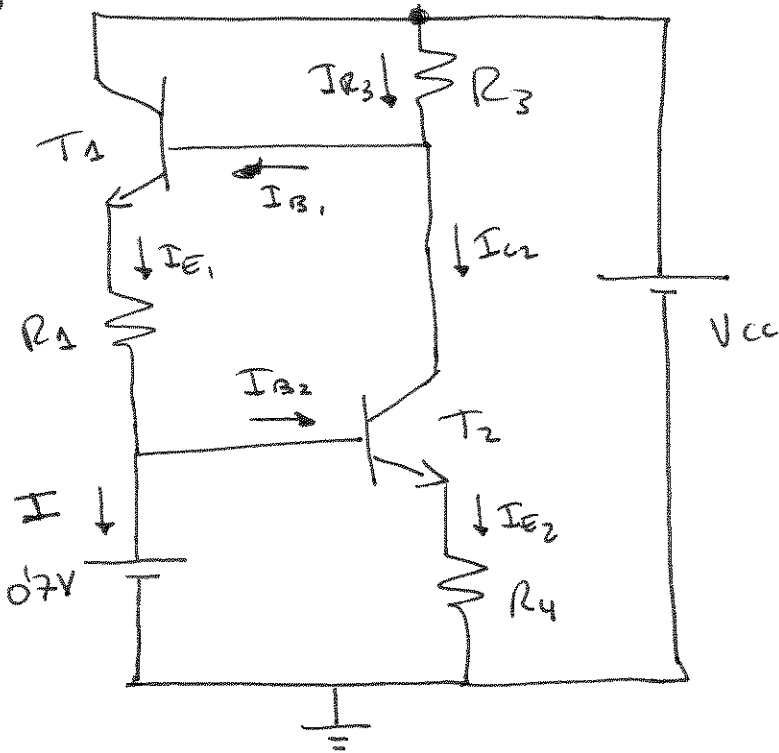

MALLA BE2

$$0.7V = V_{BE2} + I_{E2} R_4$$

$$\rightarrow I_{E2} = 0$$

T2 en limite activa-corte

$$I_{B2} = I_{C2} = I_{E2} = 0$$

$$\Rightarrow \begin{cases} I_{R3} = I_{B1} \\ I = I_{E1} \end{cases}$$

MALLA BE1: $V_{CC} = I_{B1} R_3 + V_{BE1} + I_{E1} R_1 + 0.7V$

Sup T1 en activa

$$I_{B1} = \frac{V_{CC} - 1.4}{R_3 + (\beta + 1) R_1} = 208.75 \mu A$$

$$I_{C1} = 52.99 \text{ mA}$$

$$I_{E1} = 52.4 \text{ mA}$$

MALLA CE1: $V_{CE1} = V_{BE1} + I_{B1} R_3 = 1.2V > 0.2V$ OK

MALLA CE2: $V_{CE2} = V_{CC} - I_{B1} R_3 = 14.5V > 0.2V$ OK

$$I = I_{E1} = 52.4 \text{ mA} \begin{cases} > 0 & \text{sup. diodo ON} & \underline{\underline{OK}} \\ > 25 \text{ mA} & \text{se supera la } I_{MAX} & \underline{\underline{OK}} \end{cases}$$

Cartagena99

CLASES PARTICULARES, TUTORÍAS TÉCNICAS ONLINE
LLAMA O ENVÍA WHATSAPP: 689 45 44 70

ONLINE PRIVATE LESSONS FOR SCIENCE STUDENTS
CALL OR WHATSAPP: 689 45 44 70